

# Contents

Preface	v
Introduction	1
Three-Phase Diode Bridge Rectifier	7
Principles of Current Injection	23
Current Injection Devices	31
The Optimal Third-Harmonic Current Injection	73
Current Injection Networks for the Third-Harmonic Current Injection	91
The Optimal Current Injection	117
Current Injection Networks for the Optimal Current Injection	127
Operation of the Rectifier in the Discontinuous Conduction Mode	141
Recovery of the Current Injection Network Power Applying a Current-Loaded Resistance Emulator	165
Recovery of the Current Injection Network Power Applying a Voltage-Loaded Resistance Emulator	193
Current Injection Applying a Switching Current Injection Device	233

Rectifiers that Apply Square-Wave Current Injection	267
Conclusions	303
References	307
Index	311

Three-Phase Diode Rectifiers with Low Harmonics  
Current Injection Methods

Pejovic, P.

2007, VIII, 318 p., Hardcover

ISBN: 978-0-387-29310-3