

Contents

Part I Essentials

1	Amps, Pre-amps, Pre-pre-amps	3
1.1	Purpose of the Book	3
1.2	Type 1 Phono-Amp	6
1.3	Type 2 Phono-Amp	6
1.4	Type 3 Phono-Amp	7
2	RIAA Transfer/Anti-RIAA Transfer	9
2.1	Introduction	9
2.2	Cutting Process with Anti-RIAA	9
2.3	Decoding with RIAA Transfer	10
2.4	RIAA Transfer: Ideal Situation	11
2.5	RIAA Transfer: Real Situation	14
2.6	Deviation Between Ideal and Real Situation: Calculated	14
2.7	Deviation Between Ideal and Real Situation: Simulated	16
3	Vinyl Record Reference Levels	17
3.1	Introduction	17
3.2	Cutting Modulations	17
3.2.1	Lateral Modulation	17
3.2.2	Vertical Modulation	17
3.2.3	45°/45° Modulation (Flank Modulation FM)	18
3.3	Test Records and Measurement/Calculation Methods	19
3.3.1	Cartridge Equivalent Circuit	19
3.3.2	Nominal Cartridge Data	21
3.4	Cartridge Output Voltages from Different Test Records	21
3.4.1	TSR 1005: 5 cm/s Lateral	22
3.4.2	TSR 1007: 3.54 cm/s 45°	23
3.4.3	DIN: 8 cm/s 45°+11.3 cm/s Lateral and Vertical	23

3.4.4 No-Name: 5 cm/s 45°	24
3.4.5 Other: 10 cm/s and 12 cm/s Lateral	25
3.5 Cartridge Output Voltages at Different Load Resistances	25
3.5.1 Questions	25
3.5.2 Answers	25

Part II Noise Basics

4 Noise in Components and Other General Noise Effects	31
4.1 Introduction	31
4.2 Amplifier Noise Model	32
4.3 Noise Voltages and Currents	33
4.4 1/f-Noise	33
4.5 Resistor (Johnson) Noise	35
4.6 Noise Voltage Sources Sequence-Connected	36
4.7 Noise Voltage Sources Parallel-Connected	37
4.8 Noise Current Sources Parallel-Connected	38
4.9 Noise Current Sources Sequence-Connected	38
4.10 Paralleling of Active Devices	40
4.11 Sequence of Two Amplifying Stages	41
4.12 Noise Factor and Noise Figure	43
4.13 Optimum Source Resistance	46
4.14 Signal-to-Noise Ratio	49
4.15 Weighted and/or Equalized SN	49
4.16 Excess Noise of Resistors	50
5 Noise in Bipolar Junction Transistors	55
5.1 BJT Noise Model	55
5.2 Base Spreading Resistance: Calculation Approach	55
5.3 Noise Model for BJT Plus Source	59
5.4 Noise Contribution of a Second Stage (Contribution Allowed)	61
5.5 Selection of Low-Noise BJTs and Ranking via Noise Factor Calculation	62
5.6 CE Gain Stage	67
5.7 CE Gain Stage Noise Model	70
5.8 CE Gain Stage Example Calculation Incl. Excess Noise	71
5.9 Base Spreading Resistance $r_{bb'}$: Measurement Approach	74
5.10 Optimal Source Resistance RS_{opt} and Optimal Collector Current $I_{C,opt}$	75
6 Noise in Field Effect Transistors	77
6.1 Introduction	77
6.2 Noise Voltage Relevant Data Sheet Plots	77
6.3 JFET Noise Model	79

6.4	Noise Current Calculation	80
6.5	Noise Voltage Calculation	80
6.6	JFETs and MC Input Stages	81
6.7	1/f-Noise	81
6.8	MC Case Noise Figures	82
6.9	JFETs and MM Input Stage	83
6.10	MM Case Noise Figures	83
6.11	Optimal Source Resistance	84
6.12	CS Gain Stage Calculations	85
6.13	Miller Capacitance	87
6.14	SRPP Gain Stage	88
6.15	Cascoded Gain Stage	89
6.16	Weighted SN Calculation	92
6.17	Example Calculation for a Low-Noise Gain Stage	92
7	Noise in Valves (US: Tubes)	95
7.1	Introduction	95
7.2	Triode Noise Model	95
7.3	Triode Noise Resistance	96
7.4	Triode Noise Voltage	97
7.5	Pentode Noise Resistance	100
7.6	Pentode Noise Voltage	101
7.7	Triode Noise Calculations Incl. 1/f-Noise	102
	7.7.1 Note to the Valve Manufacturing Industry	105
7.8	Selection of Low-Noise Valves	105
7.9	Cathode Resistance Noise and the Triode Cathode Input Resistance	107
7.10	Example Calculation for a Common Cathode Stage (CCS) with a Low-Noise Double-Triode in Parallel Operation	108
	7.10.1 The Calculation Course for the Un-Bypassed ("u") Version	112
	7.10.2 The Calculation Course for the Bypassed ("b") Version	115
7.11	Noise Model of the CCS Gain Stage	118
	7.11.1 Warning	119
7.12	Constant Current Generator	120
7.13	The CCA = CCS with a CCG as Anode Load	122
7.14	The SRPP Gain Stage	126
7.15	Cathode Followers CFA and CF	128
7.16	The μ -Follower Gain Stage μ -F	131
7.17	Differential (Balanced) Gain Stage with CCG as the Cathode Current Sink (DIFA)	134
7.18	Determination of Triode Constants and the Triode's Noise Production	135

7.19	Average Noise Resistance r_{Nc} in B_{20k}	139
7.20	The Circuit Worsening Factor W_z	140
7.21	Remarks on Valve Power Supplies	141
7.22	Additional Observations	144
7.23	Additional Negative Valve SN Effects	148
7.24	Summary	150
8	Noise in Operational Amplifiers	153
8.1	Introduction	153
8.2	Series Configuration	153
8.3	Shunt Configuration	154
8.4	Noise Relevant Features of the Series and Shunt Op-Amp Configuration	154
8.5	Series Configured Noise Model	157
8.6	Series Configuration Example Calculation for Noise Voltage, Noise Current, SN, NF	157
8.7	Shunt Configured Noise Model	158
8.8	Shunt Configuration Example Calculation for Noise Voltage, Noise Current, SN, NF	159
8.9	1/f-Noise Effects	160
8.10	Optimal Source Resistance	161
8.11	Noise Gain of a Shunt Configured Op-Amp	163
9	Noise in Instrumentation Amps	165
9.1	Introduction	165
9.2	Basic Op-Amp and In-Amp Gain Setting Options	165
9.3	In-Amp Noise Model with Two Different i/p Sources	165
9.4	In-Amp Noise Model with Two Equal i/p Sources	168
9.5	In-Amp Noise Model with Floating i/p Source	169
9.6	In-Amp Noise Model with an Un-Balanced i/p Source	170
9.7	Example Calculation for a Floating i/p Source	171
9.8	Example Calculation for a Grounded i/p Source	172
9.9	In-Amp IC Circuitry Topologies	174
9.10	Draft Design of a Lowest-Noise In-Amp	177
10	Noise in Transformers	179
10.1	Introduction	179
10.2	Turns Ratio	179
10.3	Frequency and Phase Response	180
10.4	Transformer and MC Cartridge Classification	181
10.5	Transformer Equations: Ideal Situation	181
10.6	Transformer Equations: Real Situation	183
10.7	SN Example Calculations	184
10.8	The Noise Voltage Approach (Approach 1)	185
10.9	The Noise Figure Approach (Approach 2)	186

10.10	Delta of Approach 1 Versus Approach 2	189
10.11	Q & A	190
11	Noise of Vinyl Records: On How Much Phono-Amp SN is Needed?	201
11.1	Introduction	201
11.2	Cutting Technologies: Lacquer and DMM	201
11.3	DMM Process	202
11.4	Third Octave DMM Spectral Noise Density	202
11.5	Step by Step Vinyl Record SN Calculation	204
11.6	NF of Neumann Phono-Amp PUE 74	204
11.7	SN of the Shure V15V MM Cartridge	205
11.8	SN of the VR MOTHER	213
11.9	Noise Voltage of the VR MOTHER	214
11.10	Transfer Factor of a Cartridge	214
11.11	Worst Case SNs for a VR	215
11.12	Sum of Two SNs	217
11.13	Cartridge O/P Voltage Correction Factor	217
11.14	SNs of a Selection of MM and MC Phono-Amps	217
11.15	DMM SN Measurement Set-Up	220
11.16	Neumann PUE 74 Details	220
12	Noise Basics: Mathcad Worksheets	225
12.1	MCD-WS: Amp NF_e Calculations for Various Source Resistances (Eqs. (4.50) ff)	227
12.2	MCD-WS: OP27 NF_e Calculation (Fig. 4.13)	228
12.3	MCD-WS: Resistor Excess Noise Calculation (Fig. 4.17)	229
12.4	MCD-WS: BJT $r_{bb'}$ Calculation (Eq. (5.11))	230
12.5	MCD-WS: BJT Excess Noise Calculations (Eqs. (5.36) ff)	231
12.6	MCD-WS: BJT Optimal Source Resistance (Eq. (4.54))/ Optimal Collector Current (Eq. (5.47) ff)	234
12.7	MCD-WS: BJT Voltage Noise and Current Noise Density vs. Collector Current (Figs. 5.3 and 5.4)	236
12.8	MCD-WS: JFET f_{ce} Calculation (Eq. (6.8) ff)	238
12.9	MCD-WS: JFET NF Calculations (Eqs. (6.9) ff)	239
12.10	MCD-WS: JFET NF_e vs. RS Calculations (Fig. 6.6)	241
12.11	MCD-WS: JFET SN Calculations (Figs. 6.10 and 6.11)	242
12.12	MCD-WS: Triode (E88CC) NF and SN Calculations of a CCS and a CCA (Figs. 7.7, 7.11, 7.22 and 7.23) ...	243
12.13	MCD-WS: Triode (E88CC) NF and SN Calculations of a SRPP (Fig. 7.13)	254
12.14	MCD-WS: Triode (E88CC) NF and SN Calculations of a μ -F (Fig. 7.15)	260
12.15	MCD-WS: Op-Amp Series Configured Noise Calculations (Eqs. (8.9) ff)	267

12.16 MCD-WS: Op-Amp Shunt Configured Noise Calculations (Eqs. (8.17) ff)	269
12.17 MCD-WS: Op-Amp Optimal Source Resistance, Noise Factor and SN Graphs (Figs. 8.7 and 8.8)	271
12.18 MCD-WS: In-Amp Draft Design NF and SN Calculations (Figs. 9.17–9.19)	274
12.19 MCD-WS: Trafo SN Approach 1 and 2 Calculations (Fig. 10.9)	277

Part III Best Practice

13 Noise of MM Cartridges	283
13.1 Introduction	283
13.2 Comparison of Manufacturer's and Measured Data	284
13.3 Cartridge Impedance and Phase Measurement	285
13.4 Third Octave Band Measurement	286
13.5 Cartridge Equivalent Model	287
13.6 Complete Measurement Arrangement	289
13.7 Mathematical Model with Mathcad	290
13.8 Noise Model of Measurement Amp Plus MM Cartridge	292
13.9 $r_{bb'}$ Calculation	295
13.10 Noise Voltage and Current of Measurement Amp	296
13.11 SN Calculations	297
13.12 RIAA Transfer Function and Respective SNs	298
13.13 A-Filter Transfer Function and Respective SNs	299
13.14 Measurement Amp Design	300
13.15 Results	302
13.16 Influence of the Cartridge Loading Capacitor	304
13.17 Influence of the Gain Setting Resistor and of Temperature	304
13.18 Summary	305
14 Noise of MM Cartridges: Mathcad Worksheets	307
14.1 MCD-WS: Noise in MM Cartridges: Chap. 13 Calculations	308
14.2 MCD-WS: Noise in MM Cartridges: $r_{bb'}$ Calculation	317
15 Noise of Solid-State MC Phono-Amps	319
15.1 Introduction	319
15.2 Benchmarks and Related MC Phono-Amp Problems	320
15.3 Mathematical Rules to Calculate Any Kind of SN by Simple Means	321
15.4 S-Filter	324
15.5 Calculation Results of a Variety of MC Phono-Amp Design Solutions	327
15.6 The Transformer Solution	327
15.7 Equivalent Circuit	327
15.8 Trafo Plus BUVO MM Phono-Amp	329

15.9	Wiring Between Turntable and Phono-Amp	332
15.10	The Solid-State Approach	333
15.11	Selection of the Phono-Amp Input BJTs	333
15.12	Calculation and Measurement Results of Various i/p Devices ..	333
15.13	Circuit of the BUVO Solid-State MC Phono-Amp	336
15.14	Test Circuit for the i/p Capacitance	336
15.15	Power Supply	337
15.16	Sound	337
15.17	Frequency Response Defining Components	340
15.18	Additional Measurement Results	341
15.19	Graphs of o/p Noise Voltage Densities	343
16	Noise of Solid-State MC Phono-Amps: Mathcad Worksheets	345
16.1	MCD-WS: Various SNs of Resistors	346
16.2	MCD-WS: SNs of Various Transfer Functions (RIAA, A-Weighting, S-Filter)	347
16.3	MCD-WS: Change of Input Load of the Linn Linto	348
16.4	MCD-WS: SN Evaluation of the DOSE MC Pre-Pre-Amp	352
16.5	MCD-WS: SN Evaluation of the BUVO MM Phono-Amp+DOSE MC ppa	357
16.6	MCD-WS: SN Evaluation of the BUVO MC Trafo-Coupled Phono-Amp	359
16.7	MCD-WS: SN Evaluation of the BUVO MC Solid-State Phono-Amp	361
16.8	MCD-WS: SN Evaluation of a BFW16A MC Solid-State Phono-Amp	365
17	Noise of Triode Driven Phono-Amps	367
17.1	Introduction	367
17.2	Power Supply Unit	369
17.3	Requirements for Test Gain-Stages	372
17.4	Circuits of the Test Gain-Stages	373
17.5	Test Gain-Stage Calculation and Measurement Results	379
17.6	The Test Gain-Stages as Active Parts of Phono-Amps: Theory	381
	17.6.1 The Zwicky Approach	381
	17.6.2 Calculation Approach	385
	17.6.3 Open Questions	389
17.7	The Test Gain-Stages as Active Parts of Phono-Amps: Practice	391
	17.7.1 Example 2-Pham	391
	17.7.2 Example 3-Pham	397
17.8	Calculation Approach of the Example Phono-Amps	401
	17.8.1 General Remarks	401
	17.8.2 Calculation by Blocks: The 2-Pham	402
	17.8.3 Calculation by Blocks: The 3-Pham	404

17.9	Results	407
17.10	Determination of the Resistor Current Noise Index of the Used Resistors	409
17.11	How Much g_m Do We Really Need?	410
17.12	Summary	415
18	Noise of Triode Driven Phono-Amps: Mathcad Worksheets	419
18.1	MCD-WS: CCA_{bb} Based Evaluation of the Real Triode Constants of an E88CC/6922 Example Double-Triode	420
18.2	MCD-WS: RIAA Networks for the 2-Pham and 3-Pham Topologies	425
18.3	MCD-WS: Zwicky Matrix: SN Calculations of a Theoretical 2-Pham, Based on the μ -Follower Test Gain-Stages and Data Sheet Figures	428
18.4	MCD-WS: Zwicky Matrix: SN Calculations of a Theoretical 3-Pham, Based on the μ -Follower Test Gain-Stages and Data Sheet Figures	432
18.5	MCD-WS: Evaluation of the Current Noise Index NI of the Gain-Stage Resistors by Application of a $CCSCF_b$ Configured Gain-Stage	436
18.6	MCD-WS: SN Calculations of the Example 2-Pham, Based on Data-Sheet Values (2-Pham-ds)	438
18.7	MCD-WS: SN Calculations of the Example 2-Pham, Based on Circuit and Triode Values Determined by the WS 18.1 Approach (2-Pham-re)	453
18.8	MCD-WS: SN Calculations of the Example 3-Pham, Based on Data-Sheet Values (3-Pham-ds)	469
18.9	MCD-WS: SN Calculations of the Example 3-Pham, Based on Circuit and Triode Values Determined by the WS 18.1 Approach (3-pham-re)	485
18.10	MCD-WS: Calculation of the Required Maximum Mutual Conductance g_m	501
19	RIAA Networks	505
19.1	Introduction	505
19.2	Un-Balanced (ub) Solutions	506
19.3	The Fully Passive 1-Step-Solution Types A_{ub} and B_{ub}	507
19.3.1	Type A_{ub} : Ideal Case	508
19.3.2	Type B_{ub} : Ideal Case	508
19.3.3	Type $A_{ub,real}$	509
19.3.4	Type $B_{ub,real}$	511
19.3.5	The Succ-Apps Approach	512
19.4	The Fully Passive 2-Step-Solution Type AB_{ub}	515
19.5	The Active-Passive 2-Step-Solution Types C_{ub} and D_{ub}	519

19.5.1	Type C_{ub}	519
19.5.2	Type D_{ub}	520
19.6	The Fully Active 1-Step Solution Types E_{ub} , F_{ub-A} , F_{ub-B}	522
19.6.1	Type E_{ub}	523
19.6.2	Type F_{ub-A}	523
19.6.3	Type F_{ub-B}	524
19.7	Shunt Mode	524
19.7.1	Type E_{ub}	524
19.7.2	Type F_{ub-A}	525
19.7.3	Type F_{ub-B}	526
19.8	Series Mode and Fourth Time Constant T_4	526
19.8.1	Type E_{ub}	526
19.8.2	Type E_{ub} Succ-Apps Method	527
19.8.3	Type E_{ub} Specific Formulae Method	528
19.8.4	Difference Between v1.0 and v2.0	529
19.8.5	Type F_{ub-A} Succ-Apps Method	530
19.8.6	Type F_{ub-B} Succ-Apps Method	530
19.9	Balanced (b) Solutions	531
19.9.1	The Fully Passive 2-Step Solution Type (AB_b)	531
19.9.2	The Active/Passive 2-Step Solution Types C_b and D_b with Balanced In/Un-Balanced Out	532
19.9.3	The Active/Passive 2-Step Solution Types C_b and D_b with Balanced In/Balanced Out	533
20	RIAA Networks: Mathcad Worksheets	535
20.1	MCD-WS: 1-Step Passive Type A_{ub} Solution in an Ideal Environment	536
20.2	MCD-WS: 1-Step Passive Type B_{ub} Solution in an Ideal Environment	538
20.3	MCD-WS: 1-Step Passive Type A_{ub} Solution in a Real Environment	540
20.4	MCD-WS: 1-Step Passive Type B_{ub} Solution in a Real Environment	542
20.5	MCD-WS: 2-Step Active-Passive Type C_{ub} Solution	544
20.6	MCD-WS: 2-Step Active-Passive Type D_{ub} Solution	546
20.7	MCD-WS: Fully Active Type E_{ub} Succ-Apps Solution for MC Phono-Amps	548
20.8	MCD-WS: Fully Active Type E_{ub} Succ-Apps Solution for MM Phono-Amps	550
20.9	MCD-WS: Fully Active Type E_{ub} Formulae Solution for MC Phono-Amps	552
20.10	MCD-WS: Derivation of Proportional Factors to Calculate Type E_{ub} RIAA Networks	555

Part IV Noise and Hum Measurement System

21	System Overview	559
21.1	Introduction	559
21.2	Noise Measurement System Overview	559
21.3	The Measurement Confusion	565
21.4	Derivation of the Difference Between ARM and RMS Meter Reading	570
21.5	Summary	571
22	Measurement Amps, Noise Generators and FFT	
	Noise Measurements	573
22.1	Introduction	573
22.2	Measurement Amps	573
22.3	Noise Generators and FFT Noise Measurements	579
22.4	Camouflages by FFT Diagrams	583
22.5	The Customer FFT Confusion	586
22.6	Tables for SN Guessings via FFT Diagrams	590
23	Measurement Filters and Networks	591
23.1	Introduction	591
23.2	Basic Filter Equipment	591
23.3	RIAA and Anti-RIAA Transfer Performing Networks	597
23.4	The Equivalent Noise Bandwidth ENB	602
23.5	The Creation of a Second Filter Bank	604
23.6	The Final WYCIWYM Approach	607
23.7	The Silly A-weighting Application	609
23.8	The Dolby ARM Approach	612
24	The Hum Figure of Linear Amps	617
24.1	Introduction	617
24.2	Thorough Information is Necessary	618
24.3	Standardizing Information	620
24.4	Demonstrating the Usefulness of the Hum Figure	621
24.5	First HF Evaluation Approach: F-A	622
24.6	Second HF Evaluation Approach: FFT-A	627
24.7	Summary	628
25	The Hum Figure of Phono-Amps	631
25.1	Introduction	631
25.2	Details of the Phono-Amp HF Measurement	633
25.3	In Search of the Un-Equalized Phono-Amp's Signal-to-Noise Ratio SN_{ne}	634
25.4	In Search of the White-Noise Based Signal-to-Noise Ratio $SN_{ne,wn}$	636

25.5 HF Measurement Instrument and Results	639
25.6 Final Remarks	643
26 Mathcad Worksheets of Chaps. 22–25	645
26.1 MCD-WS: The Hum Figure of a Valve Pre-Amp	646
26.2 MCD-WS: Measurement Filters and Their Damping Figures (Fig. 23.18)	649
26.3 MCD-WS: The Hum Figure of Phono-Amps (Figs. 25.6, 25.8 and 25.9)	657

Part V The RIAA Phono-Amp Engine

27 Overview	671
27.1 Purpose and Goals	671
27.2 Development Results	672
27.3 Engine Functions	672
28 Modules 1–4	679
28.1 Module 1: Introduction and Function	679
28.2 Module 2: Introduction and Function	679
28.3 Module 2: Power-Supply Issues	680
28.4 Module 3: Introduction and Function	683
28.5 Module 3: Phono-Amp Section	687
28.6 Module 3: Relay Control	688
28.7 Module 3: Phono-Amp SN Calculation and Measurement Results	689
28.8 Module 4: Introduction and Function	690
29 Engine Performance	693
29.1 Graphs	693
29.2 Summary Tables	703
29.3 Sound	703

Part VI Appendices A1–A7

A1 Appendix 1: List of MCD Worksheets	707
A2 Appendix 2: List of Figures (Figures on Text Pages and on MCD Worksheets)	709
A3 Appendix 3: List of Tables	727
A4 Appendix 4: Abbreviations and Symbols	729
A5 Appendix 5: Physical Constants and Mathematical Sizes	735
A6 Appendix 6: Useful Literature and Web Sites	737

Index	741
--------------------	------------

The Sound of Silence

Lowest-Noise RIAA Phono-Amps: Designer's Guide

Vogel, B.

2011, XXIII, 752 p., Hardcover

ISBN: 978-3-642-19773-4