

# Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
1.1	The Origin of DC-DC Converters	2
1.1.1	Basic Considerations	2
1.1.2	Historical Notes	3
1.2	Low Power DC-DC Converter Applications	9
1.2.1	Mains-Operated	10
1.2.2	Battery-Operated	11
1.3	Monolithic DC-DC Converters: A Glimpse into the Future	14
1.3.1	CMOS Technology	15
1.3.2	The Challenges	20
1.4	Structural Outline	23
1.5	Conclusions	24
<b>2</b>	<b>Basic DC-DC Converter Theory</b>	<b>27</b>
2.1	Linear Voltage Converters	27
2.1.1	Series Converter	28
2.1.2	Shunt Converter	29
2.2	Charge-Pump DC-DC Converters	31
2.2.1	On Capacitors	32
2.2.2	Series-Parallel Step-Down Converter	34
2.2.3	Series-Parallel Step-Up Converter	38
2.3	Inductive Type DC-DC Converters	41
2.3.1	On Inductors	41
2.3.2	Inductors and Capacitors: The Combination	44
2.3.3	Reflections on Steady-State Calculation Methods	49
2.4	INTERMEZZO: The Efficiency Enhancement Factor	59
2.4.1	The Concept	59
2.4.2	Interpretations	61
2.5	Conclusions	62
<b>3</b>	<b>Inductive DC-DC Converter Topologies</b>	<b>65</b>
3.1	Step-Down Converters	65

3.1.1	Buck Converter . . . . .	66
3.1.2	Bridge Converter . . . . .	72
3.1.3	Three-Level Buck Converter . . . . .	74
3.1.4	Buck <sup>2</sup> Converter . . . . .	77
3.1.5	Watkins-Johnson Converter . . . . .	79
3.1.6	Step-Down Converter Summary . . . . .	81
3.2	Step-Up Converters . . . . .	82
3.2.1	Boost Converter . . . . .	84
3.2.2	Current-Fed Bridge Converter . . . . .	85
3.2.3	Inverse Watkins-Johnson Converter . . . . .	86
3.2.4	Step-Up Converter Summary . . . . .	88
3.3	Step-Up/Down Converters . . . . .	90
3.3.1	Buck-Boost Converter . . . . .	91
3.3.2	Non-inverting Buck-Boost Converter . . . . .	92
3.3.3	Ćuk Converter . . . . .	93
3.3.4	SEPIC Converter . . . . .	94
3.3.5	Zeta Converter . . . . .	95
3.3.6	Step-Up/Down Converter Summary . . . . .	97
3.4	Other Types of Inductive DC-DC Converters . . . . .	99
3.4.1	Galvanic Separated Converters . . . . .	99
3.4.2	Resonant DC-DC Converters . . . . .	104
3.5	Topology Variations . . . . .	107
3.5.1	Multi-phase DC-DC Converters . . . . .	107
3.5.2	Single-Inductor Multiple-Output DC-DC Converters . . . . .	115
3.5.3	On-Chip Topologies . . . . .	118
3.6	Conclusions . . . . .	121
<b>4</b>	<b>A Mathematical Model: Boost and Buck Converter . . . . .</b>	<b>123</b>
4.1	Second-Order Model: Boost and Buck Converter . . . . .	124
4.1.1	Differential Equations: Boost Converter . . . . .	124
4.1.2	Calculating the Output Voltage: Boost Converter . . . . .	126
4.1.3	Differential Equations: Buck Converter . . . . .	131
4.1.4	Calculating the Output Voltage: Buck Converter . . . . .	132
4.2	Non-ideal Converter Components Models . . . . .	135
4.2.1	Inductor . . . . .	136
4.2.2	Capacitor . . . . .	142
4.2.3	Switches . . . . .	146
4.2.4	Buffers . . . . .	152
4.2.5	Interconnect . . . . .	154
4.3	Temperature Effects . . . . .	158
4.3.1	Inductor . . . . .	159
4.3.2	Switches . . . . .	159
4.4	The Final Model Flow . . . . .	160
4.4.1	Inserting the Dynamic Losses . . . . .	161
4.4.2	Inserting the Temperature Effects . . . . .	163
4.4.3	Reflections on Design . . . . .	164
4.5	Conclusions . . . . .	167

<b>5</b>	<b>Control Systems</b>	169
5.1	Inductive Type Converter Control Strategies	170
5.1.1	Pulse Width Modulation	170
5.1.2	Pulse Frequency Modulation	175
5.1.3	Pulse Width Modulation vs. Pulse Frequency Modulation	176
5.2	Constant On/Off-Time: COOT	181
5.2.1	The COOT Concept	181
5.2.2	Single-Phase, Single-Output Implementations	184
5.2.3	Single-Phase, Two-Output SIMO Implementation	188
5.3	Semi-Constant On/Off-Time: SCOOT	193
5.3.1	The SCOOT Concept	193
5.3.2	Multi-phase Implementations	195
5.4	Feed-Forward Semi-Constant On/Off-Time: F <sup>2</sup> -SCOOT	203
5.4.1	The F <sup>2</sup> -SCOOT Concept	203
5.4.2	Single-Phase, Two-Output Implementation	205
5.5	Start-up	209
5.5.1	The Concept	210
5.5.2	Implementations	210
5.6	Conclusions	211
<b>6</b>	<b>Implementations</b>	213
6.1	Monolithic Converter Components	214
6.1.1	Inductor	214
6.1.2	Capacitor	216
6.1.3	Switches	220
6.2	On Measuring DC-DC Converters	224
6.2.1	Main Principles	224
6.2.2	Practical Example	226
6.3	Boost Converters	228
6.3.1	Bondwire, Single-Phase, Single-Output	228
6.3.2	Metal-Track, Single-Phase, Two-Output SIMO	232
6.4	Buck Converters	235
6.4.1	Bondwire, Single-Phase, Single-Output	236
6.4.2	Metal-Track, Single-Phase, Single-Output	240
6.4.3	Metal-Track, Four-Phase, Single Output	244
6.4.4	Metal-Track, Four-Phase, Two-Output SMOC	248
6.4.5	Bondwire, Single-Phase, Two-Output SMOC	250
6.5	Comparison to Other Work	254
6.5.1	Inductive Step-Up Converters	255
6.5.2	Inductive Step-Down Converters	256
6.6	Conclusions	259
<b>7</b>	<b>General Conclusions</b>	261
7.1	Conclusions	261
7.2	Remaining Challenges	263

<b>References</b> . . . . .	265
<b>Index</b> . . . . .	273

Design and Implementation of Fully-Integrated Inductive  
DC-DC Converters in Standard CMOS

Wens, M.; Steyaert, M.

2011, XLII, 282 p., Hardcover

ISBN: 978-94-007-1435-9