

# Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
1.1	The Global Development of Wireless Technologies	1
1.2	Analog and RF Circuits in Nanoscale CMOS	2
1.3	Research Objectives	2
1.4	Organization of the Book	6
	References	7
<b>2</b>	<b>General Considerations of High-/Mixed-<math>V_{DD}</math> Analog and RF Circuits and Systems</b>	<b>9</b>
2.1	Introduction	9
2.2	System Considerations	9
2.3	Device Reliability in Ultra-scaled Processes	11
2.3.1	AMR	11
2.3.2	HCI Lifetime	11
2.3.3	TDDDB	11
2.3.4	NBTI	12
2.3.5	Punchthrough	12
2.4	Extend the Voltage Capability of Thin- and Thick-Oxide Transistors	12
2.5	High-/Mixed-Voltage Building Blocks	14
2.5.1	Power Amplifier and Wideband Balun-LNA (High- $V_{DD}$ + Mixed-Transistor)	14
2.5.2	Passive Mixers (High- $V_{DD}$ + Thin-Oxide Transistor)	15
2.5.3	Differential Pair (High- $V_{DD}$ + Thin-Oxide Transistor)	17
2.5.4	Recycling Folded Cascode Operational Amplifier (High- $V_{DD}$ + Thin-Oxide Transistor)	18
2.5.5	OpAmp-Based Analog-Baseband Circuits (Mixed- $V_{DD}$ + Mixed-Transistor)	27
2.5.6	Low-Dropout-Regulator (Mixed- $V_{DD}$ + Mixed-Transistor)	29

2.5.7	Sample-and-Hold Amplifier (High- $V_{DD}$ + Mixed-Transistor) .....	31
2.5.8	Line Driver (High- $V_{DD}$ + Thin-Oxide Transistor).....	32
2.6	Summary .....	33
	References.....	33
<b>3</b>	<b>A Full-Band Mobile-TV LNA with Mixed-Voltage ESD Protection in 90-nm CMOS .....</b>	<b>35</b>
3.1	Introduction.....	35
3.2	Circuit Description.....	36
3.2.1	Full-Band Mobile-TV Tuner Architecture .....	36
3.2.2	PMOS-Based Open-Source Input Structure and Mixed-Voltage ESD Protection .....	36
3.2.3	Double Current Reuse for $g_m$ -Enhancement.....	39
3.2.4	Single-Stage Thermal-Noise Cancellation.....	41
3.3	Key Practical Design Issues.....	43
3.3.1	Package Effect on Input Impedance Match .....	43
3.3.2	Self-Startup Constant- $g_m$ Bias Circuit .....	44
3.3.3	Power-Up/Down Control with Reliability Concern .....	45
3.3.4	Mixed-Voltage ESD Protection Scheme .....	45
3.4	Simulation Results, Discussions and Benchmarks.....	46
3.5	Summary .....	51
	References.....	53
<b>4</b>	<b>A High-Voltage-Enabled Mobile-TV RF Front-End in 90-nm CMOS.....</b>	<b>55</b>
4.1	Introduction.....	55
4.2	Tuner Architecture for TV-GSM Interoperation.....	55
4.3	On/Off-Chip Circuit Design .....	58
4.3.1	Basic-Cell of the LNA .....	58
4.3.2	ESD Protection Scheme.....	64
4.3.3	Programmable $C$ - $2C$ Attenuator .....	64
4.3.4	I/Q Mixer Drivers .....	68
4.3.5	Customized External Preselect Filters .....	70
4.3.6	Feedforward Gain Roll-Off Compensation.....	72
4.4	Experimental Results, Discussions and Benchmarks.....	73
4.5	Summary .....	78
	References.....	78
<b>5</b>	<b>A Mixed-Voltage Unified Receiver Front-End for Full-Band Mobile TV in 65-nm CMOS.....</b>	<b>81</b>
5.1	Introduction.....	81
5.2	RFE Architecture and Technology Features.....	83
5.3	Wideband Balun-LNA .....	84

5.3.1	CG-CS Noise-Canceling Balun-LNA .....	84
5.3.2	Proposed Gain-Boosting Current-Balancing Balun-LNA with VGC .....	85
5.4	Current-Reuse Mixer-LPF .....	96
5.4.1	Circuit Description .....	96
5.4.2	Noise Figure .....	100
5.4.3	Simulation Results .....	101
5.5	Multi-phase LOG .....	102
5.5.1	Brief Overview .....	102
5.5.2	Open Loop Multi-phase LO Generators (Conventional and Proposed) .....	103
5.5.3	Circuit Implementation and Simulation Results .....	105
5.6	Measurement Results .....	108
5.6.1	The RFE .....	109
5.6.2	The LOG .....	113
5.6.3	Performance Comparison .....	113
5.6.4	Architecture Comparison .....	115
5.7	Summary .....	117
	References .....	118
<b>6</b>	<b>Conclusions</b> .....	121
6.1	Concluding Remarks .....	121
6.2	Recommendations for Future Research .....	122
	<b>Appendix: Open-Loop Multiphase LO Generators</b> .....	125
	<b>Index</b> .....	143

High-/Mixed-Voltage Analog and RF Circuit Techniques  
for Nanoscale CMOS

Mak, P.-I.; Martins, R.P.

2012, XVIII, 146 p., Hardcover

ISBN: 978-1-4419-9538-4