

Contents

1	Differential Structures	1
1.1	Mathematical Analysis for Synthesis of Differential Amplifiers	1
1.1.1	First Mathematical Principle (PR 1.1)	1
1.1.2	Second Mathematical Principle (PR 1.2)	2
1.1.3	Third Mathematical Principle (PR 1.3)	2
1.1.4	Fourth Mathematical Principle (PR 1.4)	2
1.1.5	Fifth Mathematical Principle (PR 1.5)	3
1.1.6	Sixth Mathematical Principle (PR 1.6)	3
1.1.7	Seventh Mathematical Principle (PR 1.7)	3
1.1.8	Different Mathematical Principle for Differential Amplifiers (PR 1.D)	3
1.2	Analysis and Design of Differential Structures	4
1.2.1	Differential Structures Based on the First Mathematical Principle (PR 1.1)	8
1.2.2	Differential Structures Based on the Second Mathematical Principle (PR 1.2)	23
1.2.3	Differential Structures Based on the Third Mathematical Principle (PR 1.3)	34
1.2.4	Differential Structures Based on the Fourth Mathematical Principle (PR 1.4)	59
1.2.5	Differential Structures Based on the Fifth Mathematical Principle (PR 1.5)	61
1.2.6	Differential Structures Based on the Sixth Mathematical Principle (PR 1.6)	62
1.2.7	Differential Structures Based on the Seventh Mathematical Principle (PR 1.7)	69
1.2.8	Differential Structures Based on Different Mathematical Principle (PR 1.D)	80
1.3	Conclusions	85
	References	85

2	Voltage and Current Multiplier Circuits	89
2.1	Mathematical Analysis for Synthesis of Multipliers	89
2.1.1	Mathematical Analysis of Voltage Multiplier Circuits	90
2.1.2	Mathematical Analysis of Current Multiplier Circuits	92
2.2	Analysis and Design of Multiplier Circuits	93
2.2.1	Design of Voltage Multiplier Circuits	93
2.2.2	Design of Current Multiplier Circuits	164
2.3	Conclusion	181
	References.....	182
3	Squaring Circuits	185
3.1	Mathematical Analysis for Synthesis of Squaring Circuits	185
3.1.1	Mathematical Analysis of Voltage Squaring Circuits	185
3.1.2	Mathematical Analysis of Current Squaring Circuits	186
3.2	Analysis and Design of Squaring Circuits.....	188
3.2.1	Design of Voltage Squaring Circuits	188
3.2.2	Design of Current Squaring Circuits	224
3.3	Conclusions	246
	References.....	246
4	Square-Root Circuits	249
4.1	Mathematical Analysis for Synthesis of Square-Root Circuits	249
4.1.1	First Mathematical Principle (PR 4.1).....	249
4.1.2	Second Mathematical Principle (PR 4.2)	249
4.1.3	Third Mathematical Principle (PR 4.3).....	250
4.1.4	Fourth Mathematical Principle (PR 4.4).....	250
4.1.5	Different Mathematical Principle (PR 4.D)	250
4.2	Analysis and Design of Square-Root Circuits.....	250
4.2.1	Square-Root Circuits Based on the First Mathematical Principle (PR 4.1)	250
4.2.2	Square-Root Circuits Based on the Second Mathematical Principle (PR 4.2)	252
4.2.3	Square-Root Circuits Based on the Third Mathematical Principle (PR 4.3)	257
4.2.4	Square-Root Circuits Based on the Fourth Mathematical Principle (PR 4.4)	260
4.2.5	Square-Root Circuits Based on Different Mathematical Principles (PR 4.D).....	262
4.3	Conclusions	264
	References.....	264

5 Exponential Circuits	267
5.1 Mathematical Analysis for Synthesis of Exponential Circuits	267
5.1.1 First Mathematical Principle (PR 5.1)	267
5.1.2 Second Mathematical Principle (PR 5.2)	268
5.1.3 Third Mathematical Principle (PR 5.3)	269
5.1.4 Fourth Mathematical Principle (PR 5.4)	270
5.1.5 Fifth Mathematical Principle (PR 5.5)	271
5.1.6 Sixth Mathematical Principle (PR 5.6)	273
5.1.7 Seventh Mathematical Principle (PR 5.7)	274
5.1.8 Eighth Mathematical Principle (PR 5.8)	277
5.1.9 Ninth Mathematical Principle (PR 5.9)	278
5.2 Analysis and Design of Exponential Circuits	280
5.2.1 Exponential Circuits Based on the First Mathematical Principle (PR 5.1)	280
5.2.2 Exponential Circuits Based on the Second Mathematical Principle (PR 5.2)	295
5.2.3 Exponential Circuits Based on the Third Mathematical Principle (PR 5.3)	297
5.2.4 Exponential Circuits Based on the Fourth Mathematical Principle (PR 5.4)	299
5.2.5 Exponential Circuits Based on the Fifth Mathematical Principle (PR 5.5)	300
5.2.6 Exponential Circuits Based on the Sixth Mathematical Principle (PR 5.6)	301
5.2.7 Exponential Circuits Based on the Seventh Mathematical Principle (PR 5.7)	302
5.2.8 Exponential Circuits Based on the Eighth Mathematical Principle (PR 5.8)	303
5.2.9 Exponential Circuits Based on the Ninth Mathematical Principle (PR 5.9)	304
5.3 Conclusions	306
References	306
6 Euclidean Distance Circuits	309
6.1 Mathematical Analysis for Synthesis of Euclidean Distance Circuits	309
6.1.1 Euclidean Distance of Voltage Input Vectors	309
6.1.2 Euclidean Distance of Current Input Vectors	310
6.2 Analysis and Design of Euclidean Distance Circuits	311
6.2.1 Euclidean Distance Circuits for Voltage Input Vectors	311
6.2.2 Euclidean Distance Circuits for Current Input Vectors	312
6.3 Conclusions	322
References	322

7 Active Resistor Circuits	323
7.1 Mathematical Analysis for Synthesis of Active Resistor Circuits	323
7.1.1 First Mathematical Principle (PR 7.1)	323
7.1.2 Second Mathematical Principle (PR 7.2)	323
7.1.3 Third Mathematical Principle (PR 7.3)	324
7.1.4 Fourth Mathematical Principle (PR 7.4)	324
7.1.5 Fifth Mathematical Principle (PR 7.5)	324
7.1.6 Different Mathematical Principles (PR 7.D)	324
7.2 Analysis and Design of Active Resistor Circuits	324
7.2.1 Active Resistor Circuits Based on the First Mathematical Principle (PR 7.1)	324
7.2.2 Active Resistor Circuits Based on the Second Mathematical Principle (PR 7.2)	341
7.2.3 Active Resistor Circuits Based on the Third Mathematical Principle (PR 7.3)	346
7.2.4 Active Resistor Circuits Based on the Fourth Mathematical Principle (PR 7.4)	349
7.2.5 Active Resistor Circuits Based on the Fifth Mathematical Principle (PR 7.5)	352
7.2.6 Active Resistor Circuits Based on Different Mathematical Principles (PR 7.D)	356
7.3 Conclusions	360
References	360
8 Multifunctional Structures	363
8.1 Mathematical Analysis for Synthesis of Multifunctional Structures	363
8.1.1 First Mathematical Principle (PR 8.1)	363
8.1.2 Second Mathematical Principle (PR 8.2)	371
8.1.3 Third Mathematical Principle (PR 8.3)	374
8.1.4 Fourth Mathematical Principle (PR 8.4)	374
8.2 Analysis and Design of Multifunctional Structures	385
8.2.1 Multifunctional Structures Based on the First Mathematical Principle	385
8.2.2 Multifunctional Structures Based on the Second Mathematical Principle	409
8.2.3 Multifunctional Structures Based on the Third Mathematical Principle	412
8.2.4 Multifunctional Structures Based on the Fourth Mathematical Principle	415
8.3 Conclusions	427
References	427

Contents	xv
Appendix 1	431
Appendix 2	437
Index	441

Synthesis of Computational Structures for Analog
Signal Processing

Popa, C.R.

2012, XV, 449 p., Hardcover

ISBN: 978-1-4614-0402-6