

Contents

1	Introduction	1
1.1	Problems in Integration of Analog Filters	2
1.2	Filter Design Approaches	4
1.2.1	LC Filters	4
1.2.2	Active RC Filters	5
1.2.3	Active R and Partially Active R Filters	6
1.2.4	SC Filters	6
1.2.5	OTA-C (G_m -C) Filters	8
1.2.6	MOSFET-C Filters	8
1.2.7	Log-Domain Filters	9
1.2.8	Current-Mode Filters	10
	References	10
2	Active RC Filters Using Opamps	13
2.1	Amplifiers Using Opamps	13
2.2	Integrators Using Opamps	21
2.3	First-Order Filters Using Opamps	27
2.3.1	Low-Pass Filters	27
2.3.2	First-Order All-Pass Filters	29
2.4	Sallen–Key Active RC Low-Pass Filter	29
2.4.1	Effect of Finite Gain of the Opamp	32
2.4.2	Effect of Finite Bandwidth of the Opamp	33
2.4.3	Active Compensation of Sallen–Key Filter with $K = 1$	35
2.4.4	Sensitivity Analysis	36
2.5	Second-Order Filters Based on Multiple Feedback	42
2.5.1	Friend’s Biquad	42
2.5.2	Multiple Feedback-Type Low-Pass Filter Due to Friend	46
2.5.3	Active Filters Using Single Fully Differential Amplifier	53

2.6	Biquads Using Two Opamps	55
2.6.1	GIC-Based Biquads	55
2.6.2	Two-Amplifier Biquads Derived from Single-Amplifier Biquads	58
2.7	Biquads Using More Than Two Opamps	60
2.7.1	KHN Biquad	60
2.7.2	Tow–Thomas Biquad	63
2.7.3	Akerberg–Mossberg Biquad	66
2.7.4	Scaling for Optimal Dynamic Range	67
2.7.5	Variants of Tow–Thomas and KHN Biquads	68
2.7.6	Tarmy–Ghausi–Moschytz Three Opamp Biquad and Its Variations	74
2.8	Second-Order Active Filters Using Amplifier Pole and One Capacitor	76
2.8.1	Using Single Capacitor	76
2.8.2	Second-Order Filters Using Only Resistors and Amplifier Poles	81
2.9	Active Filters Based on RLC Ladder Filters	88
2.9.1	Component Simulation Technique	89
2.9.2	FDNR-Based Filters	92
2.9.3	Active RC Ladder Filters Based on Operational Simulation	93
2.9.4	Operational Simulation of High-Pass Filters: Yoshihoro’s Technique	100
2.9.5	Operational Simulation of General-Parameter Ladder Filters	104
2.10	Multiloop Feedback-Based Active RC Filters	106
2.10.1	FLF (Follow-the-Leader Feedback)	106
2.10.2	PRB (Primary Resonator Block) Structure	109
2.10.3	SCF (Shifted Companion Form) Structure	109
2.10.4	Multiloop Feedback (MLF) Structure	110
2.10.5	IFLF (Inverse Follow-the-Leader Feedback) Structure	110
2.10.6	MSF (Minimum Sensitivity Feedback) Structure	110
2.11	Noise in Active RC Filters	112
2.12	Distortion in Active RC Filters	122
2.13	Problems	126
	References	142
3	OTA-C Filters	147
3.1	OTA-C Integrators	148
3.2	First-Order OTA-C Filters	150
3.2.1	First-Order OTA-C Filters Using OTAs with Single-Current Output	150

3.2.2	First-Order Filters Using OTAs with Current Input and Current Output	152
3.3	Voltage-Mode Second-Order OTA-C Filters	154
3.4	Current-Mode Second-Order OTA-C Filters	166
3.5	OTA-C Filters Using First-Order All-Pass Sections	189
3.5.1	OTA-C Filters Derived from Tarmy–Ghausi Active RC Filter	189
3.5.2	Second-Order All-Pass OTA-C Filter Realization Derived from Mitra–Hirano and Gray–Markel Structures	195
3.6	High-Order OTA-C Filters	197
3.6.1	Inductance Simulation Using OTAs	197
3.6.2	Voltage-Mode OTA-C Filters Derived from RLC Ladder Filters Using Component Simulation	198
3.6.3	Table-Based Linear Transformation Type OTA-C Filters Based on Ladder Filters	202
3.6.4	Current-Mode OTA-C Filters Based on RLC Ladder Filters	209
3.7	Multiple-Feedback-Type OTA-C Filters	216
3.8	Analytical Synthesis-Based OTA-C Filters	219
3.9	Effect of OTA Nonidealities	223
3.10	OTA-C Oscillators	227
3.11	Derivation of Voltage-Mode OTA-C Filters from Active RC Filters and Current-Mode OTA-C Filters from Voltage-Mode OTA-C Filters	232
3.12	Distortion in OTA-C Filters	235
3.13	Noise Analysis of OTA-C Biquads	239
3.14	Problems	245
	References	246
4	Switched Capacitor Filters	251
4.1	Basic Concept of Switched-Capacitor Resistor	251
4.2	Analysis of SC Filters	254
4.2.1	Laker’s z -Domain Equivalent Circuit Method	254
4.3	First-Order SC Circuits	257
4.4	Stray-Insensitive SC Biquads	262
4.4.1	Fliescher–Laker SC Biquad	262
4.4.2	Design Procedure	264
4.4.3	Capacitor Spread Evaluation	265
4.4.4	Sensitivity Evaluation	267
4.5	Multiplexed Single-Amplifier SC Filters	268
4.5.1	Parasitic Compensated SC Biquads	268
4.5.2	Multiplexed Single Opamp High-Order SC Filters	270

4.6	Improved SC Biquads	272
4.6.1	Multiplexing of Capacitors	272
4.6.2	Split-Integrating Capacitor Technique	273
4.6.3	Nagaraj's SC Filters with Low Capacitor Spread	276
4.6.4	T-Cell Integrator-Based Biquads	278
4.7	Optimal Design of SC Biquads	279
4.8	SC Ladder Filters Based on Component Simulation and Operational Simulation	287
4.8.1	SC Realization of L, C, and R Elements	288
4.8.2	SC Low-Pass and Band-Pass Filters Derived Using Operational Simulation of LC Ladder Filters	291
4.8.3	SC High-Pass Filters Derived Using Operational Simulation of LC Ladder Filters	296
4.9	High-Frequency SC Filters	298
4.9.1	SC Filters Using Double Sampling Scheme	302
4.9.2	SC Filters Based on POG (Precise Opamp Gain)	304
4.9.3	SC N-Path Filters	306
4.10	High-Frequency SC Ladder Filters	325
4.11	SC FIR Filters	331
4.12	Compensation of Finite Gain and Offset Voltage of SC Integrators and Amplifiers	337
4.12.1	Offset and Finite Gain Compensation in Integrators	337
4.12.2	Compensation of Opamp Offset and Finite Gain in SC Amplifiers	342
4.13	Distortion in SC Filters	346
4.14	Low-Voltage SC Filter Design Techniques	349
4.14.1	Switched-Opamp Technique-Based SC Filters	351
4.14.2	Clock Boosting Technique	355
4.14.3	Local Switch Bootstrapping	355
4.14.4	Reset-Opamp Technique	359
4.14.5	BIOC (Biased Inverting Opamp Configuration) Based SC Filters	360
4.15	Noise in SC Filters	365
4.16	Effect of Finite Bandwidth of Opamp on the Performance of SC Filters	374
4.16.1	Effect of Opamp Bandwidth on SC Filters Using Opamps	374
4.16.2	Effect of Opamp Bandwidth on SC Filters Using OTAs	378
4.17	Charge Injection in MOS Switches	381

4.18	SC Sigma-Delta Modulators	382
4.18.1	First-Order and Second-Order Modulators	382
4.18.2	High-Order Sigma-Delta Modulators	387
4.18.3	Practical Considerations in the Design of Sigma-Delta Modulators	403
4.18.4	Band-Pass Sigma-Delta Modulators	411
4.19	Problems	424
	References	432
5	Practical Designs of VLSI Analog Filters	439
5.1	Integrated Resistors and Capacitors	439
5.2	Active RC Filter Designs for Wireless Applications	440
5.3	Active RC Filters for ADSL	462
5.4	Active RC Filters for Software Radio	465
5.5	Active RC Filters for Other Applications	466
5.6	G_m -C Filters for Wireless Applications	478
5.7	G_m -C Filters for Optical Receivers	515
5.8	G_m -C Filters for Software Radio	515
5.9	G_m -C Filters for EEG Application	522
5.10	G_m -C Filters for HDD	523
5.11	G_m -C Filters for Power Supply Applications	529
5.12	G_m -C Filters for Other Applications	532
5.13	G_m -C Filter Tuning Techniques	571
5.14	SC Filters Using Comparators	578
5.15	Sigma-Delta Modulators	582
5.16	LC Filters	591
5.17	Evaluation of CT Filters	598
5.18	Problems	600
	References	604
	Appendix A	609
	Appendix B	613
	Index	617

VLSI Analog Filters

Active RC, OTA-C, and SC

Mohan, P.V.A.

2013, XV, 618 p. 451 illus., 37 illus. in color., Hardcover

ISBN: 978-0-8176-8357-3

A product of Birkhäuser Basel