

Contents

1	Introduction	1
1.1	Electromagnetic Compatibility	1
1.2	Possible Sources of Interference in Hospitals	3
1.3	Examples of Electromagnetic Interference	5
1.3.1	Examples of EMI in Medical Equipment	5
1.3.2	Examples of EMI in Non-Medical Equipment.	6
1.4	Regulations and Standards	7
1.5	Determining EMC Specifications.	9
1.6	Origin of Electromagnetic Interference.	10
1.6.1	Additional Circumstances Affecting Interference.	15
1.7	Negative-Feedback Amplifiers	15
1.7.1	A Classification of Errors in Negative-Feedback Amplifiers	16
1.7.2	Signal-to-Error Ratio	20
1.8	Design for Electromagnetic Compatibility	21
1.9	Outline of this Book	22
	References	22
2	Decreasing the Disturbance Coupled to Amplifiers	27
2.1	Coupling of Electromagnetic Fields	28
2.1.1	Coupling Mechanisms	29
2.2	Electrical Model of the Interconnect	30
2.3	Intended Signal Transfer in Electrically-Small Interconnect	33
2.4	Intended Signal Transfer in Electrically-Large Interconnect	35
2.5	Parameters of Interconnects	39
2.6	Coupling of Interference to the Interconnect.	41
2.6.1	Plane Wave Coupling to Electrically-Short Interconnects.	43
2.6.2	Plane Wave Coupling to Large Interconnects	46
2.6.3	Design for Low Plane Wave Coupling.	47
2.7	Differential and Common-Mode Disturbances.	48
2.7.1	Decreasing the Common-Mode Disturbance	50

2.8	Shield Design	51
2.8.1	Shield Design Considerations	52
2.8.2	Surface Transimpedance	53
2.8.3	Shielded Electrically-Small Systems	54
2.8.4	Shielded Electrically-Large Systems	56
2.9	Conclusions	57
	References	58
3	Modelling of Active Devices	61
3.1	The Bipolar Junction Transistor.	62
3.1.1	Deriving the Components of the Hybrid- π Model	64
3.1.2	Secondary Effects Affecting BJT Nonlinearity	76
3.1.3	BJT Second-Order Nonlinear Behavior as Function of Frequency	80
3.1.4	Model Limitation.	82
3.2	Field-Effect Transistors	83
3.3	The Metal-Oxide-Semiconductor Field-Effect Transistor	83
3.4	FET Hybrid- π Model.	86
3.4.1	First-Order Approximations	86
3.4.2	Secondary Effects	87
3.4.3	MOSFET Model Limitations.	90
3.4.4	Modelling the Secondary Effects	90
3.5	The Junction Field-Effect Transistor	98
3.6	The Metal-Semiconductor Field-Effect Transistor	100
3.7	Conclusions	101
	References	102
4	The Cascode and Differential Amplifier Stages	105
4.1	Cascode Stages	105
4.2	Generic Cascode	106
4.2.1	BJT-BJT Cascode.	110
4.2.2	FET-BJT Cascode.	111
4.2.3	BJT-FET Cascode.	111
4.2.4	FET-FET Cascode	112
4.3	Traditional View on Differential Stages	112
4.4	New Differential Stage Model.	114
4.4.1	Design Considerations Regarding EMI.	119
4.5	Simplified Differential Stage Hybrid- π Models	128
4.5.1	Modified Hybrid- π Model of the BJT Differential Stage.	129
4.5.2	Modified Hybrid- π Model of the FET Differential Stage.	136

4.6	Reducing Differential Pair Second-Order Nonlinearity	139
4.6.1	Design Considerations	139
4.6.2	Biasing Differential Stages	140
4.6.3	Transistor Matching	145
4.7	Conclusions	145
	References	146
5	Design of EMI-Resilient Single-Stage Amplifiers	149
5.1	Error Reduction Techniques	150
5.1.1	Compensation	150
5.1.2	Error-Feedforward	151
5.1.3	Negative Feedback	151
5.1.4	Introduction to Systematic Negative-Feedback Amplifier Design	156
5.2	Systematic Negative-Feedback Amplifier Design Strategy	157
5.2.1	Amplifier Specifications	158
5.2.2	Determining the Proper Type of Feedback	159
5.2.3	Noise Performance	160
5.2.4	Distortion	162
5.2.5	Interference	170
5.2.6	Bandwidth	171
5.2.7	Bias Circuitry	172
5.3	Envelope Detection in Single-Stage Negative-Feedback Amplifiers	173
5.3.1	Frequency Dependency of the Nonlinear Behavior of a Single-Stage Negative-Feedback Amplifier	177
5.4	Design for a Specified Envelope Detection Behavior	181
5.4.1	Example: Minimal Bias Current in a Single-Stage Voltage Follower	181
5.4.2	Example: Minimal Bias Current in a Single-Stage Current Follower	184
5.5	Design Requirements for Low EMI Susceptibility in Single-Stage Amplifiers	187
5.6	Conclusions	188
	References	188
6	Design of EMI-Resilient Dual-Stage Amplifiers	191
6.1	Design Considerations for Low EMI-Susceptible Dual-Stage Negative-Feedback Amplifiers	191
6.1.1	Dual-Stage Negative-Feedback Amplifier Model	192
6.1.2	Envelope Detection in Negative-Feedback Amplifiers Using Global- and Local Feedback	194
6.1.3	Concluding Remarks About Local Feedback	197

6.2	Model of a Dual-Stage Negative-Feedback Amplifier Without Local Feedback.	198
6.2.1	Envelope Detection in Negative-Feedback Amplifiers with Global Feedback Only	199
6.2.2	Second-Order Nonlinearity Factor as a Function of Frequency.	200
6.2.3	The Effect of an Additional Stage on χ_1	201
6.2.4	Maximal Value of χ_1 of a Dual-Stage Negative-Feedback Amplifier	202
6.3	E_{s,ω_l} of a Dual-Stage Negative-Feedback Amplifier	208
6.3.1	A. Second-Order Nonlinear Dependencies of the Input Stage	208
6.3.2	B. Second-Order Nonlinear Dependencies of the Output Stage.	211
6.3.3	C. Active Part Implementation	213
6.3.4	Generally Valid Design Rules.	215
6.3.5	Differential Input Stage	216
6.4	Technology Considerations.	219
6.5	Overview of the Proposed Design Method	220
6.5.1	Disturbance and Envelope Detection in a Second-Order Amplifier	221
6.5.2	Proposed Design Procedure.	223
6.5.3	Overview of Negative-Feedback Amplifier Design	225
6.6	Design Example of a Voltage Amplifier.	228
6.7	Conclusions	231
	References	232
7	Realizations	233
7.1	AM Detection Effects in a Single-Stage Transimpedance Amplifier	233
7.2	Design of a Transimpedance Amplifier with Specified SER	238
7.2.1	Determining the Disturbing Current.	239
7.2.2	Design Approach.	240
7.2.3	Noise	241
7.2.4	Calculation of the Required Transconductance	241
7.2.5	Implementation of the BJT Transimpedance Amplifier	244
7.2.6	Measurements	248
7.2.7	Discussion	248
7.3	Multiple-Stage Transadmittance Amplifier	249
7.3.1	System Design	250
7.3.2	Specifications	251
7.3.3	Measurements of 3T MRI Induced Interference.	253
7.3.4	Magnitude of the Required Transfers	258

7.3.5	Design of the Feedback Network.	258
7.3.6	Noise Calculation and Input Stage Bias Current	259
7.3.7	Output Stage.	260
7.3.8	Linear Transfers	260
7.3.9	EMI Behavior of the Transadmittance Amplifier.	263
7.3.10	Measurements	263
7.3.11	Resolving In-Band Interference Problems.	266
7.4	Conclusions	267
	References	267
8	Conclusions and Recommendations.	269
8.1	Conclusions	269
8.2	Recommendations	272
	Reference	272
	Appendix A: Shielding.	273
	Appendix B: Single-Stage Nullor Implementation	279
	Appendix C: Derivation of Differential Stage Equations	283
	Appendix D: Differential Input and Output Stage Negative-Feedback Amplifier.	295
	Index	301

EMI-Resilient Amplifier Circuits

van der Horst, M.J.; Serdijn, W.A.; Linnenbank, A.C.

2014, XV, 307 p., Hardcover

ISBN: 978-3-319-00592-8