

Contents

1	Introduction	1
1.1	Types of Signals	1
1.2	Root-Mean-Square and Average Values of Periodic Signals	5
1.3	Power of Periodic Currents	9
1.4	Switching Elements	16
1.5	Magnetic Elements	24
1.5.1	Chokes	26
1.5.2	Transformers	27
1.6	Capacitors	30
1.7	Radio-Frequency Interference	33
1.8	Cooling of Components	35
	References	41
2	Diodes and Transistors	43
2.1	Diode as a Switch	43
2.1.1	The Temperature Characteristics	47
2.1.2	Dynamic Diode Characteristics	50
2.1.3	Schottky Diodes	54
2.1.4	The Selection of Pulse Diodes	56
2.2	Bipolar Transistor as a Switch	58
2.2.1	The Cut Off Region	59
2.2.2	The Saturation Region	67
2.2.3	Static Transfer Characteristic	72
2.2.4	Dynamic Inverter Characteristics	75
2.2.5	Nonsaturated Switch	92
2.2.6	Capacitatively Loaded Inverter	96
2.2.7	Inductively Loaded Switch	101
2.2.8	Transistor Selection	110
2.2.9	Driver Circuits	116

2.3	Power MOS Transistor as Switch	117
2.3.1	Power VDMOS Transistor	119
2.3.2	Power BiMOS Switch	121
2.3.3	Static Parameters	123
2.3.4	Safe Operation Area	138
3	Regenerative Switches	143
3.1	Unijunction Transistor	145
3.1.1	Temperature Characteristics	148
3.1.2	Programmable Unijunction Transistor	150
3.1.3	Complimentary UniJunction Transistor	154
3.1.4	Pulse Generators	156
3.1.5	Non-standard Applications	161
3.2	Thyristors	166
3.2.1	Triode Thyristor—SCR	166
3.2.2	Gate Assisted Turn-Off Thyristor	188
3.2.3	Asymmetric Thyristor	189
3.2.4	Reverse Conducting Thyristor	189
3.2.5	Gate Turn-Off Thyristor.	190
3.2.6	MOS Thyristor	191
3.2.7	Insulated Gate Control Thyristor.	192
3.2.8	Emitter Turn-Off Thyristor	196
3.2.9	Photo-thyristor	199
3.2.10	Unilateral Switch	199
3.2.11	Double Switch—SBS	200
3.2.12	Diode Thyristors.	200
3.2.13	TRIAC	203
	References.	209
4	PWM DC/DC Converters	211
4.1	Forward Converters.	213
4.1.1	Analysis of the Basic Circuit	214
4.2	Galvanically Isolated Forward Converter	240
4.3	Boost Converter	246
4.3.1	Analysis of the Basic Scheme.	246
4.3.2	Variation of the Output Voltage	252
4.3.3	Boundary Between the Continuous and the Discontinuous Mode	255
4.3.4	Discontinuous Mode	256
4.3.5	Power Losses	258

4.4	Indirect Converter	260
4.4.1	Boundary Between the Continuous and the Discontinuous Mode	263
4.4.2	Discontinuous Mode	263
4.4.3	Indirect Converter with Galvanic Separation.	267
4.5	Push–Pull (Symmetric) Converters	275
4.5.1	Analysis of Idealized Circuit in Continuous Mode	277
4.5.2	Output Characteristics	285
4.5.3	Selection of Components	288
4.5.4	DC Premagnetization of the Core	296
4.5.5	Half-Bridge Converter	297
4.5.6	Bridge Converter	298
4.5.7	Hamilton Circuit.	301
4.6	Ćuk Converters	302
4.6.1	Elimination of the Current Ripple	305
4.6.2	Ćuk Converters with Galvanic Isolation.	306
	References.	309
5	Control Modules.	311
5.1	Basic Principles and Characteristics of PWM Control Modules.	312
5.1.1	Circuit Analysis	314
5.1.2	Simple PWM	317
5.2	Voltage-Controlled PWM.	323
5.3	Current-Controlled PWM.	324
5.3.1	Compensated PWM	327
5.4	IC Control Modules	330
5.4.1	Control Module TL494	337
5.4.2	Control Module SG1524/2524/3524	341
5.4.3	Control Module TDA 1060	352
	Reference	357
6	DC/AC Converters–Inverters	359
6.1	Single-Phase Voltage Inverters	360
6.1.1	Pulse-Controlled Output Voltage.	365
6.2	Pulse-Width Modulated Inverters	368
6.2.1	Unipolar PWM.	373
6.3	Three-Phase Inverters	377
6.3.1	Overmodulation ($m_a > 1$).	383
6.3.2	Asynchronous PWM.	384

6.4	Space Vector Modulation	384
6.4.1	Space Vector Modulation—Basic Principles	384
6.4.2	Application of Space Vector Modulation Technique	387
6.4.3	Direct and Inverse Sequencing	390
6.5	Real Drive Influence	391
	References.	394
7	AC/DC Converters—Rectifiers	395
7.1	Half-Wave Single-Phase Rectifiers	396
7.2	Full-Wave Rectifiers	397
7.2.1	Commutation of Current	400
7.3	Output Filters	404
7.3.1	Capacitive Filter	404
7.3.2	L Filter	408
7.4	Voltage Doublers	410
7.5	Three-Phase Rectifiers	411
7.6	Phase Controlled Rectifiers	416
7.6.1	Full-Wave Thyristor Rectifiers	417
7.6.2	Three-Phase Thyristor Bridge Rectifiers.	424
7.7	Twelve-Pulse Rectifiers	426
7.8	Rectifiers with Circuit for Power Factor Correction.	429
7.9	Active Rectifier	432
7.9.1	Active Rectifier with Hysteresis Current Controller	433
7.10	PWM Rectifiers	436
7.10.1	Advanced Control Techniques of PWM Rectifiers.	441
7.10.2	PWM Rectifier with Current Output	445
7.10.3	PWM Rectifiers in Active Filters	450
7.10.4	Some Topologies of PWM Rectifiers.	450
7.10.5	Applications of PWM Rectifiers	452
	References.	455
8	AC/AC Converters	457
8.1	Single-Phase AC/AC Voltage Converters	457
8.1.1	Time Proportional Control	464
8.2	Three-Phase Converters	466
8.3	Frequency Converters	468
8.3.1	Direct Frequency Converters	468
8.4	Introduction to AC/AC Matrix Converters	478
8.4.1	Basic Characteristics	478
8.4.2	Bidirectional Switches	481

8.4.3	Realization of Input Filter	482
8.4.4	Current Commutation	483
8.4.5	Protection of Matrix Converter	486
8.4.6	Application of Matrix Converter	488
	References.	491
9	Resonant Converters.	493
9.1	Resonant Circuits	495
9.2	Resonant Converters of Class D	499
9.2.1	Series Resonant Converters	501
9.2.2	Parallel Resonant Converters	509
9.2.3	Series-Parallel Resonant Converter	512
9.3	Series Resonant Converters Based on GTO Thyristors.	514
9.4	Class E Resonant Converters	518
9.5	DC/DC Converters Based on Resonant Switches	521
9.5.1	ZCS Quasi-resonant Converters	523
9.5.2	ZVS Quasi-resonant Converters	531
9.5.3	Multiresonant Converters	537
9.6	ZVS Resonant DC/AC Converters	539
9.7	Soft Switching PWM DC/DC Converters.	540
9.7.1	Phase Shift Bridge Converters	541
9.7.2	Resonant Transitions PWM Converters	547
9.8	Control Circuits of Resonant Converters	551
9.8.1	Integrated Circuit Family UCx861-8	553
9.8.2	Integrated Circuits for Control of Soft Switching PWM Converters	556
10	Introduction to Multilevel Converters	559
10.1	Basic Characteristics	559
10.2	Multilevel DC/DC Converters.	563
10.2.1	Time Interval: $nT < t < nT + DT$, $n = 0, 1, 2, \dots$	565
10.2.2	Time Interval: $nT + DT < t < (n + 1)T$	565
10.3	Multilevel Inverters.	573
10.3.1	Cascaded H-Bridge Inverters	573
10.3.2	Diode-Clamped Multilevel Inverters	578
10.3.3	Flying Capacitor Multilevel Inverter	580
10.3.4	Other Multilevel Inverter Topologies.	582
10.4	Control of Multilevel Inverters	585
10.4.1	Multilevel SPWM.	586

10.4.2	Space Vector Modulation.	589
10.4.3	Space Vector Control	590
10.4.4	Selective Harmonic Elimination	591
	References.	592
	Bibliography	593
	Index	595

Power Electronics

Converters and Regulators

Dokić, B.L.; Blanuša, B.

2015, XVIII, 598 p. 496 illus., 22 illus. in color.,

Hardcover

ISBN: 978-3-319-09401-4