
Contents

Part I The RIAA Phono-Amp Engine II

1	The Complete Engine II—Overview	3
1.1	Intro and Goals	3
1.2	General Concept	5
1.3	Basic Considerations	6
1.4	Pictures of Cases and PCBs	11
1.4.1	Cases	11
1.4.2	Printed Circuit Boards	12
1.4.3	Front and Rear of the Engine	13
1.5	Power Supplies	15
1.6	Mainboard	20
2	The Triode Driven Central Amplifier Amp3	21
2.1	General Design of Amp3	21
2.2	Gain and Noise Calculations	25
2.2.1	Gain of a DIF Followed by Two CFs	25
2.2.2	RIAA Transfer Function	26
2.2.3	Noise and SN Calculations According to Fig. 1.2	27
2.2.4	A Look into the Content of MCD-WS 3.1	29
3	Mathcad Worksheets Amp3	31
3.1	MCD-WS: The Triode Gain Stage Amp3 with RIAA Networks	32
4	The Solid-State (Op-Amp) Driven Central Amplifier Amp4	49
4.1	General Design of Amp4	49
4.2	Gain and CMRR	52
4.2.1	Gain	52
4.2.2	RIAA Transfer Function	54
4.2.3	CMRR	55
4.3	Noise Calculations	56
4.3.1	Output Noise Voltage of the Amp4 Input Gain Stage (2nd in Figs. 1.2 + 4.1) with OPs 3 & 4	58

4.3.2	Output Noise Voltage of the Amp4 Output Gain Stage (3rd in Figs. 1.2 + 4.1) with OPs 5 & 6	59
4.3.3	Total Input and Output Noise Voltages of Amp4	60
4.3.4	Noise and SN Calculations According to Fig. 1.2	60
4.3.5	A Look into the Content of MCD-WS 5.1	61
4.3.6	100 % Correlated Noise Voltages of Amp4	62
5	Mathcad Worksheets Amp4	65
5.1	MCD-WS: The Solid-State Gain Stage Amp4 with RIAA Networks	66
6	The Op-Amp and Transformer Driven Output Stage Amp5	83
6.1	General Design and Gain of Amp5	83
6.2	Power Supply	84
6.3	CMRR and Noise	86
6.3.1	CMRR	86
6.3.2	Noise and SNs	86
6.4	Additional Remarks	89
7	Mathcad Worksheets Amp5	91
7.1	MCD-WS: The Op-Amp + Transformer Driven Output Stage Amp5	92
8	The Op-Amp and Transformer Driven Input Stage Amp1	101
8.1	General Design and Gain of Amp1	101
8.2	CMRR and Noise	103
8.2.1	CMRR	103
8.2.2	Noise and SNs	104
8.3	Measurement Results.	105
8.4	Additional Remarks	108
8.4.1	DC Servo	108
8.4.2	Wild Oscillation	109
9	Mathcad Worksheets Amp1	111
9.1	MCD-WS: The Transformer + Op-Amp Driven Amp1 (Real Data)	112
9.2	MCD-WS: The Transformer + Op-Amp Driven Amp1 (Data Sheet Data)	119
10	The BJT and Op-Amp Driven Input Amp2	125
10.1	General Design and Gain of Amp2	125
10.2	CMRR	127

10.3	Noise	127
10.3.1	General Noise Aspects.	127
10.3.2	The BJT Noise Model Reloaded.	128
10.3.3	In Search of the Slope Figures ‘x’ (2SC3329) and ‘y’ (2SA1316)	132
10.3.4	The SN Calculation Process	137
10.3.5	Results	140
10.4	Additional Remarks	141
10.4.1	Input Resistors R2, R3, R4	141
10.4.2	Wild Oscillation	141
11	Mathcad Worksheets Amp2	143
11.1	MCD-WS: Evaluation of the 1/f-Noise Corner Frequency of a 2SA1316 BJT	144
11.2	MCD-WS: Evaluation of the 1/f-Noise Corner Frequency of a 2SC3329 BJT	148
11.3	MCD-WS: Amp2 SN and Gain Calculations—1/f-Noise Based Version	152
12	Engine II Performance	165
12.1	Visible and Audible Effects	165
12.1.1	Visible Effects	165
12.1.2	Audible Effects.	167
12.1.3	Test Records	168
12.1.4	Test Noise and Source Equipment.	168
12.1.5	Loudspeaker Situation and Headphones	169
12.1.6	Listening Tests	169
12.2	Measurement Results.	170
12.2.1	Noise	170
12.2.2	THD and IMD Matters, Left Channel	171
12.2.3	THD and IMD Matters, Right Channel	175
12.2.4	General THD and IMD Matters	176
12.2.5	Summary Tables and Graphs	176
12.3	Conclusions and Final Remarks	180
 Part II Knowledge Transfer		
13	Selection of Draft Designs of Other Input Stages	187
13.1	Intro	187
13.2	BJT/Op-Amps Driven MC Input Stage with Un-balanced Input and Balanced Output.	188
13.3	BJT/Op-Amps Driven MC Input Stage with Balanced Transformer Input and Balanced Output.	189

13.4	Fully Triode Driven MC/MM Pre-Amp with Transformer MC-Input and Balanced Output	191
13.5	Other Development Examples.	195
13.5.1	The Joachim Gerhard Approach	195
13.5.2	The Ovidiu Popa Approach	197
13.5.3	The Bob Cordell Approach	199
13.6	The Output Stage	200
13.7	Summary of Results	201
14	Mathcad Worksheets Draft Designs	205
14.1	MCD-WS: BJT/Op-Amp Driven MC Input Stage with Un-Balanced Input and Balanced Output	206
14.2	MCD-WS: BJT/Op-Amp Driven MC Input Stage with Balanced Transformer Input and Balanced Output	215
14.3	MCD-WS: Fully Triode Driven MC/MM Pre-Amp with Transformer MC-Input and Balanced Output.	222
15	Measurement Tools and Trimming	233
15.1	Computer Test Equipment	233
15.1.1	Intro	233
15.1.2	Signal-to-Noise Ratio	234
15.1.3	Distortion (THD)	236
15.1.4	IMD	237
15.2	The Un-Balanced to Balanced Converter UBC	239
15.2.1	Circuit.	239
15.2.2	F & P and SN Performance	239
15.2.3	THD Performance.	241
15.2.4	Output Resistances	243
15.3	RIAA Encoder and Trimming	244
15.3.1	Encoder.	244
15.3.2	Trimming Actions.	244
16	The Very Low-Noise Balanced Measurement Amp PMMA.	247
16.1	Intro	247
16.2	The Input Noise Voltage Density Question	249
16.3	The Roles of the MA Input Resistance and Input Noise Current Density	251
16.3.1	Influence of the DUT Output Resistance	251
16.3.2	The Input Noise Current Density Question.	252
16.3.3	Conclusions	254
16.4	The Final PMMA	256
16.4.1	Principal Circuit Approach.	256
16.4.2	Gain Calculations	258
16.4.3	Noise Calculations—Rule-of-Thumb SN Calculation Approach	260

16.4.4	Noise Calculations—Detailed SN Calculation Approach	261
16.5	The Complete PMMA Circuit	264
16.6	PMMA Performance	266
16.7	Practical Issues	268
16.7.1	Ground Loop Avoidance and CMRR of a Following Amp	268
16.7.2	Enclosure.	269
16.7.3	Room for Improvements	269
16.8	Recommendations	271
16.8.1	DUT Output Resistance $\leq 10 \Omega$	272
16.8.2	DUT Output Resistance $> 10 \Omega$	272
16.8.3	Summary of Recommendations.	273
16.9	Final Notes	273
17	The Galvanically Isolated Measurement Amp PFMA	275
17.1	Intro	275
17.2	Ground Loop Avoidance	275
17.3	Additional PFMA Data	277
17.4	Gain and SN Calculations	278
17.4.1	Gains	278
17.4.2	Evaluation of Noise Voltages and SNs	279
17.5	Enclosure.	281
18	Mathcad Worksheets of Measurement Tools	283
18.1	MCD-WS: The UBC.	284
18.2	MCD-WS: The PMMA	290
18.3	MCD-WS: The PFMA	302
19	A Unique MM Phono-Amp Noise Reduction Method	307
19.1	Intro	307
19.2	The Un-Balanced Noise Reduction Approach.	307
19.2.1	Basics	307
19.2.2	The M1 ELS	310
19.2.3	The M2 ELS	312
19.2.4	Results	313
19.2.5	Consequences.	313
19.3	The Balanced Noise Reduction Approach	314
19.3.1	Basics	314
19.3.2	Results	317
19.3.3	Consequences.	317
19.4	SN Calculations	317

20	Mathcad Worksheets of the MM Noise Reduction	319
20.1	MCD-WS: The Un-Balanced Version	320
20.2	MCD-WS: The Balanced Version	332
21	BJT Circuits in CE Configuration	341
21.1	Intro	341
21.2	BJT—Bipolar Junction Transistor—Basics	341
21.2.1	Equations for Low Frequency Small Signal Calculations	341
21.2.2	Circuit Parameter Based Formulae	343
21.2.3	Noise of a BJT—Frequency Independent Version	343
21.2.4	Noise of a BJT—Frequency Dependent Version	344
21.2.5	Noise of a Resistor R	345
21.2.6	Noise Factor & Noise Figure	345
21.2.7	Signal-to-Noise Ratios SN	346
21.3	Basic (b) CE _b Circuit.	346
21.3.1	Idle Gains G_b and $G_{b,rot}$	347
21.3.2	$G_b(RL) = RL$ Dependent Gain G_b	347
21.3.3	Input Resistance r_i (O/P Open).	347
21.3.4	Output Resistance $r_{o,o}$ (I/P = Open).	347
21.3.5	Output Resistances $r_{o,s}$ and $r_{o,s,rot}$ (I/P = Shorted) . . .	348
21.3.6	Operating Gains $G_{op}(R0, RL)$ and $G_{ops}(f, R0, RL)$. .	348
21.3.7	Noise—Frequency Independent Version.	349
21.3.8	Noise—Frequency Dependent Version.	351
21.4	CE Circuit CE _{cf} with Current Feedback.	351
21.4.1	Gains G_{cf} and $G_{cf,rot}$	351
21.4.2	Input Resistances r_i and $r_{i,rot}$ (O/P Open).	352
21.4.3	Output Resistances $r_{o,o}$ and $r_{o,o,rot}$ (I/P = Open)	353
21.4.4	Output Resistances $r_{o,s}$ and $r_{o,s,rot}$ (I/P = Shorted)	353
21.4.5	Operating Gains $G_{op}(R0, RL)$ and $G_{ops}(f, R0, RL)$. .	353
21.4.6	Noise and SN.	355
21.5	CE Type 2 Circuit CE _{vcf2} with Voltage Feedback and Current Feedback	356
21.5.1	Gain G_{vcf2}	356
21.5.2	Input Resistance r_i (O/P Open).	357
21.5.3	Output Resistance $r_{o,s}$ (I/P Shorted).	357
21.5.4	Output Resistance $r_{o,o}$ (I/P Open)	358
21.5.5	Other Equations	358
21.5.6	Noise and SN.	358
21.6	Correction of a TSOS-1 and TSOS-2 Gain Result.	359
21.7	The CE in Series Configuration with an Op-Amp	360
21.7.1	Basics	360
21.7.2	Noise and SN.	361

22	Differential (DIF) Amps	365
22.1	Intro	365
22.2	The DIFA-OPA	366
22.2.1	Basics	366
22.2.2	Noise Calculations Version 1	367
22.2.3	Noise Calculations Version 2	368
22.2.4	Noise Calculations Version with One Input Lead Grounded.	370
22.3	The DIFA-IC	370
22.3.1	Basics	370
22.3.2	Noise Calculations Version 1	371
22.3.3	Noise Calculations Version 2	372
23	Mathcad Worksheets of DIF Amps	375
23.1	MCD-WS: DIFA-OPA	376
23.2	MCD-WS: DIFA-IC	380
24	Old Stuff?	385
24.1	Intro	385
24.2	The BRAUN Tracking Force Measurement Instrument	387
24.3	Professional Test and Calibration Records	387
24.4	Final Note	390
Appendix 1: List of Mathcad Worksheets		391
Appendix 2: Useful Literature and Web Sites		393
Index TSOS-1		397
Index TSOS-2		403
Index TSOS-E		415

Balanced Phono-Amps

An Extension to the 'The Sound of Silence' Editions

Vogel, B.

2016, XXXVII, 424 p. 281 illus., 12 illus. in color.,

Hardcover

ISBN: 978-3-319-18523-1