

# Contents

|          |   |          |
|----------|---|----------|
| <b>1</b> | <b>Introduction.</b>  | <b>1</b> |
| 1.1      | Typical Structure and Equivalent Circuits of Power Supply Systems. Features of Circuits with Variable Operating Regime Parameters | 1        |
| 1.2      | Disadvantages of the Well-Known Calculation Methods of Regime Parameters in the Relative Form for Active Two-Poles.               | 3        |
| 1.2.1    | Volt–Ampere Characteristics of an Active Two-Pole   | 3        |
| 1.2.2    | Regime Parameters in the Relative Form.   | 4        |
| 1.2.3    | Regime Change in the Relative Form  | 7        |
| 1.2.4    | Active Two-Port with Changeable Resistance  | 9        |
| 1.2.5    | Scales of Regime Parameters for Cascaded Two-Ports  | 9        |
| 1.3      | Analysis of the Traditional Approach to Normalizing of Regime Parameters for the Voltage Linear Stabilization                     | 11       |
| 1.4      | Active Two-Port   | 14       |
| 1.4.1    | Volt Characteristics of an Active Two-Port  | 14       |
| 1.4.2    | Traditional Recalculation of the Load Currents.   | 14       |
| 1.5      | Nonlinear Characteristics.  | 17       |
| 1.5.1    | Efficiency of Two-Ports with Different Losses   | 17       |
| 1.5.2    | Characteristic Regimes of Solar Cells   | 20       |
| 1.5.3    | Quasi-resonant Voltage Converter.   | 20       |
| 1.5.4    | Power-Source and Power-Load Elements.   | 21       |
| 1.6      | Regulated Voltage Converters  | 21       |
| 1.6.1    | Voltage Regulator with a Limited Capacity Voltage Source  | 21       |
| 1.6.2    | Buck Converter  | 23       |
| 1.6.3    | Boost Converter.  | 24       |
|          | References  | 25       |

## **Part I Electrical Circuits with one Load. Projective Coordinates of a Straight Line Point**

|          |   |           |
|----------|---|-----------|
| <b>2</b> | <b>Operating Regimes of an Active Two-Pole. Display of Projective Geometry. . . . .</b>                                 | <b>29</b> |
| 2.1      | Volt–Ampere Characteristics of an Active Two-Pole. Affine and Projective Transformations of Regime Parameters . . . . . | 29        |
| 2.1.1    | Affine Transformations . . . . .  | 29        |
| 2.1.2    | Projective Transformations . . . . .  | 37        |
| 2.2      | Volt–Ampere Characteristics of an Active Two-Pole with a Variable Element . . . . .                                     | 42        |
| 2.2.1    | Thévenin Equivalent Circuit with the Variable Internal Resistance . . . . .   | 42        |
| 2.2.2    | Norton Equivalent Circuit with the Variable Internal Conductivity . . . . .   | 44        |
| 2.3      | Regime Symmetry for a Load-Power . . . . .  | 47        |
| 2.3.1    | Symmetry of Consumption and Return of Power . . . . .   | 48        |
| 2.3.2    | Symmetry Relatively to the Maximum Power Point . . . . .  | 50        |
| 2.3.3    | Two Systems of Characteristic Points . . . . .  | 52        |
|          | References . . . . .  | 54        |
| <b>3</b> | <b>Generalized Equivalent Circuit of an Active Two-Pole with a Variable Element. . . . .</b>                            | <b>55</b> |
| 3.1      | Introduction. . . . .   | 55        |
| 3.2      | Circuit with a Series Variable Resistance. . . . .  | 56        |
| 3.2.1    | Disadvantage of the Known Equivalent Circuit . . . . .  | 56        |
| 3.2.2    | Generalized Equivalent Circuit. . . . .   | 57        |
| 3.2.3    | Relative Operative Regimes. Recalculation of the Load Current . . . . .   | 60        |
| 3.2.4    | Example . . . . .   | 65        |
| 3.3      | Circuit with a Shunt Variable Conductivity . . . . .  | 70        |
| 3.3.1    | Disadvantage of the Known Equivalent Circuit . . . . .  | 70        |
| 3.3.2    | Generalized Equivalent Circuit. . . . .   | 71        |
| 3.3.3    | Relative Operative Regimes. Recalculation of the Load Current . . . . .   | 74        |
| 3.3.4    | Example . . . . .   | 78        |
| 3.4      | General Case of an Active Two-Pole with a Variable Conductivity . . . . .   | 82        |
| 3.4.1    | Known Equivalent Generator. . . . .   | 83        |
| 3.4.2    | Generalized Equivalent Circuit. . . . .   | 84        |
| 3.4.3    | Example of a Circuit. Recalculation of the Load Current . . . . .   | 87        |
| 3.5      | Stabilization of the Load Current . . . . .   | 91        |
|          | References . . . . .  | 94        |

|          |  |     |
|----------|--|-----|
| <b>4</b> | <b>Two-Port Circuits</b>   | 97  |
| 4.1      | Input-Output Conformity of Two-Ports as Affine Transformations     | 97  |
| 4.1.1    | Conformity of a Two-Port   | 97  |
| 4.1.2    | Conformity of Cascaded Two-Ports                                   | 99  |
| 4.2      | Input-Output Conformity of Two-Ports as Projective Transformations | 102 |
| 4.2.1    | Conformity of a Two-Port   | 102 |
| 4.2.2    | Versions of Conformities, Invariants, and Cross Ratios             | 106 |
| 4.2.3    | Conformity of Cascaded Two-Ports                                   | 109 |
| 4.3      | Use of Invariant Properties for the Transfer of Measuring Signals  | 116 |
| 4.3.1    | Transfer of Signals over an Unstable Two-Port                      | 116 |
| 4.3.2    | Conductivity Measurement by an Unstable Two-Port                   | 119 |
| 4.4      | Deviation from the Maximum Efficiency of a Two-Port                | 120 |
| 4.4.1    | Regime Symmetry for the Input Terminals                            | 121 |
| 4.4.2    | Regime Symmetry for the Output or Load                             | 123 |
| 4.5      | Effectiveness of Modular Connections                               | 126 |
| 4.5.1    | Complementary Knowledge About a Two-Port                           | 126 |
| 4.5.2    | Parallel Connection of Two Converters                              | 127 |
| 4.5.3    | Connection of Two-Ports with the Interaction                       | 130 |
| 4.6      | Effectiveness Indices of a Two-Port with Variable Losses           | 131 |
| 4.6.1    | Problems of Energy Indices   | 131 |
| 4.6.2    | Influence of Losses on the Load Power                              | 131 |
| 4.6.3    | Influence of Losses on the Efficiency                              | 135 |
|          | References   | 138 |
| <b>5</b> | <b>Paralleling of Limited Capacity Voltage Sources</b>             | 141 |
| 5.1      | Introduction   | 141 |
| 5.2      | Initial Relationships  | 141 |
| 5.3      | Influence of the Load Value on the Current Distribution            | 143 |
| 5.3.1    | Analysis of Paralleling Voltage Sources                            | 143 |
| 5.3.2    | Introduction of Two Concepts                                       | 145 |
| 5.3.3    | Comparison of a Loading Regime of Different Circuits               | 148 |
| 5.4      | Influence of the Equalizing Resistance on the Current Distribution | 153 |
| 5.4.1    | Analysis of Paralleling Voltage Sources                            | 153 |
| 5.4.2    | Introduction of Two Concepts                                       | 154 |
| 5.4.3    | Comparison of a Loading Regime of Different Circuits               | 157 |
|          | References   | 162 |

## **Part II Multi-port Circuits. Projective Coordinates of a Point on the Plane and Space**

|          |  |     |
|----------|--|-----|
| <b>6</b> | <b>Operating Regimes of an Active Multi-port</b> . . . . .                                     | 167 |
| 6.1      | Active Two-Port. Affine and Projective Coordinates on the Plane . . . . .                      | 167 |
| 6.1.1    | Affine Coordinates . . . . .   | 167 |
| 6.1.2    | Particular Case of a Two-Port. Introduction of the Projective Plane . . . . .                  | 173 |
| 6.1.3    | General Case of a Two-Port. Projective Coordinates . . . . .                                   | 175 |
| 6.2      | Projective Coordinates in Space . . . . .  | 183 |
| 6.2.1    | Particular Case of a Multi-port . . . . .  | 183 |
| 6.2.2    | General Case of a Multi-port. The Balanced Networks . . . . .                                  | 190 |
| 6.3      | Projective Coordinates of an Active Two-Port with Stabilization of Load Voltages . . . . .     | 198 |
|          | References . . . . .   | 205 |
| <b>7</b> | <b>Recalculation of Load Currents of Active Multi-ports</b> . . . . .                          | 207 |
| 7.1      | Recalculation of Currents for the Case of Load Changes . . . . .                               | 207 |
| 7.1.1    | Active Two-Port . . . . .  | 207 |
| 7.1.2    | Active Three-Port . . . . .  | 210 |
| 7.2      | Recalculation of Currents for the Case of Changes of Circuit Parameters . . . . .              | 213 |
| 7.2.1    | Change of Lateral Conductivity . . . . .   | 213 |
| 7.2.2    | Change of Longitudinal Conductivity . . . . .  | 219 |
| 7.3      | Comparison of Regimes and Parameters of Active Two-Ports . . . . .                             | 224 |
| 7.4      | Comparison of Regime of Active Two-Ports with Linear Stabilizations of Load Voltages . . . . . | 228 |
|          | References . . . . .   | 235 |
| <b>8</b> | <b>Passive Multi-port Circuits</b> . . . . .   | 237 |
| 8.1      | Input-Output Conformity of Four-Ports as an Affine Transformation . . . . .                    | 237 |
| 8.2      | Input-Output Conformity of Four-Ports as a Projective Transformation . . . . .                 | 244 |
| 8.2.1    | Output of a Four-Port . . . . .  | 244 |
| 8.2.2    | Input of a Four-Port . . . . .   | 246 |
| 8.2.3    | Recalculation of Currents at Load Changes . . . . .  | 251 |
| 8.2.4    | Two Cascaded Four-Port Networks . . . . .  | 252 |
| 8.2.5    | Examples of Calculation . . . . .  | 254 |
| 8.3      | Transmission of Two Signals Over Three-Wire Line . . . . .                                     | 260 |
| 8.3.1    | Transmission by Using of Cross-Ratio . . . . .   | 260 |
| 8.3.2    | Transmission by Using of Affine Ratio . . . . .  | 262 |

|  |   |            |
|--|---|------------|
| 8.4  | Input-Output Conformity of a Balanced Six-Port . . . . .  | 263        |
|  | References . . . . .  | 273        |
| <b>9</b>   | <b>Generalized Equivalent Circuit of a Multi-port . . . . .</b>                                       | <b>275</b> |
| 9.1  | Generalized Equivalent of an Active Two-Port. . . . .   | 275        |
| 9.1.1  | Disadvantages of Known Equivalent. . . . .  | 275        |
| 9.1.2  | Introduction of the Formal Variant<br>of a Generalized Equivalent. . . . .                            | 276        |
| 9.1.3  | Introduction of the Principal Variant<br>of a Generalized Equivalent Circuit . . . . .                | 279        |
| 9.2  | Generalized Equivalent of an Active Three-Port. . . . .   | 282        |
|  | References . . . . .  | 286        |
| <br><b>Part III Circuits with Non-Linear Regulation Curves</b> |   |            |
| <b>10</b>  | <b>Regulation of Load Voltages. . . . .</b>   | <b>289</b> |
| 10.1   | Base Model. Display of Conformal Geometry . . . . .   | 289        |
| 10.2   | Using of Hyperbolic Geometry Model . . . . .  | 295        |
| 10.2.1   | Case of One Load . . . . .  | 296        |
| 10.2.2   | Case of Two Loads . . . . .   | 299        |
| 10.3   | Example . . . . .   | 305        |
| 10.3.1   | Case of One Load . . . . .  | 306        |
| 10.3.2   | Case of Two Loads . . . . .   | 308        |
|  | References . . . . .  | 312        |
| <b>11</b>  | <b>Stabilization of Load Voltages . . . . .</b>   | <b>313</b> |
| 11.1   | Analysis of Load Voltage Stabilization Regimes . . . . .  | 313        |
| 11.1.1   | Case of One Load . . . . .  | 313        |
| 11.1.2   | Use of Hyperbolic Geometry . . . . .  | 315        |
| 11.1.3   | Case of Two Loads . . . . .   | 322        |
| 11.2   | Given Voltage for the First Variable Load and Voltage<br>Regulation of the Second Given Load. . . . . | 324        |
| 11.2.1   | Use of Hyperbolic Geometry . . . . .  | 328        |
| 11.2.2   | Regime Change for the First Given<br>Load Resistance. . . . .   | 330        |
| 11.2.3   | Example . . . . .   | 333        |
|  | References . . . . .  | 334        |
| <b>12</b>  | <b>Pulse-Width Modulation Regulators . . . . .</b>  | <b>337</b> |
| 12.1   | Introduction. . . . .   | 337        |
| 12.2   | Regulation Characteristic of Boost Converter. . . . .   | 337        |
| 12.3   | Regulation Characteristic of Buck–Boost Converter . . . . .   | 348        |
| 12.3.1   | Buck–Boost Converter with an Idealized Choke. . . . .   | 348        |
| 12.3.2   | Buck–Boost Converter with Losses of Choke . . . . .   | 354        |
|  | References . . . . .  | 357        |

## **Part IV    Circuits with Non-Linear Load Characteristics**

|   |     |
|---|-----|
| <b>13    Power-Source and Power-Load Elements</b> . . . . .   | 361 |
| 13.1    Introduction. . . . .   | 361 |
| 13.2    Two-Valued Regime of a Regulated Converter.<br>The Concept of a Power-Source and Power-Load Element . . . .   | 361 |
| 13.3    Influence of Voltage Source Parameters and Power-Load<br>Element onto a Power Supply Regime . . . . .   | 363 |
| 13.3.1    Ideal Voltage Source . . . . .  | 363 |
| 13.3.2    Voltage of a Power Supply with Limited Capacity . . . .   | 364 |
| 13.3.3    Internal Resistance of a Voltage Source . . . . .   | 370 |
| 13.3.4    Power of a Power-Load Element . . . . .   | 372 |
| 13.4    Power-Load Element with Losses. . . . .   | 374 |
| 13.4.1    Series Loss Resistance . . . . .  | 374 |
| 13.4.2    Two-Port Loss Circuit. . . . .  | 375 |
| 13.5    Power Supply Line with Losses. . . . .  | 381 |
| References . . . . .  | 388 |
| <b>14    Quasi-resonant Voltage Converter with Self-limitation<br/>        of Load Current. Similarity of Load Characteristics<br/>        of Some Electronic Devices</b> . . . . . | 389 |
| 14.1    Load Curve of an Active Two-Pole with Self-limitation<br>of the Current . . . . .   | 389 |
| 14.2    Equivalent Generator of an Active Two-Pole<br>with Self-limitation of Current . . . . .   | 392 |
| 14.3    Deviation from the Maximum Load Power Point . . . . .   | 396 |
| 14.4    Symmetrical Load Characteristic for the Full Area of the Load<br>Voltage Variation. . . . .   | 400 |
| 14.5    Asymmetrical Load Characteristics. . . . .  | 401 |
| 14.6    Linearly Hyperbolic Approximation of a Solar Cell<br>Characteristic. . . . .  | 405 |
| 14.6.1    Approximation Problem . . . . .   | 405 |
| 14.6.2    Formal Linearly Hyperbolic Approximation. . . . .   | 405 |
| References . . . . .  | 410 |
| <b>Conclusions</b> . . . . .  | 413 |
| <b>Index</b> . . . . .  | 415 |

Analysis of Electrical Circuits with Variable Load Regime  
Parameters

Projective Geometry Method

Penin, A.

2016, XXI, 417 p. 269 illus. in color., Hardcover

ISBN: 978-3-319-28450-7