

Contents

1	The Electrical Circuit and Its Components	1
1.1	Introduction	1
1.2	Electrical Components	3
1.2.1	Electrical Symbols	5
1.2.2	Resistor	6
1.2.3	Capacitor	7
1.2.4	Inductor	8
1.2.5	Generators	11
1.2.6	Controlled Generators	12
1.3	Real Components	14
1.3.1	Real Resistors	15
1.3.2	Real Capacitors	17
1.3.3	Real Inductors	19
1.3.4	Skin Effect	20
1.4	Usage Limits for Real Electrical Components	22
	Problems	22
	References	25
2	Direct Current Circuits	27
2.1	Introduction	27
2.2	Kirchhoff's Laws	27
2.2.1	Network Geometry	28
2.3	Solution Methods for Electric Circuits	30
2.3.1	The Method of Nodes	30
2.3.2	The Method of Meshes	32
2.3.3	Example of Circuit Solution: The Wheatstone's Bridge	34
2.3.4	Nonlinear Circuits	37
2.4	Analysis of Linear Networks	38
2.4.1	Superposition Theorem	38
2.4.2	Thévenin's Theorem	39

2.4.3	Norton's theorem	42
2.4.4	Reciprocity Theorem	43
2.5	Maximum Power Transfer Theorem	46
	Problems	47
3	Uncertainty in Electrical Measurements	53
3.1	Introduction	53
3.2	Notes on Measurement Theory.	54
3.3	Uncertainty	56
3.3.1	Type A Evaluation of Standard Uncertainty.	58
3.3.2	Type B Evaluation of Standard Uncertainty.	59
3.4	Combined Uncertainty	59
3.4.1	Combined Uncertainty for Monomial Functions	62
3.5	Expanded Uncertainty and Coverage Factor.	63
3.6	Compatibility of Different Measured Values	64
3.7	Evaluating Uncertainties	66
3.8	Examples of Uncertainty Evaluation	66
3.8.1	Voltage Measurements with an Analog Voltmeter	67
3.8.2	Voltage Measurements with a Digital Multimeter	68
3.8.3	Standard Resistor	69
3.8.4	Examples of Correlated Measurements	71
	Problems	74
	References	78
4	Direct Current Electrical Measurements	79
4.1	Introduction.	79
4.2	Properties of Measuring Instruments.	80
4.3	Electrical Current Measurements	82
4.3.1	Moving Coil Ammeter	84
4.3.2	Considerations on the Motion of the Moving Coil	86
4.4	Measurement of Voltage Difference: Analog Voltmeters	90
4.4.1	Digital Voltmeters	91
4.4.2	Electrostatic Voltmeter	95
4.5	Resistance Measurements	96
4.5.1	Voltmeter–Ammeter Method	97
4.5.2	Ohmmeter	98
	Problems	102
	Reference	106
5	Alternating Current Circuits	107
5.1	Introduction.	107
5.2	Periodic and Alternating Signals	108
5.3	Alternating Current Circuits and Their Solution	109
5.3.1	Components of Alternating Current Circuits.	110
5.3.2	The Solution of Alternating Current Circuits	111

5.4	Sinusoidal Signals	113
5.4.1	Differentiation and Integration of the Sinusoidal Signal	114
5.5	Sinusoidal Function Representation by Phasors and Complex Numbers	116
5.5.1	The Symbolic Method	119
5.6	Electric Power in AC Circuits	122
5.7	Theorems for AC Linear Networks.	124
	Problems	125
	References	126
6	Alternating Current: Basic Circuits for Applications	127
6.1	Introduction.	127
6.2	Resonant Circuits	128
6.2.1	The Circuit RLC Series.	128
6.2.2	The Circuit RLC Parallel.	131
6.2.3	The Resonant Behavior.	132
6.3	Resonant Circuits with Real Components	134
6.4	Series-Parallel Transformation	135
6.5	Bridge Circuits	137
6.6	Two-Port Circuits.	140
6.6.1	Two-Port Circuit Characteristics.	140
6.6.2	The Transfer Function and Bode's Diagrams	141
6.7	The Low-Pass RC Circuit	142
6.8	The High-Pass RC Circuit.	144
6.9	RL Circuits	146
6.10	RL and RC Circuits as Differentiators and Integrators.	147
6.11	Mutual Magnetic Induction and Transformers	148
6.12	Impedance Matching.	153
6.13	Matching Networks	155
	Problems	158
	References	161
7	Measurement of Alternating Electrical Signals.	163
7.1	Introduction.	163
7.2	Characteristics of Alternating Signals	164
7.2.1	Sinusoidal Signal	166
7.2.2	Triangular Signal	166
7.2.3	Rectangular Signal	167
7.2.4	Sawtooth Signal	169
7.3	AC Coupling.	170
7.4	Analog Instruments	171
7.5	Digital Instruments.	174
7.5.1	Peak or Average Converter	175
7.5.2	Analog AC/DC Converters	175

7.5.3	Thermal AC/DC Converters.	176
7.5.4	Digital Sampling	177
7.5.5	Phase Measurements.	178
7.5.6	Impedance Measurement	178
	Problems	179
	References	180
8	The Oscilloscope	181
8.1	Introduction.	181
8.2	The Analog Oscilloscope	182
8.2.1	Synchronization	185
8.2.2	The Analog Oscilloscope: Scheme of the Instrument	185
8.2.3	Response Time	187
8.3	The Digital Oscilloscope	188
8.4	Phase Measurements.	190
8.5	A Few Practical Considerations	193
	Reference	194
9	Pulsed Circuits.	195
9.1	Introduction.	195
9.2	The Step Signal	196
9.3	High-Pass RC Circuit	197
9.3.1	Response to Voltage Step	198
9.3.2	Response to Voltage Pulse	199
9.3.3	Response to Rectangular Waveform	200
9.3.4	Response to Voltage Ramp	203
9.3.5	Response to the Exponential Signal	204
9.4	High-Pass RC Circuit as Differentiator	205
9.5	Low-Pass RC Circuit	206
9.5.1	Response to the Voltage Step	206
9.5.2	Response to Voltage Pulse	207
9.5.3	Response to Rectangular Waveform	207
9.5.4	Response to Voltage Ramp	209
9.6	Low-Pass RC Circuit as Integrator	210
9.7	RL Circuits	211
9.8	RLC Parallel Circuit: Response to Voltage Step.	212
9.9	RLC Series Circuit: Response to Voltage Step.	215
9.9.1	Exponential Pulse.	216
9.10	Compensated Voltage Divider	219
9.10.1	Compensated Attenuator—Analysis in Frequency Domain.	220
9.10.2	Compensated Attenuator—Analysis in Time Domain.	222
9.10.3	Frequency Limitation of Compensated Attenuators	227
	Problems	227

10 The Transmission Line	231
10.1 Introduction	231
10.2 Transmission Lines	232
10.2.1 Model of the Transmission Line	233
10.3 Solution of Telegrapher Equation	235
10.3.1 Lossless Line	237
10.4 The Coaxial Cable	238
10.5 Reflections on Transmission Lines	239
10.5.1 Shorted and Open Line	241
10.5.2 Multiple Reflections	242
10.6 Line Discharge	243
10.7 Lossy Transmission Line	244
10.8 Transmission Lines in Sinusoidal Steady State	246
Problems	248
References	250
 Appendix A: Laboratory Experiments	 251
 Appendix B: Skin Effect	 269
 Appendix C: Fourier Analysis	 273
 Index	 283

Electrical Measurements in the Laboratory Practice

Bartiromo, R.; De Vincenzi, M.

2016, XV, 286 p. 121 illus., Softcover

ISBN: 978-3-319-31100-5