
Contents

1	Fundamentals of Passive Circuit Analysis	1
1.1	Laplace Transform	1
1.2	Definitions of Passive Elements	1
1.3	Time-Domain Analysis of First Order Passive Circuits . . .	3
1.3.1	RC Circuits	3
1.3.2	RL Circuits	6
1.4	First Order Passive Circuit Analysis Using Natural Frequencies	12
1.5	Time-Domain Analysis of Second Order Passive Circuits	14
1.6	Transfer Function and Circuit Stability	19
2	Diode and Bipolar Transistor Circuits	33
2.1	A Brief Review of Semiconductors	33
2.2	PN Junction	36
2.3	Rectifying Diode Circuits	38
2.4	Zener Diode Circuits	42
2.5	Light Emitting Diode (LED)	42
2.6	Bipolar Transistors	43
2.7	Bipolar Transistor Circuits	45
3	MOS Transistors and CMOS Circuits	57
3.1	N-Channel MOSFET (NMOSFET)	57
3.2	P-Channel MOSFET (PMOSFET)	59
3.3	Complementary MOS (CMOS) Inverter	62
3.4	Two-Input CMOS NAND Logic Gate	63
3.5	Two-Input CMOS NOR Logic Gate	65
3.6	Complex CMOS Logic Gate Implementation	66
3.7	Rise and Fall Times	72
3.8	Rise and Fall Delays	73
4	TTL Logic and CMOS-TTL Interface	89
4.1	TTL Inverter	89
4.2	TTL Inverter with Open Collector	93
4.3	Two-Input TTL Nand Logic Gate	97
4.4	Two-Input TTL NOR Logic Gate	99
4.5	Input Current and Voltage Measurements of a Logic Gate	102

4.6	Output Current and Voltage Measurements of a Logic Gate	103
4.7	TTL-CMOS Interface with a Pull-up Resistor	104
4.8	TTL-CMOS Interface with a Bipolar Transistor	108
4.9	CMOS-TTL Interface with a Pull-Down Resistor	115
4.10	CMOS-TTL Interface with a Bipolar Transistor	118
5	Physics of Sensors	123
5.1	Thermocouple	123
5.2	Photodiode	125
5.3	Solar Cell	127
5.4	Photo-resistor	129
5.5	Piezoelectric Materials and Accelerometers	129
5.6	Hall-Effect Devices	132
6	Operational Amplifiers and Circuits	135
6.1	Operational Amplifier Properties	135
6.2	Voltage Amplifier Circuits for Sensors	135
6.3	Trans-resistance Amplifier Circuits for Sensors	144
6.4	Analog Voltage Comparator	146
6.5	Schmitt Trigger	147
6.6	Square Waveform Generator	150
7	Data Converters	157
7.1	Analog-to-Digital Converter Principles	157
7.2	Sample and Hold Principle	160
7.3	Flash Type Analog-to-Digital Converter	160
7.4	Ramp Type Analog-to-Digital Converter	162
7.5	Successive Approximation Type Analog-to-Digital Converter	165
7.6	Weighted Sum Type Digital-to-Analog Converter	169
7.7	Ladder Type Digital-to-Analog Converter	170
8	Front-End Electronics for Embedded Systems	175
8.1	Electromechanical Device Control	175
8.2	Pulse Width Modulation Circuits	178
8.3	DC Motor Control	181
8.4	Servo Control	181
8.5	Hall-Effect Sensor Control	182
8.6	Design Project 1: Designing Front-End Electronics for an Analog Microphone	183
8.7	Design Project 2: Designing Front-End Electronics for a Temperature Measurement System	185
8.8	Project 3: Designing Front-End Electronics for a Light Level Measurement System	189
8.9	Project 4: Designing Photo Detector Circuits	191
8.10	Project 5: Designing Front-End Electronics for an Optoelectronic Tachometer	194
8.11	Project 6: Designing Front-End Electronics for a Hall-Effect-Based Tachometer	196

9	Review of Combinational and Sequential Logic Circuits and Design	201
9.1	Logic Gates	202
9.2	Boolean Algebra	208
9.3	Designing Combinational Circuits Using Truth Tables	211
9.4	Combinational Logic Minimization—Karnaugh Maps	214
9.5	Basic Logic Blocks	220
9.6	Adders	229
9.7	Subtractors	240
9.8	Shifters	241
9.9	Multipliers	244
9.10	D Latch	247
9.11	Timing Methodology Using D Latches	249
9.12	D Flip-Flop	250
9.13	Timing Methodology Using D Flip-Flops	252
9.14	Timing Violations	254
9.15	Register	259
9.16	Shift Register	261
9.17	Counter	262
9.18	Moore-Type State Machine	263
9.19	Mealy-Type State Machine	268
9.20	Controller Design: Moore-Type State Machine Versus Counter-Decoder Scheme	272
9.21	A Simple Memory Block	276
9.22	A Design Example	279
	Index	295



<http://www.springer.com/978-3-319-39437-4>

Electronics for Embedded Systems

Bindal, A.

2017, XIII, 298 p. 357 illus., Hardcover

ISBN: 978-3-319-39437-4