

Contents

Part I Circuit Variables and Topology

1 Basic Concepts	3
1.1 Physical Systems, Models, Circuits	3
1.2 Components	6
1.3 Descriptive Variables	6
1.3.1 Descriptive Variables for Two-Terminal Elements	8
1.4 Electric Power and Energy	9
1.5 Kirchhoff's Laws	11
1.5.1 Loop and Kirchhoff's Voltage Law	12
1.5.2 Cut-Set and Kirchhoff's Current Law	14
1.6 Descriptive Variables for n -Terminal Elements	16
1.6.1 Descriptive Currents	16
1.6.2 Descriptive Voltages	17
1.6.3 Descriptive Variables in the Standard Choice (Associated Reference Directions)	19
1.7 Electric Power in n -Terminal Elements	19
1.8 Problems	21
Reference	22
2 Advanced Concepts	23
2.1 Basic Elements of Graph Theory	23
2.1.1 Graphs of Components and Circuits	26
2.1.2 Subgraph, Path, Loop, and Cut-Set	27
2.1.3 Tree and Cotree	29
2.2 Matrix Formulation of Kirchhoff's Laws	30
2.2.1 Fundamental Cut-Set Matrix	31
2.2.2 Fundamental Loop Matrix	34
2.2.3 Some General Concepts on Vector Spaces and Matrices	36
2.2.4 The Cut-Set and Loop Matrices and Their Associate Space Vectors	39

2.3	Tellegen's Theorem	43
2.4	Problems	44
	References	45

Part II Memoryless Multi-terminals: Descriptive Equations and Properties

3	Basic Concepts	49
3.1	Solving a Circuit: Descriptive Versus Topological Equations	49
3.2	Descriptive Equations of Some Components	51
3.2.1	Resistor	51
3.2.2	Ideal Voltage Source	52
3.2.3	Ideal Current Source	53
3.2.4	Elementary Circuits	54
3.2.5	Diode	58
3.2.6	Bipolar Junction Transistor	63
3.3	General Component Properties	64
3.3.1	Linearity	64
3.3.2	Time-Invariance	64
3.3.3	Memory	65
3.3.4	Basis	66
3.3.5	Energetic Behavior	68
3.3.6	Reciprocity	69
3.4	Thévenin and Norton Equivalent Representations of Two-Terminal Resistive Components	73
3.4.1	Thévenin Equivalent	73
3.4.2	Norton Equivalent	76
3.4.3	Comparisons Between the Two Equivalent Models	79
3.5	Series and Parallel Connections of Two-Terminals	80
3.5.1	Series Connection	80
3.5.2	Parallel Connection	82
3.5.3	Numerical Aspects	87
3.6	Resistive Voltage and Current Dividers	87
3.6.1	Resistive Voltage Divider	87
3.6.2	Resistive Current Divider	88
3.7	Problems	88
	References	92
4	Advanced Concepts	93
4.1	Potential Functions	93
4.2	Content and Cocontent for Two-Terminal Memoryless Elements	94
4.2.1	Content Function	94
4.2.2	Cocontent Function	96
4.2.3	Legendre Transformation	98

4.3 Content and Cocontent for Multiterminal Resistive Elements 99

4.4 Additivity of Potential Functions 101

4.5 Kirchoff’s Laws and Variational Principles for Potential
Functions 102

4.6 A Particular Variational Result: Resistive Circuits
that Minimize Potential Functions 107

4.7 Minimum Heat Theorem 109

References 110

Part III Memoryless Multi-ports: Descriptive Equations and Properties

5 Basic Concepts 113

5.1 Port and n -Ports 113

5.2 Descriptive Equations of Some Two-Ports 115

5.2.1 Controlled Sources 115

5.2.2 Nullor 121

5.3 Matrix-Based Descriptions for Linear, Time-Invariant, and
Memoryless Two-Ports 125

5.3.1 Resistance Matrix 126

5.3.2 Conductance Matrix 127

5.3.3 Hybrid Matrices 129

5.3.4 Transmission Matrices 130

5.3.5 Generalizations to Higher Numbers of Ports 131

5.4 Reciprocity of Two-Ports 132

5.4.1 Matrix R 132

5.4.2 Matrix H 132

5.4.3 Matrix T 133

5.4.4 Remarks and Examples 134

5.5 Symmetry of Two-Ports 136

5.5.1 Matrix R 136

5.5.2 Hybrid Matrices 137

5.5.3 Transmission Matrices 138

5.6 Directionality of Two-Ports 138

5.7 Two-Port Ideal Power Transferitors 139

5.7.1 Ideal Transformer 140

5.7.2 Gyrator 144

5.8 Connections of Two-Ports 148

5.8.1 Cascade Connection 148

5.8.2 Series-Series Connection 150

5.8.3 Parallel-Parallel Connection 151

5.8.4 Other Connections and Case Studies 151

5.9 Problems 154

References 163

6	Advanced Concepts	165
6.1	Tellegen's Theorem: A Tool to Investigate Circuit Properties	165
6.2	Passivity	166
6.3	Reciprocity	166
6.4	Circuit Biasing and Small-Signal Relations	169
6.5	Local Activity and Amplification	171
6.6	Colored Edge Theorem	174
6.7	Circuits Consisting of Two-Terminal Elements: No-Gain Theorems	178
	References	181
Part IV Analysis of Memoryless Circuits		
7	Basic Concepts	185
7.1	Nodal Analysis	185
7.1.1	Pure Nodal Analysis	185
7.1.2	Modified Nodal Analysis	189
7.1.3	Substitution Rule	190
7.2	Mesh Analysis	191
7.2.1	Pure Mesh Analysis	192
7.2.2	Modified Mesh Analysis	196
7.2.3	Substitution Rule	198
7.3	Superposition Principle	199
7.4	Substitution Principle	204
7.5	Practical Rules	205
7.5.1	Millmann's Rule	205
7.5.2	Two-Ports with $T - \Pi$ Structure	207
7.5.3	$T \rightleftharpoons \Pi$ Transformations	210
7.5.4	Lattice (Bridge) Structures	211
7.5.5	(Resistive) Ladder Structures	214
7.6	Problems	219
8	Advanced Concepts	227
8.1	From Mesh to Loop Currents: A Graph-Based Generalization	227
8.2	Tableau Method for Linear Time-Invariant Resistive Circuits	230
8.3	Superposition Theorem	232
8.4	Equivalent Representations of Memoryless Multiports	233
8.4.1	Thévenin Equivalent Representation of Memoryless Multiports	234
8.4.2	Norton Equivalent Representation of Memoryless Multiports	241
8.4.3	Hybrid Equivalent Representations of Memoryless Multiports	248
8.5	Summarizing Comments	248

Contents	xvii
8.6 Problems	250
References	253
Appendix: Synoptic Tables	255
Solutions	259
Index	271



<http://www.springer.com/978-3-319-61233-1>

Linear and Nonlinear Circuits: Basic & Advanced
Concepts

Volume 1

Parodi, M.; Storable, M.

2018, XXI, 273 p. 309 illus., 2 illus. in color., Hardcover

ISBN: 978-3-319-61233-1