

Contents

- 1 Introduction 1**
 - 1.1 Power Converters with Integrated Circuits 1
 - 1.2 Major Control Modes for Power Converters 14
 - 1.3 Load Transient Response and Load Regulation 17
 - 1.4 Efficiency 22
 - References 34

- 2 Review of the PWM Control Circuits for Power Converters 37**
 - 2.1 Voltage-Mode Control Circuit for Power Converters 37
 - 2.2 Current-Mode Control Circuit for Power Converters 45
 - 2.3 Compensation Design for Power Converters 55
 - 2.4 Experimental Results 67
 - 2.5 Summary 78
 - References 78

- 3 Designing a Dynamic Ramp with Invariant Inductor in Current-Mode Control Circuit for Buck Converter 81**
 - 3.1 Challenges for Wide Input Voltage Range 81
 - 3.2 Dynamic Slope Compensation Design 87
 - 3.3 Experimental Results 94
 - 3.4 Summary 101
 - References 101

- 4 Review of the Adaptive On-time Control Circuits for Buck Converters 103**
 - 4.1 Adaptive On-time Control Circuits for Buck Converters 103
 - 4.2 Ripple-Based Adaptive On-time Control Circuits with Virtual Inductor Current Ripple for Buck Converters 108
 - 4.3 Current-Mode Adaptive On-time Control Circuit for Buck Converters 111

4.4	Adaptive On-time Control Circuits with Adaptive Voltage Positioning Design for Voltage Regulators	117
4.5	Summary	119
	References	120
5	Adaptive On-time Control Circuit for Buck Converters	123
5.1	Increasing Light Load Efficiency with PSM Mode	123
5.2	On-time Generator Circuit of the Adaptive On-time Control Circuits for Buck Converters	128
5.3	Comparison of Quick Dynamic Response and Conventional Quick Response of the On-time Generator Circuit	133
5.4	Experimental Results	137
5.5	Summary	142
	References	143
6	Ripple-Based Constant Frequency On-time Control Circuit with Virtual Inductor Current Ripple for Buck Converters	145
6.1	Challenges for Adaptive On-time Control Circuits for Buck Converters	145
6.2	Implemented Control Circuits of the Virtual Inductor Current Ripple	148
6.3	On-time Generator Circuit of the Constant Frequency On-time Control Circuits for Buck Converters	156
6.4	Comparison of Quick Dynamic Response and Conventional Quick Response of the On-time Generator Circuit	158
6.5	Experimental Results	162
6.6	Summary	167
	References	167
7	Constant Current Ripple On-Time Control Circuit With Native Adaptive Voltage Positioning Design for Voltage Regulators	171
7.1	Challenges for Voltage Regulators	171
7.2	Native Adaptive Voltage Positioning Design for Voltage Regulators	174
7.3	On-Time Generator Circuit of the Constant Current Ripple On-Time Control Circuit for Voltage Regulators	177
7.4	Comparison of Quick Dynamic Response and Conventional Quick Response of the On-Time Generator Circuit	180
7.5	Experimental Results	183
7.6	Summary	188
	References	188

Control Techniques for Power Converters with
Integrated Circuit

Chen, W.-W.; Chen, J.-F.

2018, VI, 190 p. 170 illus., 120 illus. in color., Hardcover

ISBN: 978-981-10-7003-7