

Appendix 2.4

Table 2.10 : Summary of all Inductive Peaking Circuits

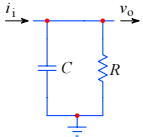
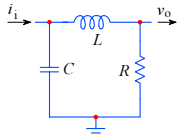
Single RC (non-peaking)	values	pole	frequency- & step-response
Reference For All Circuits 	$T = RC$ $\omega_h = 1/T$	$\sigma_{1p} = -\omega_h$	$ F(\omega) = \frac{1}{\sqrt{1 + (\omega/\omega_h)^2}}$ $\eta_b = 1$ $f(t) = 1 - e^{-t/T}$ $\tau_r = 2.2 RC \quad \eta_r = 1 \quad \delta = 0$
2-pole Series Peaking	MFA values	poles	frequency-response
	$\omega_h = 1/RC$ $L = 0.5 R^2 C$	$\sigma_{1p} = -\omega_h$ $\omega_{1p} = \pm \omega_h$	$ F(\omega) = \frac{1}{\sqrt{1 + 0.25 (\omega/\omega_H)^4}}$ $\eta_b = 1.41$
	MFED values	poles	step-response
	$T = RC$ $L = 0.33 R^2 C$	$\sigma_{1p} = -1.5/T$ $\omega_{1p} = \pm 0.866/T$	$f(t) = 1 + 2 e^{-1.5t/T} \sin(0.866 t/T + 0.524 + \pi)$ $\eta_r = 1.36 \quad \delta = 0.43 \%$

Table 2.10.1 : Summary of all Inductive Peaking Circuits (continued)

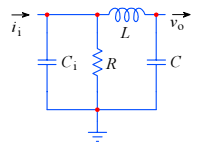
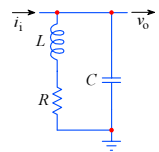
3-pole Series Peaking	MFA values	poles	frequency-response
	$\omega_h = 1/R(C + C_i)$ $L = \frac{2}{3} R^2 (C + C_i)$ $C_i = 0.25(C + C_i)$	$\sigma_{1p} = -\omega_h$ $\omega_{1p} = \pm 1.732 \omega_h$ $\sigma_{2p} = -2 \omega_h$	$ F(\omega) = \frac{1}{\sqrt{1 + 0.0156 (\omega/\omega_h)^6}}$ $\eta_b = 2$
	MFED values	poles	step-response
	$T = R(C + C_i)$ $L = 0.48 R^2 C$ $C_i = 0.17(C + C_i)$	$\sigma_{1p} = -1.839/T$ $\omega_{1p} = \pm 1.754/T$ $\sigma_{3p} = -2.322/T$	$f(t) = 1 + 1.849 e^{-1.839 t/T} \sin(1.754 t/T + 2.597 + \pi)$ $- 1.951 e^{-2.322 t/T}$ $\eta_r = 1.82 \quad \delta = 0.75 \%$
2-pole Shunt Peaking	MFA values	poles & zeros	frequency-response
	$\omega_h = 1/RC$ $L = 0.414 R^2 C$	$\sigma_{1p} = -1.208 \omega_h$ $\omega_{1p} = \pm 0.978 \omega_h$ $\sigma_z = -2.416 \omega_h$	$ F(\omega) = \sqrt{\frac{1 + 0.172 (\omega/\omega_h)}{1 - 0.172 (\omega/\omega_h) + (\omega/\omega_h)^2}}$ $\eta_b = 1.72$
	MFED values	poles & zeros	step-response
	$T = RC$ $L = 0.32 R^2 C$	$\sigma_{1p} = -1.5518/T$ $\omega_{1p} = \pm 0.5374/T$ $\sigma_z = -3.1037/T$	$f(t) = 1 + 1.617 e^{-1.5518 t/T} \sin(0.5374 t/T + 0.6668 + \pi)$ $\eta_r = 1.60 \quad \delta = 0.80 \%$

Table 2.10.1 : Summary of all Inductive Peaking Circuits (continued)

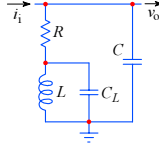
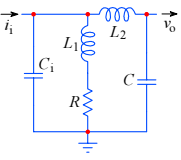
3-pole Shunt Peaking	MFA values	poles & zeros	frequency-response
	$\omega_h = 1/RC$ $L = 0.414 R^2 C$ $C_L = 0.35 C$	$\sigma_{1p} = -0.850 \omega_h$ $\omega_{1p} = \pm 1.577 \omega_h$ $\sigma_{3p} = -2.125 \omega_h$ $\sigma_z = -1.412 \omega_h$ $\omega_z = \pm 2.197 \omega_h$	$ F(\omega) = \sqrt{\frac{[1 - 0.146 (\omega/\omega_h)^2]^2 + 0.171 (\omega/\omega_h)^2}{[1 - 0.560 (\omega/\omega_h)^2]^2 + [1 - 0.146 (\omega/\omega_h)^2]^2 (\omega/\omega_h)^2}}$ $\eta_b = 1.84$
	MFED values	poles & zeros	step-response
	$T = RC$ $L = 0.33 R^2 C$ $C_L = 0.20 C$	$\sigma_{1p} = -1.839/T$ $\omega_{1p} = \pm 1.754/T$ $\sigma_{3p} = -2.322/T$ $\sigma_z = -2.500/T$ $\omega_z = \pm 2.958/T$	$f(t) = 1 + 0.8054 e^{-1.604 t/T} \sin(1.839 t/T - 0.1772 + \pi) - 1.142 e^{-2.322 t/T}$ $\eta_r = 1.73 \quad \delta = 0.37 \%$
4-pole Shunt-Series Pkg.	MFA values	poles & zeros	frequency-response
	$\omega_h = 1/R(C + C_i)$ $L_1 = 0.146 R^2(C + C_i)$ $L_2 = 0.604 R^2(C + C_i)$ $C_i = 0.586(C + C_i)$	$\sigma_{1p} = -2.4142 \omega_h$ $\omega_{1p} = \pm 1.000 \omega_h$ $\sigma_{3p} = -1.000 \omega_h$ $\omega_{3p} = \pm 2.4142 \omega_h$ $\sigma_z = -6.8284 \omega_h$	$ F(\omega) = \sqrt{\frac{0.02 (\omega/\omega_h)^2 + 1}{[0.02 (\omega/\omega_h)^4 - 0.49 (\omega/\omega_h)^2 + 1]^2 + [(\omega/\omega_h) - 0.14 (\omega/\omega_h)^3]^2}}$ $\eta_b = 2.61$
	MFED values	poles & zeros	step-response
	$T = R(C + C_i)$ $L_1 = 0.100 R^2(C + C_i)$ $L_2 = 0.463 R^2(C + C_i)$ $C_i = 0.7101(C + C_i)$	$\sigma_{1p} = -2.8962/T$ $\omega_{1p} = \pm 0.8672/T$ $\sigma_{3p} = -2.1038/T$ $\omega_{3p} = \pm 2.6574/T$ $\sigma_z = -10.0/T$	$f(t) = 1 + 4.0525 e^{-2.8976 t/T} \sin(0.8649 t/T + 0.6080 + \pi) + 1.3733 e^{-2.1024 t/T} \sin(2.6573 t/T - 1.2780 + \pi)$ $\eta_r = 2.17 \quad \delta = 0.94 \%$

Table 2.10.1 : Summary of all circuits discussed (continued)

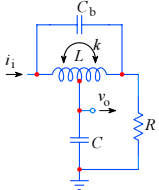
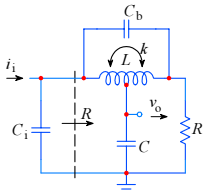
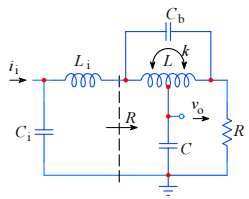
2-pole T-coil Peaking	MFA values	poles	frequency-response
	$\omega_h = 1/RC$ $L = R^2C$ $k = 0.33$ $C_b = 0.125 C$	$\sigma_{1p} = -2 \omega_h$ $\omega_{1p} = \pm 2 \omega_h$	$ F(\omega) = \frac{1}{\sqrt{1 + 15.62 \cdot 10^{-3} (\omega/\omega_h)^4}}$ $\eta_b = 2.83$
	MFED values	poles	step-response
	$T = RC$ $L = R^2C$ $k = 0.5$ $C_b = 0.083 C$	$\sigma_{1p} = -3/T$ $\omega_{1p} = \pm \sqrt{3}/T$	$f(t) = 1 + 2 e^{-3t/T} \sin(\sqrt{3} t/T + 0.5236 + \pi)$ $\eta_r = 2.72 \quad \delta = 0.43 \%$
3-pole T-coil Peaking	MFA values	poles	frequency-response
	$\omega_h = 1/R(C + C_i)$ $L = R^2C$ $k = 0$ $C_b = 0.25 C$	$\sigma_{1p} = -1.5 \omega_h$ $\omega_{1p} = \pm 2.6 \omega_h$ $\sigma_{3p} = -3 \omega_h$	$ F(\omega) = \frac{1}{\sqrt{1 + 1.367 \cdot 10^{-3} (\omega/\omega_h)^6}}$ $\eta_b = 3$
	MFED values	poles	step-response
	$T = 1/R(C + C_i)$ $L = R^2C$ $k = 0.35$ $C_b = 0.119 C$ $C_i = 0.28 (C + C_i)$	$\sigma_{1p} = -2.886/T$ $\omega_{1h} = \pm 2.7532/T$ $\sigma_{3p} = -3.6447/T$	$f(t) = 1 + 1.8489 e^{-2.886 t/T} \sin(2.7532 t/T - 0.54 + \pi)$ $- 1.9507 e^{-3.6447 t/T}$ $\eta_r = 2.78 \quad \delta = 0.75 \%$

Table 2.10.1 : Summary of all Inductive Peaking Circuits (continued)

4-pole T-coil Peaking	MFA values	poles	frequency-response
	$\omega_h = 1/R(C + C_i)$ $L = R^2 C$ $k = 0.55$ $C_b = 0.073 C$ $L_i = 1.71 R^2 C_i$ $C_i = 0.17 (C + C_i)$	$\sigma_{1p} = -4.121 \omega_h$ $\omega_{1p} = \pm 1.0707 \omega_h$ $\sigma_{3p} = -1.707 \omega_h$ $\omega_{3p} = \pm 4.121 \omega_h$	$ F(\omega) = \frac{1}{\sqrt{1 + 6.387 \cdot 10^{-6} (\omega/\omega_h)^8}}$ $\eta_b = 4.46$
	MFED values	poles	step-response
	$T = R(C + C_i)$ $L = R^2 C$ $k = 0.57$ $C_b = 0.068 C$ $L_i = 0.65 R^2 C_i$ $C_i = 0.22 (C + C_i)$	$\sigma_{1p} = -4.7317/T$ $\omega_{1p} = \pm 1.4167/T$ $\sigma_{3p} = -3.4376/T$ $\omega_{3p} = \pm 4.3419/T$	$f(t) = 1 + 5.6632 e^{-4.7317 t/T} \sin(1.4167 t/T + 0.4866 + \pi) +$ $+ 1.6484 e^{-3.4376 t/T} \sin(4.3419 t/T + 1.5389)$ $\eta_r = 3.45 \quad \delta = 0.83 \%$