

Appendix 7.2

Transfer Function Analysis of the MFB-2 circuits

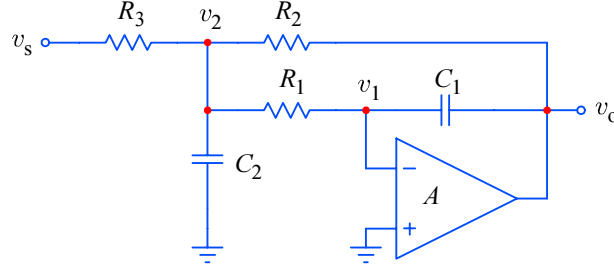


Fig. A7.2.1: The ‘Multiple Feedback’ 2-pole (MFB-2) low pass filter configurations

The derivation of the transfer function for the second-order stage, shown in [Fig. A7.2.1](#), is a little easier than for the third-order system. Using again the ideal opamp approximation, by summing the currents at v_1 we have:

$$\frac{v_2 - v_1}{R_1} = \frac{v_1 - v_o}{\frac{1}{s C_1}} \quad (\text{A7.2.1})$$

and by setting $v_1 = 0$:

$$v_2 = -v_o R_1 s C_1 \quad (\text{A7.2.2})$$

By summing the currents at v_2 :

$$\frac{v_s - v_2}{R_3} = \frac{v_2}{R_1} + \frac{v_2 - v_o}{R_2} + v_2 s C_2 \quad (\text{A7.2.3})$$

which we solve for v_s :

$$v_s = v_2 \left(\frac{R_3}{R_1} + \frac{R_3}{R_2} + 1 + R_3 s C_2 \right) - v_o \frac{R_3}{R_2} \quad (\text{A7.2.4})$$

We substitute v_2 from [Eq. A7.2.2](#):

$$v_s = -v_o R_1 s C_1 \left(\frac{R_3}{R_1} + \frac{R_3}{R_2} + 1 + R_3 s C_2 \right) - v_o \frac{R_3}{R_2} \quad (\text{A7.2.5})$$

and we can rewrite this as:

$$v_s = -v_o \left\{ \left[R_1 s C_1 \left(\frac{R_3}{R_1} + \frac{R_3}{R_2} + 1 \right) + R_1 R_3 s^2 C_1 C_2 \right] + \frac{R_3}{R_2} \right\} \quad (\text{A7.2.6})$$

Our only voltage nodes are now the input node v_s and the output node v_o , therefore we can obtain the transfer function by writing the following output to input ratio:

$$\frac{v_o}{v_s} = - \frac{1}{s^2 R_3 R_1 C_1 C_2 + R_1 s C_1 \left(\frac{R_3}{R_1} + \frac{R_3}{R_2} + 1 \right) + \frac{R_3}{R_2}} \quad (\text{A7.2.7})$$

We need the normalized canonical form in the denominator:

$$\frac{v_o}{v_s} = - \frac{\frac{1}{R_1 R_3 C_1 C_2}}{s^2 + s \left(\frac{R_3}{R_1} + \frac{R_3}{R_2} + 1 \right) \frac{1}{R_3 C_2} + \frac{R_3}{R_2} \cdot \frac{1}{R_1 R_3 C_1 C_2}} \quad (\text{A7.2.8})$$

But now we must make the numerator equal to the last term of the denominator:

$$\frac{v_o}{v_s} = - \frac{R_2}{R_3} \cdot \frac{\frac{R_3}{R_2} \cdot \frac{1}{R_1 R_3 C_1 C_2}}{s^2 + s \left(\frac{R_3}{R_1} + \frac{R_3}{R_2} + 1 \right) \frac{1}{R_3 C_2} + \frac{R_3}{R_2} \cdot \frac{1}{R_1 R_3 C_1 C_2}} \quad (\text{A7.2.9})$$

and this is our transfer function. We see that the system's DC gain A_0 is:

$$A_0 = - \frac{R_2}{R_3} \quad (\text{A7.2.10})$$

and the cut off frequency is:

$$\omega_{h2} = \sqrt{\frac{R_3}{R_2} \cdot \frac{1}{R_1 R_3 C_1 C_2}} \quad (\text{A7.2.11})$$

By looking at the denominator of the transfer function we see that the circuit is optimized and the capacitance ratio is minimized by making $R_1 = R_3 = R$. We thus obtain:

$$\frac{v_o}{v_s} = - \frac{R_2}{R} \cdot \frac{\frac{R}{R_2} \cdot \frac{1}{R^2 C_1 C_2}}{s^2 + s \left(2 + \frac{R}{R_2} \right) \frac{1}{R C_2} + \frac{R}{R_2} \cdot \frac{1}{R^2 C_1 C_2}} \quad (\text{A7.2.12})$$