Contents

1 DC Systems **1**

1.1 Basic Quantities, Basic Laws 1
1.1.1 Electric Charge 1
1.1.2 Electric Current 1
1.1.3 Voltage and Potential 2
1.1.4 Ohm's Law 2
1.1.5 Resistance and Conductance 3
1.1.6 Temperature Dependence of Resistance 3
1.1.7 Inductance 4
1.1.8 Capacitance 4
1.1.9 Ideal Voltage Source 5
1.1.10 Ideal Current Source 5
1.1.11 Kirchhoff's Law 6
1.1.11.1 Kirchhoff's First Law (Current Law) 6
1.1.11.2 Kirchhoff's Second Law (Voltage Law) 6
1.1.12 Power and Energy 7
1.1.12.1 Energy and Power in a Resistor 7
1.1.12.2 Energy in an Inductor 8
1.1.12.3 Energy in a Capacitor 9
1.1.13 Efficiency 9
1.1.14 Maximum Power Transfer 10
1.2 Basic Circuits 11
1.2.1 Real Voltage and Current Sources 11
1.2.1.1 Real Voltage Source 11
1.2.1.2 Real Current Source 12
1.2.1.3 Voltage–Current Source Conversion 13
1.2.2 Circuit Elements in Series and Parallel 13
1.2.2.1 Series Combination of Resistors 13
1.2.2.2 Parallel Combination of Resistors 13
1.2.2.3 Series Combination of Conductances 14
1.2.2.4 Parallel Combination of Conductances 14
1.2.2.5 Series Combination of Inductances 15
1.2.2.6 Parallel Combination of Inductances 15
1.2.2.7 Series Combination of Capacitances 16
1.2.2.8 Parallel Combination of Capacitances 16
1.2.3 Star–Delta Transformation 17
1.2.4 Voltage and Current Divider 18
1.2.4.1 Voltage Divider 18
1.2.4.2 Current Divider 18
1.2.4.3 Capacitive and Inductive Dividers 19
1.2.5 *RC* and *RL* Combinations 19
1.2.5.1 Series Combination of R and C Driven by a Voltage Source 21
1.2.5.2 Series Combination of R and C Driven by a Current Source 21
1.2.5.3 Parallel Combination of R and C Driven by a Current Source 22
1.2.5.4 Parallel Combination of R and C Driven by a Voltage Source 22

1.2.5.5 Series Combination of R and L Driven by a Voltage Source . . . 23
1.2.5.6 Series Combination of R and L Driven by a Current Source . . . 23
1.2.5.7 Parallel Combination of R and L Driven by a Voltage Source . . . 24
1.2.5.8 Parallel Combination of R and L Driven by a Current Source . . . 24
1.2.6 *RLC* Combinations . . . 25
1.2.6.1 Series Combination of R, L and C . . . 26
1.3 Calculation Methods for Linear Circuits . . . 29
1.3.1 Rules for Signs . . . 29
1.3.2 Circuit Calculation with Mesh and Node Analysis . . . 30
1.3.3 Superposition . . . 31
1.3.4 Mesh Analysis . . . 32
1.3.5 Node Analysis . . . 33
1.3.6 Thévenin's and Norton's Theorem . . . 33
1.3.6.1 Calculating a Load Current by Thévenin's Theorem . . . 34
1.3.6.2 Calculating a Current Within a Network . . . 36
1.4 Notation Index . . . 37
1.5 Further Reading . . . 38

2 Electric Fields 39
2.1 Electrostatic Fields . . . 39
2.1.1 Coulomb's Law . . . 39
2.1.2 Definition of Electric Field Strength . . . 40
2.1.3 Voltage and Potential . . . 41
2.1.4 Electrostatic Induction . . . 42
2.1.5 Electric Displacement . . . 43
2.1.6 Dielectrics . . . 44
2.1.7 The Coulomb Integral . . . 44
2.1.8 Gauss's Law of Electrostatics . . . 45
2.1.9 Capacitance . . . 46
2.1.10 Electrostatic Field at a Boundary . . . 47
2.1.11 Overview: Fields and Capacitances of Different Geometric Configurations . . . 48
2.1.12 Energy in an Electrostatic Field . . . 49
2.1.13 Forces in an Electrostatic Field . . . 50
2.1.13.1 Force on a Charge . . . 50
2.1.13.2 Force at the Boundary . . . 50
2.1.14 Overview: Characteristics of an Electrostatic Field . . . 52
2.1.15 Relationship between the Electrostatic Field Quantities . . . 53
2.2 Static Steady-State Current Flow . . . 53
2.2.1 Voltage and Potential . . . 53
2.2.2 Current . . . 54
2.2.3 Electric Field Strength . . . 54
2.2.4 Current Density . . . 55
2.2.5 Resistivity and Conductivity . . . 56
2.2.6 Resistance and Conductance . . . 57
2.2.7 Kirchhoff's Laws . . . 58
2.2.7.1 Kirchhoff's First Law (Current Law) . . . 58
2.2.7.2 Kirchhoff's Second Law (Mesh Law) . . . 59
2.2.8 Static Steady-State Current Flow at Boundaries . . . 60

2.2.9 Overview: Fields and Resistances of Different Geometric Configurations . . . 61
2.2.10 Power and Energy in Static Steady-State Current Flow . . . 62
2.2.11 Overview: Characteristics of Static Steady-State Current Flow . . . 63
2.2.12 Relationship Between Quantities in Static Steady-StateCurrent Flow 64
2.3 Magnetic Fields . . . 64
2.3.1 Force on a Moving Charge . . . 65
2.3.2 Definition of Magnetic Flux Density . . . 66
2.3.3 Biot–Savart's Law . . . 68
2.3.4 Magnetic Field Strength . . . 69
2.3.5 Magnetic Flux . . . 70
2.3.6 Magnetic Voltage and Ampere's Law . . . 71
2.3.7 Magnetic Resistance, Magnetic Conductance, Inductance . . . 73
2.3.8 Materials in a Magnetic Field . . . 74
2.3.8.1 Ferromagnetic Materials . . . 75
2.3.9 Magnetic Fields at Boundaries . . . 77
2.3.10 The Magnetic Circuit . . . 78
2.3.11 Magnetic Circuit with a Permanent Magnet . . . 80
2.3.12 Overview: Inductances of Different Geometric Configurations . . . 82
2.3.13 Induction . . . 83
2.3.13.1 Induction in a Moving Electrical Conductor . . . 83
2.3.13.2 Faraday's Law of Induction . . . 84
2.3.13.3 Self-Induction . . . 87
2.3.14 Mutual Induction . . . 88
2.3.15 Transformer Principle . . . 90
2.3.16 Energy in a Magnetic Field . . . 90
2.3.16.1 Energy in a Magnetic Circuit with an Air Gap . . . 91
2.3.17 Forces in a Magnetic Field . . . 92
2.3.17.1 Force on a Current-Carrying Conductor . . . 92
2.3.17.2 Force at the Boundaries . . . 93
2.3.18 Overview: Characteristics of a Magnetic Field . . . 94
2.3.19 Relationship between the Magnetic Field Quantities . . . 95
2.4 Maxwell's Equations . . . 95
2.5 Notation Index . . . 96
2.6 Further Reading . . . 98

3 AC Systems 99

3.1 Mathematical Basics of AC . . . 99
3.1.1 Sine and Cosine Functions . . . 99
3.1.1.1 Addition of Sinusoidal Waveforms . . . 100
3.1.2 Complex Numbers . . . 101
3.1.2.1 Complex Arithmetic . . . 102
3.1.2.2 Representation of Complex Numbers . . . 103
3.1.2.3 Changing Between Different Representations . . . 105
3.1.3 Complex Calculus . . . 105
3.1.3.1 Complex Addition and Subtraction . . . 105
3.1.3.2 Multiplication of Complex Numbers . . . 106
3.1.4 Overview: Complex Number Arithmetic . . . 107
3.1.5 The Complex Exponential Function . . . 107
3.1.5.1 Exponential Function with Imaginary Exponents . . . 108
3.1.5.2 Exponential Function with Complex Exponents . . . 108
3.1.6 Trigonometric Functions with Complex Arguments . . . 109
3.1.7 From Sinusoidal Waveforms to Phasors . . . 109
3.1.7.1 Complex Magnitude . . . 109

3.1.7.2 Relationship Between Sinusoidal Waveforms and Phasors . . . 110
3.1.7.3 Addition and Subtraction of Phasors . . . 111
3.2 Sinusoidal Waveforms . . . 112
3.2.1 Characteristics of Sinusoidal Waveforms . . . 113
3.2.2 Characteristics of Nonsinusoidal Waveforms . . . 115
3.3 Complex Impedance and Admittance . . . 116
3.3.1 Impedance . . . 116
3.3.2 Complex Impedance of Passive Components . . . 118
3.3.2.1 Resistor . . . 118
3.3.2.2 Inductor . . . 118
3.3.2.3 Capacitor . . . 118
3.3.3 Admittance . . . 119
3.3.4 Complex Admittance of Passive Components . . . 120
3.3.5 Overview: Complex Impedance . . . 121
3.4 Impedance of Passive Components . . . 122
3.5 Combinations of Passive Components . . . 123
3.5.1 Series Combinations . . . 123
3.5.1.1 General Case . . . 123
3.5.1.2 Resistor and Inductor in Series . . . 124
3.5.1.3 Resistor and Capacitor in Series . . . 125
3.5.1.4 Resistor, Inductor and Capacitor in Series . . . 126
3.5.2 Parallel Combinations . . . 128
3.5.2.1 General Case . . . 128
3.5.2.2 Resistor and Inductor in Parallel . . . 129
3.5.2.3 Resistor and Capacitor in Parallel . . . 130
3.5.2.4 Resistor, Inductor and Capacitor in Parallel . . . 132
3.5.3 Overview of Series and Parallel Circuits . . . 134
3.6 Network Transformations . . . 135
3.6.1 Transformation from Parallel to Series Circuits and Vice Versa . . . 135
3.6.2 Star–Delta (Wye–Delta) and Delta–Star (Delta–Wye) Transformations . . . 137
3.6.3 Circuit Duality . . . 139
3.7 Simple Networks . . . 140
3.7.1 Complex Voltage and Current Division . . . 140
3.7.2 Loaded Complex Voltage Divider . . . 142
3.7.3 Impedance Matching . . . 143
3.7.4 Voltage Divider with Defined Input and Output Resistances . . . 145
3.7.5 Phase-Shifting Circuits . . . 146
3.7.5.1 RC Phase Shifter . . . 146
3.7.5.2 Alternative Phase-Shifting Circuits . . . 148
3.7.6 AC Bridges . . . 149
3.7.6.1 Balancing Condition . . . 149
3.7.6.2 Application: Measurement Technique . . . 150
3.8 Power in AC Circuits . . . 151
3.8.1 Instantaneous Power . . . 151
3.8.1.1 Power in a Resistance . . . 151
3.8.1.2 Power in a Reactive Element . . . 151
3.8.2 Average Power . . . 152
3.8.2.1 Real Power . . . 153
3.8.2.2 Reactive Power . . . 154
3.8.2.3 Apparent Power . . . 155
3.8.3 Complex Power . . . 155
3.8.4 Overview: AC Power . . . 156

3.8.5 Reactive Current Compensation . . . 156
3.9 Three-Phase Supplies . . . 158
3.9.1 Polyphase Systems . . . 158
3.9.2 Three-Phase Systems . . . 159
3.9.2.1 Properties of the Complex Operator $\underline{a}$ . . . 160
3.9.3 Delta-Connected Generators . . . 161
3.9.4 Star-Connected Generators . . . 162
3.10 Overview: Symmetrical Three-Phase Systems . . . 164
3.10.1 Power in a Three-Phase System . . . 165
3.11 Notation Index . . . 166
3.12 Further Reading . . . 167

4 Current, Voltage and Power Measurement 169

4.1 Electrical Measuring Instruments . . . 169
4.1.1 Moving-Coil Instrument . . . 169
4.1.2 Ratiometer Moving-Coil Instrument . . . 169
4.1.3 Electrodynamic Instrument . . . 170
4.1.4 Moving-Iron Instrument . . . 171
4.1.5 Other Instruments . . . 171
4.1.6 Overview: Electrical Instruments . . . 173
4.2 Measurement of DC Current and Voltage . . . 174
4.2.1 Moving-Coil Instrument . . . 174
4.2.2 Range Extension for Current Measurements . . . 174
4.2.3 Range Extension for Voltage Measurements . . . 175
4.2.4 Overload Protection . . . 176
4.2.5 Systematic Measurement Errors in Current and Voltage Measurement . . . 176
4.3 Measurement of AC Voltage and AC Current . . . 177
4.3.1 Moving-Coil Instrument with Rectifier . . . 177
4.3.2 Moving-Iron Instruments . . . 179
4.3.3 Measurement Range Extension Using an Instrument Transformer . 179
4.3.4 RMS Measurement . . . 180
4.4 Power Measurement . . . 181
4.4.1 Power Measurement in a DC Circuit . . . 181
4.4.2 Power Measurement in an AC Circuit . . . 182
4.4.2.1 Three-Voltmeter Method . . . 183
4.4.2.2 Power Factor Measurement . . . 184
4.4.3 Power Measurement in a Multiphase System . . . 185
4.4.3.1 Measurement of the Real Power in a Multiphase System . . . 185
4.4.3.2 Measurement of the Reactive Power in a Multiphase System . . . 186
4.5 Measurement Errors . . . 187
4.5.1 Systematic and Random Errors . . . 187
4.5.2 Guaranteed Error Limits . . . 188
4.6 Overview: Symbols on Measurement Instruments . . . 188
4.7 Overview: Measurement Methods . . . 190
4.8 Notation Index . . . 190
4.9 Further Reading . . . 191

5 Networks at Variable Frequency 192

5.1 Linear Systems . . . 192
5.1.1 Transfer Function, Amplitude and Phase Response . . . 192
5.2 Filters . . . 194

5.2.1 Low-Pass Filter . . . 195
5.2.2 High-Pass Filter . . . 195
5.2.3 Bandpass Filter . . . 196
5.2.4 Stop-Band Filter . . . 197
5.2.5 All-Pass Filter . . . 197
5.3 Simple Filters . . . 197
5.3.1 Low-Pass Filter . . . 197
5.3.1.1 Rise Time . . . 198
5.3.2 Frequency Normalisation . . . 199
5.3.2.1 Approximation of the Magnitude Response . . . 200
5.3.3 High-Pass Filter . . . 200
5.3.3.1 Approximation of the Magnitude Response . . . 202
5.3.4 Higher-Order Filters . . . 202
5.3.5 Bandpass Filter . . . 204
5.3.6 Filter Realisation . . . 206
5.4 Notation Index . . . 206
5.5 Further Reading . . . 207

6 Signals and Systems 208
6.1 Signals . . . 208
6.1.1 Definitions . . . 208
6.1.2 Symmetry Properties of Signals . . . 209
6.2 Fourier Series . . . 210
6.2.1 Trigonometric Form . . . 210
6.2.1.1 Symmetry Properties . . . 211
6.2.2 Amplitude–Phase Form . . . 211
6.2.3 Exponential Form . . . 212
6.2.3.1 Symmetry Properties . . . 213
6.2.4 Overview: Fourier Series Representations . . . 213
6.2.5 Useful Integrals for the Calculation of Fourier Coefficients . . . 214
6.2.6 Useful Fourier Series . . . 215
6.2.7 Application of the Fourier Series . . . 217
6.2.7.1 Spectrum of a Rectangular Signal . . . 217
6.2.7.2 Spectrum of a Sawtooth Signal . . . 218
6.2.7.3 Spectrum of a Composite Signal . . . 219
6.3 Systems . . . 220
6.3.1 System Properties . . . 220
6.3.1.1 Linear Systems . . . 220
6.3.1.2 Causal Systems . . . 221
6.3.1.3 Time-Invariant Systems . . . 221
6.3.1.4 Stable Systems . . . 222
6.3.1.5 LTI Systems . . . 222
6.3.2 Elementary Signals . . . 222
6.3.2.1 The Step Function . . . 222
6.3.2.2 The Rectangular Pulse . . . 222
6.3.2.3 The Triangular Pulse . . . 223
6.3.2.4 The Gaussian Pulse . . . 223
6.3.2.5 The Impulse Function (Delta Function) . . . 224
6.3.3 Shifting and Scaling of Time Signals . . . 225
6.3.4 System Responses . . . 226
6.3.4.1 Impulse Response . . . 226
6.3.4.2 Step Response . . . 227
6.3.4.3 System Response to Arbitrary Input Signals . . . 228
6.3.4.4 Rules of Convolution . . . 228

6.3.4.5 Transfer Function . . . 230
6.3.4.6 System Response Calculation in the Frequency Domain 230
6.3.5 Impulse and Step Response Calculation . . . 231
6.3.5.1 Normalisation of Circuits . . . 231
6.3.5.2 Impulse and Step Response of First-Order Systems . . . 232
6.3.5.3 Impulse and Step Response of Second-Order Systems . . 234
6.3.6 Ideal Systems . . . 236
6.3.6.1 Distortion-Free Systems . . . 236
6.3.6.2 Ideal Low-Pass Filter . . . 238
6.3.6.3 Ideal Bandpass Filter . . . 240
6.4 Fourier Transforms . . . 241
6.4.1 Principle . . . 241
6.4.2 Definition . . . 242
6.4.3 Representation of the Fourier Transform . . . 243
6.4.3.1 Symmetry Properties . . . 244
6.4.4 Overview: Properties of the Fourier Transform . . . 244
6.4.5 Fourier Transforms of Elementary Signals . . . 245
6.4.5.1 Spectrum of the Delta Function . . . 245
6.4.5.2 Spectrum of the Signum and the Step Functions . . . 246
6.4.5.3 Spectrum of the Rectangular Pulse . . . 247
6.4.5.4 Spectrum of the Triangular Pulse . . . 247
6.4.5.5 Spectrum of the Gaussian Pulse . . . 248
6.4.5.6 Spectrum of Harmonic Functions . . . 249
6.4.6 Summary of Fourier Transforms . . . 250
6.5 Nonlinear Systems . . . 253
6.5.1 Definition . . . 253
6.5.2 Characterisation of Nonlinear Systems . . . 253
6.5.2.1 Characteristic Equation . . . 253
6.5.2.2 Total Harmonic Distortion . . . 254
6.5.2.3 Signal-to-Intermodulation Ratio . . . 255
6.6 Notation Index . . . 258
6.7 Further Reading . . . 259

7 Analogue Circuit Design 261

7.1 Methods of Analysis . . . 261
7.1.1 Linearisation at the Operating Point . . . 261
7.1.2 AC Equivalent Circuit . . . 262
7.1.3 Input and Output Impedance . . . 263
7.1.3.1 Determination of the Input Impedance . . . 263
7.1.3.2 Determination of the Output Impedance . . . 263
7.1.3.3 Combination of Two-Terminal Networks . . . 264
7.1.4 Two-Port Networks . . . 265
7.1.4.1 Two-Port Network Equations . . . 265
7.1.4.2 Hybrid Parameters (h-Parameters) . . . 265
7.1.4.3 Admittance Parameters (y-Parameters) . . . 266
7.1.5 Block Diagrams . . . 267
7.1.5.1 Calculation Rules for Block Diagrams . . . 268
7.1.6 Bode Plot . . . 269
7.2 Silicon and Germanium Diodes . . . 269
7.2.1 Current–Voltage Characteristic of Si and Ge Diodes . . . 270
7.2.2 Temperature Dependency of the Threshold Voltage . . . 270
7.2.3 Dynamic Resistance (Differential Resistance) . . . 271
7.3 Small-Signal Amplifier with Bipolar Transistors . . . 271
7.3.1 Transistor Characteristics . . . 272

7.3.1.1 Symbols, Voltages and Currents for Bipolar Transistors . 272
7.3.1.2 Output Characteristics 272
7.3.1.3 Transfer Characteristic 273
7.3.1.4 Input Characteristic 273
7.3.1.5 Static Current Gain β_{DC} 274
7.3.1.6 Differential Current Gain β 274
7.3.1.7 Transconductance g_m 275
7.3.1.8 Thermal Voltage Drift 275
7.3.1.9 Differential Input Resistance r_{BE} 275
7.3.1.10 Differential Output Resistance r_{CE} 275
7.3.1.11 Reverse Voltage-Transfer Ratio A_r 276
7.3.1.12 Unity Gain and Critical Frequencies 276
7.3.2 Equivalent Circuits 276
7.3.2.1 Static Equivalent Circuit 276
7.3.2.2 AC Equivalent Circuit 277
7.3.2.3 The Giacoletto Equivalent Circuit 278
7.3.3 Darlington Pair 278
7.3.3.1 Pseudo-Darlington Pair 279
7.3.4 Basic Circuits with Bipolar Transistors 280
7.3.5 Common-Emitter Circuit 280
7.3.5.1 Common-Emitter Circuit Two-Port Network Equations . 281
7.3.5.2 Common-Emitter AC Equivalent Circuit 282
7.3.5.3 Common-Emitter Circuit Input Impedance 283
7.3.5.4 Common-Emitter Circuit Output Impedance 284
7.3.5.5 Common-Emitter Circuit AC Voltage Gain 285
7.3.5.6 Operating Point Biasing 286
7.3.5.7 Operating Point Stabilisation 288
7.3.5.8 Load Line 290
7.3.5.9 Common-Emitter Circuit at High Frequencies 291
7.3.6 Common-Collector Circuit (Emitter Follower) 291
7.3.6.1 Common-Collector AC Equivalent Circuit 292
7.3.6.2 Common-Collector Circuit Input Impedance 293
7.3.6.3 Common-Collector Circuit Output Impedance 293
7.3.6.4 Common-Collector Circuit AC Current Gain 294
7.3.6.5 Common-Collector Circuit at High Frequencies 294
7.3.7 Common-Base Circuit 294
7.3.7.1 Common-Base AC Equivalent Circuit 295
7.3.7.2 Common-Base Circuit Input Impedance 295
7.3.7.3 Common-Base Circuit Output Impedance 295
7.3.7.4 Common-Base Circuit AC Voltage Gain 296
7.3.7.5 Common-Base Circuit at High Frequencies 296
7.3.8 Overview: Basic Bipolar Transistor Circuits 296
7.3.9 Bipolar Transistor Current Sources 296
7.3.10 Bipolar Transistor Differential Amplifier 298
7.3.10.1 Differential Mode Gain 300
7.3.10.2 Common-Mode Gain 301
7.3.10.3 Common-Mode Rejection Ratio 301
7.3.10.4 Differential Amplifier Input Impedance 302
7.3.10.5 Differential Amplifier Output Impedance 302
7.3.10.6 Offset Voltage of the Differential Amplifier 302
7.3.10.7 Differential Amplifier Offset Current 302
7.3.10.8 Input Offset Voltage Drift 302
7.3.10.9 Differential Amplifier Examples 303
7.3.11 Overview: Bipolar Transistor Differential Amplifiers 304

7.3.12 Current Mirror 304
7.3.12.1 Current Mirror Variations 305
7.4 Field-Effect Transistor Small-Signal Amplifiers 305
7.4.1 Transistor Characteristics and Ratings 305
7.4.1.1 Symbols, Voltages and Currents for Field-Effect Transistors 305
7.4.1.2 JFET Characteristic Curves 307
7.4.1.3 IGFET Characteristic Curves 307
7.4.1.4 Transconductance 308
7.4.1.5 Dynamic Output Resistance 309
7.4.1.6 Input Impedance 309
7.4.2 Equivalent Circuit 309
7.4.2.1 Equivalent Circuit for Low Frequencies 309
7.4.2.2 Equivalent Circuit for High Frequencies 310
7.4.2.3 Critical Frequency of Transconductance 310
7.4.3 Basic Circuits using Field-Effect Transistors 310
7.4.4 Common-Source Circuit 310
7.4.4.1 Common-Source Two-Port Parameters 311
7.4.4.2 AC Equivalent Circuit of the Common-Source Circuit . . 312
7.4.4.3 Input Impedance of the Common-Source Circuit 313
7.4.4.4 Output Impedance of the Common-Source Circuit 313
7.4.4.5 AC Voltage Gain 314
7.4.4.6 Operating-Point Biasing 314
7.4.4.7 Common-Drain Circuit, Source Follower 316
7.4.4.8 AC Equivalent Circuit of the common-drain Circuit . . . 316
7.4.4.9 Input Impedance of the Common-Drain Circuit 317
7.4.4.10 Output Impedance of the Common-Drain Circuit 317
7.4.4.11 Voltage Gain of the Common-Drain Circuit 317
7.4.4.12 Common-Drain Circuit at High Frequencies 317
7.4.5 Common-Gate Circuit 317
7.4.5.1 Input Impedance of the Common-Gate Circuit 318
7.4.5.2 Output Impedance of the Common-Gate Circuit 318
7.4.5.3 Voltage Gain of the Common-Gate Circuit 318
7.4.6 Overview: Basic Circuits using Field-Effect Transistors 318
7.4.7 FET Current Source 319
7.4.8 Differential Amplifier with Field-Effect Transistors 319
7.4.8.1 Differential Mode Gain 320
7.4.8.2 Common-Mode Gain 320
7.4.8.3 Common-Mode Rejection Ratio 321
7.4.8.4 Input Impedance 321
7.4.8.5 Output Impedance 321
7.4.9 Overview: Differential Amplifier with FETs 321
7.4.10 Controllable Resistor FETs 321
7.5 Negative Feedback 322
7.5.1 Feedback Topologies 324
7.5.2 Influence of Negative Feedback on the Input and Output Impedance 326
7.5.2.1 Input and Output Impedance of the Four Kinds of Feedback 327
7.5.3 Influence of Negative Feedback on Frequency Response 327
7.5.4 Stability of Systems with Negative Feedback 328
7.6 Operational Amplifiers 329
7.6.1 Characteristics of the Operational Amplifier 330
7.6.1.1 Output Voltage Swing 330

7.6.1.2 Offset Voltage 330
7.6.1.3 Offset Voltage Drift 331
7.6.1.4 Common-Mode Input Swing 331
7.6.1.5 Differential Mode Gain 331
7.6.1.6 Common-Mode Gain 331
7.6.1.7 Common-Mode Rejection Ratio 332
7.6.1.8 Power Supply Rejection Ratio 332
7.6.1.9 Input Impedance 332
7.6.1.10 Output Impedance 332
7.6.1.11 Input Bias Current 332
7.6.1.12 Gain–Bandwidth Product (Unity Gain Frequency) 333
7.6.1.13 Critical Frequency 333
7.6.1.14 Slew Rate of the Output Voltage 333
7.6.1.15 Equivalent Circuit of the Operational Amplifier 333
7.6.2 Frequency Compensation 334
7.6.3 Comparators 335
7.6.4 Circuits with Operational Amplifiers 335
7.6.4.1 Impedance Converter (follower) 336
7.6.4.2 Noninverting Amplifier 336
7.6.4.3 Inverting Amplifier 337
7.6.4.4 Summing Amplifier 338
7.6.4.5 Difference Amplifier 339
7.6.4.6 Instrumentation Amplifier 340
7.6.4.7 Voltage-Controlled Current Source 341
7.6.4.8 Integrator 341
7.6.4.9 Differentiator 342
7.6.4.10 AC Voltage Amplifier with Single-Rail Supply 343
7.6.4.11 Voltage Setting with Defined Slew Rate 343
7.6.4.12 Schmitt Trigger 344
7.6.4.13 Triangle- and Square-Wave Generator 345
7.6.4.14 Multivibrator 346
7.6.4.15 Sawtooth Generator 346
7.6.4.16 Pulse-Width Modulator 346
7.7 Active Filters 348
7.7.1 Low-Pass Filters 349
7.7.1.1 Theory of Low-Pass Filters 349
7.7.1.2 Low-Pass Filter Calculations 356
7.7.1.3 Low-Pass Filter Circuits 357
7.7.2 High-Pass Filters 359
7.7.2.1 Theory of High-Pass Filters 359
7.7.2.2 High-Pass Filter Circuits 359
7.7.3 Bandpass Filters 361
7.7.3.1 Second-Order Bandpass Filter 361
7.7.3.2 Second-Order Bandpass Filter Circuit 362
7.7.3.3 Fourth- and Higher-Order Bandpass Filters 362
7.7.4 Universal Filter 363
7.7.5 Switched-Capacitor Filter 363
7.8 Oscillators 364
7.8.1 RC Oscillators 365
7.8.1.1 Phase-Shift Oscillator 365
7.8.1.2 Wien Bridge Oscillator 366
7.8.2 LC Tuned Oscillators 367
7.8.2.1 Meissner Oscillator 367
7.8.2.2 Hartley Oscillator 367

7.8.2.3 Colpitts Oscillator . . . 368
7.8.3 Quartz/Crystal Oscillators . . . 368
7.8.3.1 Pierce Oscillator . . . 369
7.8.3.2 Quartz Oscillator with TTL Gates . . . 370
7.8.4 Multivibrators . . . 370
7.9 Heating and Cooling . . . 370
7.9.1 Reliability and Lifetime . . . 371
7.9.2 Temperature Calculation . . . 373
7.9.2.1 Thermal Resistance . . . 373
7.9.2.2 Thermal Capacity . . . 374
7.9.2.3 Transient Thermal Impedance . . . 375
7.10 Power Amplifiers . . . 376
7.10.1 Emitter Follower . . . 376
7.10.2 Complementary Emitter Follower in Class B Operation . . . 379
7.10.3 Complementary Emitter Follower in Class C Operation . . . 382
7.10.4 The Characteristic Curves of the Operation Classes . . . 383
7.10.5 Complementary Emitter Follower in Class AB Operation . . . 383
7.10.5.1 Biasing for Class AB Operation . . . 384
7.10.5.2 Complementary Emitter Follower with Darlington Transistors . . . 385
7.10.5.3 Current-Limiting Complementary Emitter Follower . . . 386
7.10.6 Input Signal Injection to Power Amplifiers . . . 386
7.10.6.1 Input Signal Injection using a Differential Amplifier . . . 386
7.10.6.2 Input Signal Injection Using an Op-Amp . . . 388
7.10.7 Switched-Mode Amplifiers . . . 388
7.11 Notation Index . . . 389
7.12 Further Reading . . . 390

8 Digital Electronics 392
8.1 Logic Algebra . . . 392
8.1.1 Logic Variables and Logic Gates . . . 392
8.1.1.1 Inversion . . . 392
8.1.1.2 AND Function . . . 392
8.1.1.3 OR Function . . . 393
8.1.2 Logic Functions and their Symbols . . . 393
8.1.2.1 Inverter (NOT) . . . 394
8.1.2.2 AND Gate . . . 394
8.1.2.3 OR Gate . . . 394
8.1.2.4 NAND Gate . . . 395
8.1.2.5 NOR Gate . . . 395
8.1.2.6 XOR Gate, Exclusive OR . . . 396
8.1.3 Logic Transformations . . . 396
8.1.3.1 Commutative Laws . . . 396
8.1.3.2 Associative Laws . . . 397
8.1.3.3 Distributive Laws . . . 397
8.1.3.4 Inversion Laws (DeMorgan's Rules) . . . 398
8.1.4 Overview: Logic Transformations . . . 398
8.1.5 Analysis of Logic Circuits . . . 399
8.1.6 Sum of Products and Product of Sums . . . 400
8.1.6.1 Sum of Products . . . 400
8.1.6.2 Product of Sums . . . 401
8.1.7 Systematic Reduction of a Logic Function . . . 402
8.1.7.1 Karnaugh Map . . . 402
8.1.7.2 The Quine–McCluskey Technique . . . 406

8.1.8 Synthesis of Combinational Circuits 408
8.1.8.1 Implementation Using only NAND Gates 408
8.1.8.2 Implementation Using only NOR Gates 408
8.2 Electronic Realisation of Logic Circuits 409
8.2.1 Electrical Specification 409
8.2.1.1 Voltage Levels 409
8.2.1.2 Transfer Characteristic 409
8.2.1.3 Loading 410
8.2.1.4 Noise Margin 410
8.2.1.5 Propagation Delay Time 411
8.2.1.6 Rise Times 411
8.2.1.7 Power Loss 412
8.2.1.8 Minimum Slew Rate 412
8.2.1.9 Integration 412
8.2.2 Overview: Notation in Data Sheets 412
8.2.3 TTL Family 414
8.2.3.1 TTL Devices 414
8.2.3.2 Basic TTL Gate Circuit 416
8.2.4 CMOS Family 417
8.2.5 Comparison of TTL and CMOS 418
8.2.5.1 Other Logic Families 418
8.2.6 Special Circuit Variations 420
8.2.6.1 Outputs with Open Collector 420
8.2.6.2 Wired AND/OR 420
8.2.6.3 Tri-State Outputs 422
8.2.6.4 Schmitt Trigger Inputs 422
8.3 Combinational Circuits and Sequential Logic 423
8.3.1 Dependency Notation 423
8.3.1.1 Overview: Dependency Notation 425
8.3.2 Circuit Symbols for Combinational and Sequential Logic 425
8.4 Examples of Combinational Circuits 426
8.4.1 1-to-*n* Decoder 426
8.4.2 Multiplexer and Demultiplexer 426
8.4.2.1 Overview of Circuits 428
8.5 Latches and Flip-Flops 428
8.5.1 Flip-Flop Applications 428
8.5.2 SR Flip-Flop 429
8.5.2.1 SR Flip-Flop with Clock Input 430
8.5.3 D Flip-Flop 430
8.5.4 Master–Slave Flip-Flop 431
8.5.5 JK Flip-Flop 432
8.5.6 Flip-Flop Triggering 432
8.5.7 Notation for Flip-Flop Circuit Symbols 433
8.5.8 Overview: Flip-Flops 434
8.5.9 Overview: Edge-Triggered Flip-Flops 434
8.5.10 Synthesis of Edge-Triggered Flip-Flops 436
8.5.11 Overview: Flip-Flop Circuits 438
8.6 Memory 439
8.6.1 Memory Construction 439
8.6.2 Memory Access 440
8.6.3 Static and Dynamic RAMs 441
8.6.3.1 Variations of RAM 442
8.6.4 Read-Only Memory 443
8.6.5 Programmable Logic Devices 444

8.6.5.1 Principle of Operation 444
8.6.5.2 PLD Types 445
8.6.5.3 Output Circuits 446
8.7 Registers and Shift Registers 448
8.8 Counters 449
8.8.1 Asynchronous Counters 450
8.8.1.1 Binary Counter 450
8.8.1.2 Decimal Counter 450
8.8.1.3 Down Counter 453
8.8.1.4 Up/Down Counter 454
8.8.1.5 Programmable Counter 454
8.8.2 Synchronous Counters 455
8.8.2.1 Cascading Synchronous Counters 456
8.8.3 Overview: TTL and CMOS Counters 458
8.8.3.1 TTL Counters 459
8.8.3.2 CMOS Counters 459
8.9 Design and Synthesis of Sequential Logic 460
8.10 Further Reading 467

9 Power Supplies 469

9.1 Power Transformers 469
9.2 Rectification and Filtering 470
9.2.1 Different Rectifier Circuits 472
9.3 Analogue Voltage Stabilisation 473
9.3.1 Voltage Stabilisation with Zener Diode 473
9.3.2 Analogue Stabilisation with Transistor 474
9.3.3 Voltage Regulation 475
9.3.3.1 Integrated Voltage Regulators 475
9.4 Switched Mode Power Supplies 476
9.4.1 Single-Ended Converters, Secondary Switched SMPS 477
9.4.1.1 Buck Converter 477
9.4.1.2 Boost Converter 479
9.4.1.3 Buck-Boost Converter 481
9.4.2 Primary Switched SMPS 482
9.4.2.1 Flyback Converter 482
9.4.2.2 Single-Transistor Forward Converter 486
9.4.2.3 Push–Pull Converters 489
9.4.2.4 Resonant Converters 491
9.4.3 Overview: Switched-Mode Power Supplies 494
9.4.4 Control of Switched-Mode Power Supplies 496
9.4.4.1 Voltage-Mode Control 496
9.4.4.2 Current-Mode Control 497
9.4.4.3 Comparison: Voltage-Mode vs. Current-Mode Control . 498
9.4.4.4 Design of the PI Controller 498
9.4.5 Design of Inductors and High-Frequency Transformers 499
9.4.5.1 Calculation of Inductors 499
9.4.5.2 Calculation of High-Frequency Transformers 500
9.4.6 Power Factor Control 504
9.4.6.1 Currents, Voltages and Power of the PFC 505
9.4.6.2 Controlling the PFC 506
9.4.7 Radio-Frequency Interference Suppression of Switched-Mode Power Supplies 507
9.4.7.1 Radio-Frequency Interference Radiation 507
9.4.7.2 Mains Input Conducted-Mode Interference 508

9.4.7.3 Suppression of Common-Mode Radio-Frequency Interference . . . 509
9.4.7.4 Suppression of Differential-Mode Radio Frequency Interference . . . 509
9.4.7.5 Complete Radio-Frequency Interference Filter . . . 510
9.5 Notation Index . . . 511
9.6 Further Reading . . . 512

A Mathematical Basics 513

A.1 Trigonometric Functions . . . 513
A.1.1 Properties . . . 513
A.1.2 Sums and Differences of Trigonometric Functions . . . 514
A.1.3 Sums and Differences in the Argument . . . 515
A.1.4 Multiples of the Argument . . . 515
A.1.5 Weighted Sums of Trigonometric Functions . . . 516
A.1.6 Products of Trigonometric Functions . . . 516
A.1.7 Triple Products . . . 516
A.1.8 Powers of Trigonometric Functions . . . 517
A.1.9 Trigonometric Functions with Complex Arguments . . . 517
A.2 Inverse Trigonometric Functions (Arc Functions) . . . 517
A.3 Hyperbolic Functions . . . 518
A.4 Differential Calculus . . . 518
A.4.1 Basics of Differential Calculus . . . 518
A.4.2 Derivatives of Elementary Functions . . . 519
A.5 Integral Calculus . . . 519
A.5.1 Basics of Integral Calculus . . . 519
A.5.1.1 Integrals of Elementary Functions . . . 520
A.5.2 Integrals Involving Trigonometric Functions . . . 521
A.5.3 Integrals Involving Exponential Functions . . . 523
A.5.4 Integrals Involving Inverse Trigonometric Functions . . . 524
A.5.5 Definite Integrals . . . 524
A.6 The Integral of the Standard Normal Distribution . . . 527

B Tables 530

B.1 The International System of Units (SI) . . . 530
B.1.1 Decimal Prefixes . . . 531
B.1.2 SI Units in Electrical Engineering . . . 532
B.2 Naturally Occurring Constants . . . 533
B.3 Symbols of the Greek Alphabet . . . 533
B.4 Units and Definitions of Technical–Physical Quantities . . . 534
B.5 Imperial and American Units . . . 535
B.6 Other Units . . . 537
B.7 Charge and Discharge Curves . . . 540
B.8 IEC Standard Series . . . 541
B.9 Resistor Colour Code . . . 542
B.10 Parallel Combination of Resistors . . . 543
B.11 Selecting Track Dimensions for Current Flow . . . 544
B.12 American Wire Gauge . . . 545
B.13 Dry Cell Batteries . . . 546
B.14 Notation of Radio-Frequency Ranges . . . 548
B.15 Ratios . . . 549
B.15.1 Absolute Voltage Levels . . . 549
B.15.1.1 Conversion of Power and Voltage Level Ratios . . . 550
B.15.2 Relative Levels . . . 551

B.16 V.24 Interface 552
B.17 Dual-Tone Multi-Frequency 553
B.18 ASCII Coding 554
B.19 Resolution and Coding for Analogue-to-Digital Converters 555
B.20 Chemical Elements 556
B.21 Materials 559

C Acronyms **561**

D Circuit Symbols **595**

Index **601**

Springer

http://www.springer.com/978-3-540-43965-3

Electrical Engineering
A Pocket Reference
Kories, R.; Schmidt-Walter, H.
2003, XXII, 626 p. 10 illus., Softcover
ISBN: 978-3-540-43965-3