

Index

- $I \cdot T$ product 21, 22, 42
- admittance
 - matrix 26, 275
 - positive-sequence 157
 - shunt 221, 222, 242, 253, 259, 265
 - zero-sequence 157
- arc
 - equipment 78
 - furnaces 3, 45, 78, 138
- ballast
 - core and coil 47
 - electronic 47
 - non-linear reactive 47
- cables 3
 - π model 221
 - ampacity 84
 - equivalent π model 241
 - series impedance 252
 - shunt admittance 252
 - frequency of oscillation 266
 - insulation breakdown 81
 - insulation loss 83
 - nominal π model
 - series impedance 241
 - shunt admittance 241
 - subsea 145, 221, 241
 - velocity of propagation 266
 - wavelength 266
- capacitance
 - mutual 151, 229
 - phase 152
 - positive-sequence 152, 232, 233
 - self 151, 229
 - sequence 152
 - zero-sequence 152, 232
- capacitor 25, 83, 86, 103, 105, 106, 112–117, 135, 283, 286, 287, 314, 326
 - bank 1, 3, 5, 30–33, 35, 36, 38, 39, 81, 85, 88, 104, 105, 113, 122, 136, 147, 282, 284
 - modelling 151
 - power factor correction 1, 3, 5, 30, 35
 - reactive power supply 3, 5, 30, 35, 111, 115
 - relocation 105
 - shunt 3, 145
 - switching 1, 35, 37, 39
 - voltage rise 30
 - current 31, 35
 - damage 85, 86
 - dielectric loss 83, 85
 - fuses 85
 - harmonic current 25
 - harmonic voltage 25
 - heating 85
 - ideal 83
 - loading 284
 - loss-of-life 85
 - MVA rating 38
 - overloading 85, 284
 - power factor correction 91
 - MVA rating 2
 - MVAr rating 276
 - voltage 2, 276
 - rated current 25
 - rated voltage 25
 - rating 86, 112
 - reactance 31, 112, 113
 - reactive power supply 41
 - relocation 111
 - series 153
 - shunt 41, 47, 151
 - size 116, 121
 - switching 31, 38, 85, 87, 103
 - thyristor-switched – TSC 47
 - tuning 106, 112–115
 - voltage 117, 284, 286, 288, 314

- voltage rating 115, 286
- charger 66
 - battery 46, 48
- circuit
 - admittance 26
 - communication 84, 103
 - control 84
 - de-tuning 3
 - detuning 105
 - electronic 103
 - equivalent 26
 - impedance 26
 - linear 83
 - magnetic 83
 - parallel 85
 - parallel RLC 26, 30, 43
 - phasor diagram 31
 - resonant 85
 - series RLC 26, 28, 43
 - telephone 103
- circuit breakers
 - interruption capability 103
- coil
 - chorded 97, 135
 - full-pitched 98, 99, 135
 - Petersen 339
 - pitching 92
 - span 94, 96, 99, 104, 111
- commutation 49, 66, 69, 73
- components
 - positive sequence 388
 - symmetrical 3, 386
 - zero sequence 388
- composite model 315
- conduction time 47
- conductor
 - ac resistance 223
 - common return 227
 - electric image 229, 238
 - geometric mean radius 223, 233
 - insulated 108
 - magnetic image 223
 - mutual resistance 223
 - neutral 223
 - outside diameter 229, 233
 - phase 223
 - self resistance 223
 - transposed 108
 - tubular 221
- connection
 - delta 15
 - ground 15
 - neutral 40
 - star-point 14
 - ungrounded wye 40
- converter
 - six-pulse 132
 - twelve-pulse 134
- converters 138
 - 12-pulse 72, 73, 75, 107, 209, 216
 - 18-pulse 73, 79
 - 24-pulse 73, 75, 79
 - 30-pulse 73, 79
 - 36-pulse 73, 79
 - 42-pulse 73, 79
 - 48-pulse 73, 79
 - 6-pulse 73, 107
 - phase current 10, 209
 - battery 66
 - commutation
 - dc-side current 66
 - smoothing effect 73
 - drives 315
 - firing angle 66
 - harmonic control 105
 - line-commutated 66
 - phase cancellation 3, 105, 107
 - phase current 71
 - phase multiplication 107
 - power 3, 41
 - power-electronic 1
 - three-phase 66
 - three-phase 6-pulse 66, 74
- coupling
 - inductive 21, 103
 - mutual 227, 228
- crest factor
 - current 21
 - voltage 21, 81, 91
- current
 - alternating 45
 - amplification 1
 - branch 277
 - chopped 47
 - distorted 47
 - double-frequency 92, 111
 - eddy 83, 111
 - fundamental 276
 - half-wave symmetric 10
 - harmonic 82
 - line 275
 - magnetising 82
 - peaky 40
 - negative sequence 92, 210
 - neutral 84
 - non-sinusoidal 40, 45, 47

- phase 84
- positive sequence 210
- primary 40
- rated 82
- sinusoidal 40
- spectrum 74, 75
- third harmonic 103
- third-harmonic 40
- waveform distortion 1
- zero sequence 103, 170, 387
- cycloconverters 45, 47, 107
- damping
 - critical 29
- devices
 - harmonic-producing 2, 26
 - instrumentation 103
 - metering 84, 103
 - non-linear 2, 3, 25, 26, 45, 81
 - saturable 78
 - semiconductor 41
 - thyristor-controlled 45
 - thyristor-involved 41
- distortion factor 25
 - current 16, 82, 275
 - voltage 16, 82, 275
- distribution boards
 - low voltage 145, 169, 315
- distribution transformer
 - MVA rating 2
 - percentage impedance 2
 - X/R ratio 2
- domain
 - frequency 15
 - phase 226
 - sequence 226
 - time 15, 278
- drives
 - converter 145, 169
 - dc motor 46, 48
 - variable frequency ac motor 47, 66
- efficiency 1, 35, 82
- electric
 - energy transmission 45
 - utility 1
- electromagnetic
 - induction 92
 - shield 108
- electronic controls 3
- emf
 - harmonic 40
 - induced 92, 93, 98, 101, 110
 - peaky 40
- equipment
 - communication 3
 - derating 81
 - electronic 1, 3, 84, 103
 - loss-of-life 84
 - protection 3
 - protection and control 103
 - ratings 1
 - regulation 35
 - thyristor-controlled 3
 - voltage regulation 1
- excitation 83
- factor
 - amplification 86, 88, 89
 - derating 108, 109, 372
 - distortion 2, 135, 275, 283
 - distribution 93–95
 - K- 108–110, 304, 325, 349, 364, 372
 - standardised 108
 - pitch 93, 94, 110, 111, 135
 - quality 28, 29, 106, 116, 117, 121, 136, 276, 281, 282
 - winding 93, 96
- feeders
 - reconfiguration 105
- field
 - magnetic 91
 - pulsating 92, 111
 - rotating
 - backward 92, 111
 - forward 92, 111
 - in opposite directions 92
 - rotor 91, 111
 - standing 92
- filer
 - second-order damped 296
- filter 3, 105, 145, 169, 315
 - 11 kV 136
 - 20 kV 125, 279
 - 22 kV 296, 340, 341
 - 33 kV 117, 123, 317, 358
 - 6.6 kV 136
 - 690 V 128
 - active 107, 130
 - anti-resonant 106
 - current 282–284, 286, 288, 314, 326
 - damped 106, 281, 323
 - first-order 106
 - second-order 3, 106, 121–123, 136, 281–283
 - third-order 106
 - detuned 106

- double band-pass 106, 107
- eleventh-tuned 114
- fifth harmonic 113
- fifth-tuned 284, 374, 375
- five-branch 128, 136, 340, 341
- four-branch 119, 125, 126, 278, 279, 317
- high-pass 106
- impedance 114, 116, 118, 120–123, 127, 281, 282, 296, 317, 319, 323, 340, 343, 346, 358, 361, 363
- impedance locus 119, 124, 130, 318
- impedance plots 125, 129, 298, 360
- one-branch 296
- passive 105–107
- rating 123, 283, 297, 317, 358
- series-tuned 3, 106, 116–118, 136, 281, 374, 375
- size 116, 121, 136, 276, 281
- three-branch 123–125, 358
- tuned 106, 281, 323
- tuning order 276
- type 276, 281
- voltages 283, 314, 326
- flux density 82
 - flattened 40
- Fourier series 3, 5, 7, 209
 - coefficients 52, 54, 58, 62
 - expansion 7, 10, 14, 15, 52, 58, 62
 - cosine terms 10
 - dc-component 10, 11, 52, 58, 62
 - sine terms 10, 11
 - time function 9, 11
- frequency
 - fundamental 2, 5, 16, 23–25, 31, 38, 83, 90, 93, 111–113, 278
 - natural 92
 - oscillation 255
 - resonant 26, 37, 38, 85, 86, 111, 112
 - scan 2, 26, 275
 - tuned 105, 112, 113, 115–117
 - tuning 106
- generator 3, 46, 78, 92, 105, 145
 - ac three-phase synchronous 92, 96, 99, 104
 - armature resistance 150
 - impedance 150
 - local 290, 373
 - negative-sequence reactance 150
 - rating 35, 91
 - subtransient reactance 150
 - synchronous 150
 - zero-sequence reactance 150
- grounding
 - Petersen coil 339
 - resistance 296, 316, 339, 358
 - solid 296, 316, 358
- harmonic
 - amplification 41, 85, 91, 290, 305, 350, 352, 373
 - analysis 209, 214, 216, 300, 321, 344, 361, 368
 - analysis programs 2, 26
 - balanced triplen currents 15
 - branch currents 3, 145, 169, 221
 - bus voltages 2, 3, 26, 145, 169, 221
 - cancellation 209, 214
 - characteristic 106, 290, 373
 - components 9, 11, 15, 96–98, 104
 - components – sinusoids 5
 - content 73
 - current
 - circulating 108
 - current distortion limits 141
 - current injection pattern 26
 - current spectrum 18, 22, 42, 76, 77, 79, 80, 142, 209, 214, 216, 358, 366
 - 12-pulse 209, 214
 - 6-pulse 209, 214
 - current waveform 298, 359, 367
 - currents 108, 275
 - negative sequence 92, 172
 - positive sequence 91, 172
 - triplen 46, 170, 277
 - distortion 1, 7, 81, 296, 305, 313, 324, 327, 335, 348, 350, 358, 366
 - distortion effects 3, 81
 - distortion factors 2, 105
 - distortion levels 290, 305, 324, 348, 350, 373
 - distortion limits 137, 283, 304, 324, 348, 364, 371
 - distortion measures 3
 - distortion results 2, 3, 145, 169, 221, 304–313, 324, 326–334, 336–338, 348, 349, 351–357, 364, 365, 371, 373
 - effects 3, 84, 91, 103
 - elimination 107
 - environment 86, 91, 92, 104, 109, 135, 283
 - filter 169, 296, 340, 358
 - flux 93
 - flux component 99
 - flux density 93

- frequency 2, 26, 38, 39, 85, 93, 105, 112
- impedances 2
- injection 303, 324, 348, 363, 371
- line currents 2, 26
- line voltage components 99
- nodal injection currents 26
- order 2, 24–26, 82, 93, 112, 113, 222, 253, 275
- phase sequence 14
- phase voltage components 99
- power flow analysis program 275
- power flow study 2, 26
- problems 2, 275
- solutions – preventive 105
- solutions – remedial 105
- situations 25
- studies 2, 3, 25, 145, 169, 221, 275
- case labelling 290
- trapping 112, 114, 116
- tuned 106, 112, 114
- voltage distortion limits 137
- voltages 85, 98, 101, 110, 275
- negative sequence 172
- positive sequence 172
- waveforms 5–7
- harmonic source 302, 303, 323, 325, 347, 363, 364, 370, 371
- classical, traditional 45
- current 2
- current pattern 22, 42
- current spectrum 275, 276
- fundamental current 276
- modelling and simulation 26
- modern, power-electronic 45
- harmonics 1–5, 15, 20, 81, 83, 84, 92, 94, 103
- characteristic 72
- characteristics 3, 5
- even 10, 11, 52, 58, 62
- even-order 10
- fundamental, fourth, seventh, ... 14
- fundamentals 5
- individual frequency 105
- non-characteristic 107
- odd 40
- origins 3
- second, fifth, eighth, ... 14
- triplen 14, 84, 108, 170, 276, 302, 323, 346, 363, 370
- triplen (third, sixth, ninth, ...) 14
- zero-sequence 47
- high voltage grid 3, 145
- model 147
- short-circuit equivalent 147
- HVDC transmission 45, 46
- impedance
- characteristic 86, 88, 89, 242, 253, 281
- dip 2, 26
- driving point 2, 26, 275
- equivalent 31, 39, 275
- equivalent system 255, 260
- harmonic 275
- matrix 26, 225, 275
- mutual 159, 228
- phase 158, 225
- positive-sequence 157, 228, 232
- rise 2, 26
- scan 2, 25, 275, 302, 305, 306, 308, 310, 311, 313, 323, 325, 328–331, 333, 335, 337, 338, 346, 347, 351, 353, 355, 357, 363, 370
- self 159, 228
- sequence 158, 225, 226
- series 221, 222, 242, 253, 259, 265
- mutual 222
- self 222
- surge 251
- system 32, 33, 36, 88, 89, 260, 276, 300, 303, 305, 307, 309, 311, 312, 321, 324, 332, 334, 336, 344, 347, 352, 354, 356, 361, 364, 368, 371
- zero-sequence 157, 228, 232
- in-plant point of coupling – IPC 138, 293, 372
- inductance 85, 112
- positive-sequence 233
- saturable, current-dependent 40
- inductor 24
- harmonic current 24
- harmonic voltage 24
- rated current 24
- rated voltage 24
- shunt 47
- industrial plants 2, 169
- inverter 45, 78
- dc/ac 66
- PWM 18
- six-pulse three-phase dc/ac 69
- three-phase bridge-controlled 67
- three-phase dc/ac 66
- iron core 82
- magnetisation 82
- laminations 83

- lights
 - fluorescent 3, 45, 46, 78
 - ignition 46
 - negative resistance 46
 - incandescent 103
 - mercury 78
- load 3, 145, 147
 - Δ -connected 155, 156
 - apparent power 35, 155
 - balanced 2, 84, 159
 - disruption 81
 - electronic 103
 - impedance matrix 158
 - individual 154
 - inductive 35
 - lumped 154
 - model
 - parallel 153
 - reactive element 153
 - resistive element 153
 - series 153
 - motor 290, 373
 - no- 91
 - non-linear 81, 91, 108
 - non-sinusoidal current 108, 372
 - passive 155, 290, 373
 - phase admittance matrix 156, 158
 - phase impedance matrix 158, 159
 - power factor 155
 - rated 91
 - reactive power 35
 - sequence admittance matrix 157
 - sequence impedance matrix 157, 159
 - three-phase 158
 - Y-connected 155, 157
- loss
 - angle 84
 - copper 81, 90, 91
 - dielectric 81, 83
 - eddy-current 82, 83, 91
 - hysteresis 82, 83, 91
 - insulation 83
 - iron 5, 81, 82, 91
 - line 1, 35
 - load 90
 - power 23, 83
 - stray 90
 - thermal 81
 - winding eddy-current 90
- magnetic
 - field 82, 83, 91, 92
 - flux density 93
 - materials 46, 82
 - saturation 83
- matrix
 - admittance 240
 - capacitance 152
 - cyclically symmetric 161
 - determinant 245
 - diagonal 159, 226, 237, 239
 - impedance 158, 240
 - perfectly symmetric 159, 225
 - phase impedance 225
 - reduced 224
 - sequence impedance 226
 - series impedance 236
 - shunt capacitance 230, 236
 - symmetric 158, 225, 240
 - transformation – A 3, 385
 - determinant 385
- modelling
 - frequency-dependent, detailed 26
- motor 78
 - X/R ratio 276
 - Δ -connected 164, 165, 167, 296, 316, 339
 - admittance 165
 - counter emf 48
 - dc 48
 - efficiency 164
 - equivalent circuit 160
 - high voltage 145, 169, 315
 - impedance 165, 276
 - induction 3, 145, 160
 - number of pole pairs 161
 - phase admittance matrix 161
 - phase impedance matrix 162
 - power factor 164
 - rating 276
 - rotor speed 161
 - sequence admittance matrix 161
 - sequence impedance matrix 161
 - shaft power 164
 - slip 161
 - speed 48
 - squirrel-cage induction 47
 - subtransient impedance 164
 - synchronous 47
 - synchronous speed 161
 - terminal voltage 48
 - voltage 276
 - Y-connected 164
 - zero-sequence impedance 164
- neutral 84, 108

- current 2, 108
- return path 40
- wire 170, 387
- derating 84
- oversizing 84, 108
- order
 - $h = pn \pm 1$ 72
 - resonance 37
 - tuning 113, 115, 281
- oscillation
 - torsional 92
- passive load
 - power factor 276
 - rating 276
 - voltage 276
- permeability 223
- permittivity 229
- phase shift 107
 - harmonic cancellation 209, 210, 214
- phase voltages
 - Fourier series representation 13
- pitch
 - pole 94, 96, 99, 104, 111
 - slot 95
- point of common coupling – PCC 138, 143, 276, 295
- power
 - absorption 24, 35
 - active 19, 20, 23
 - apparent 20, 35
 - delivery 25, 35
 - dissipation 23
 - distortion 20, 42
 - quality 1
 - reactive 19, 20, 24, 25, 35
 - sinusoidal 1
 - triangle 35
- power factor 1, 20, 21, 35, 83
 - actual 21
 - correction 41
 - displacement 20, 21
 - distortion 20
 - improved 35
 - low 35
 - original 35
 - unity 21
- power flow studies
 - formulation and solution 26
- power supply
 - ac 66
 - aircraft 66
 - dc 66
 - dc, regulated 46
 - space 66
 - switched-mode 2, 45, 76
- power systems 1, 30, 37, 81
 - ≤ 69 kV 16
 - balanced 15, 388
 - balanced three-phase 13, 14
 - bilateral components 10
 - complex 26, 275
 - component modelling 2, 145, 169, 221
 - equipment 81
 - equivalent impedance 37
 - harmonics 3, 4
 - industrial 145, 146, 169, 221, 275, 315, 316, 339
 - large 26
 - loads 81
 - simple linear 26
 - Thévenin equivalent 37
- protective relays 84, 103
 - electromechanical 103
 - ground 103
 - time delay characteristics 103
 - tripping 103
- reactance 112
 - ac line 49
 - capacitive 26, 112, 153
 - characteristic 113, 116, 117, 121
 - dc 50
 - inductive 26, 111–113, 115
- reactor 105, 106, 112, 114, 116, 283, 284, 326
 - current 121, 286, 288
 - loading 284
 - rating 284, 286, 287, 314
 - reactive power absorption 115
 - rms current 284
 - thyristor-controlled – TCR 47
 - tuning 106, 111
- rectifier 45
 - ac/dc 66
 - continuous current 56
 - diode 18, 77
 - discontinuous current 64
 - firing angle 50, 56, 60, 64, 70, 78
 - load voltage 50, 54, 56, 78
 - single-phase 131
 - single-phase center tap controlled 50, 60, 69
 - single-phase controlled 48, 58
 - single-phase full-wave diode 49

- six-pulse three-phase diode 131
- reliability 1
- resistance 23, 37, 82, 114
 - constant 23
 - earth 223
- resistivity 223
- resistor 23, 106, 283, 284, 326
 - current 121, 286, 288
 - harmonic current 24
 - harmonic voltage 24
 - power loss 122
 - rated current 24
 - rated voltage 24
 - rating 286, 314
- resonance 2, 3, 5, 25–27, 29, 32, 33, 36–39, 41, 84–86, 88, 89, 91, 105, 112, 113, 118, 137, 275, 283, 290, 296, 303, 305, 307, 309, 311–313, 324, 325, 327, 332, 334, 336, 347, 349, 350, 352–354, 356, 358, 364, 366, 371, 373
 - conditions 26, 145, 169, 221
 - order 37
 - parallel 2, 26, 28, 30, 111, 112, 255, 261, 266, 276
 - series 2, 26–28, 255, 261, 266
 - shifting 260, 290, 305, 307, 309, 311, 327, 332, 334, 336, 350, 352, 354, 356, 373
 - supersynchronous 92, 103
- response 15
- rotating machines 3, 45, 46, 81, 91, 105
 - armature 94
 - armature core 83
 - backward mmf 111
 - coil spanning 46
 - distorted mmf 46
 - fifth harmonics 46
 - heating 91
 - pole pitch 94
 - pole shoes 111
 - seventh harmonics 46
 - slot pitch 95
 - slots 95
 - sinusoidally distributed 46
 - stator 91
 - three-phase 46
- SCMVA 260, 290, 305, 350, 373
- sequence
 - $12n \pm 1$ 72
 - currents
 - negative 15, 72, 291
 - positive 72, 291
 - zero 15, 170, 171, 388
 - harmonics
 - negative 72, 172
 - positive 72, 172
 - negative 13, 14
 - phase currents
 - negative 171, 388
 - positive 171, 388
 - phase voltages
 - negative 170, 389
 - positive 170, 389
 - positive 13, 14, 170, 276, 302, 323, 346, 363, 370
 - voltages
 - negative 72, 291
 - positive 72, 291
 - zero 170, 389
 - zero 13–15, 46, 170, 277, 303, 324, 348, 364, 371
- short-circuit capacity 290
- short-circuit capacity – SCC 37, 86, 112, 113, 143, 260, 276, 291, 296, 300, 305, 307, 314, 323, 327, 332, 334, 336, 344, 349, 362, 373
- silicon controlled rectifiers – SCR's 45
 - asymmetrical 46
 - firing angle 48
 - light-activated 46
- skin effect 23, 81, 108, 146, 150, 173, 221
- standards 2, 3, 105, 137, 283
 - ANSI 72, 92, 172, 291
 - EN 50160 140
 - IEC 60289 284
 - IEC 60871-1 284–287, 314, 326
 - IEC 61000-2-2 138
 - IEC 61000-2-4 138, 295, 304, 325, 348, 364, 372
 - IEC 61000-3-2 141
 - IEEE 18 86, 283, 285, 287, 314, 327
 - IEEE 519 16, 22, 42, 91, 137, 294, 304, 324, 348, 364, 371
 - IEEE C57.110-1986 109
 - IEEE C57.12.00-1987 91
 - NORSOK E-001/2 141
- star-point
 - oscillation 40
- static VAR compensators 45, 47
- stress
 - insulation 81, 91
 - thermal 81
 - voltage 81
- superposition 83

- switchgear 155
 - high voltage 145, 169, 315
- symmetry
 - cyclic 161
 - even 10, 11
 - half-wave 10, 11, 52, 58, 62
 - odd 10
 - perfect 159, 225
- telephone interference 21
 - weighting factor 21, 22, 42
- thermal limit 92
- thyristors
 - bidirectional diode – diacs 46
 - bidirectional triode – triacs 45
 - gate turn off – GTO's 46
 - reverse blocking diode 46
 - reverse blocking triode 45
 - reverse conducting triode 46
 - static inductive 46
- torque
 - pulsating 91
- total harmonic distortion – THD 17, 18, 276
 - current 91
 - voltage 91
 - calculations 170, 277, 303, 324, 348, 364, 371
 - current 3, 16, 59, 63, 109, 143, 145, 169, 221, 284
 - results 290
 - variations 373
 - voltage 3, 16, 94, 96–98, 102, 137, 138, 140, 145, 169, 221, 307, 309, 311, 312, 332, 334, 336, 352, 354, 356
- transformation
 - modal 151, 230
 - similarity 151, 205, 230, 497
- transformer 3, 45, 66, 78, 81, 90, 105, 145, 147, 169, 315
 - X/R ratio 276
 - Δ –Y 172, 175, 186, 197, 199, 216, 421, 481, 488, 494
 - Δ – Y_g 109, 135, 184, 418
 - Δ –Z 204, 206, 496, 504
 - Δ – Δ 175, 188, 204, 206, 216, 366, 462, 496, 504
 - 11/3.6 kV 135
 - 110/20 kV 174
 - 11000/400 V 174
 - 11000/690 V 109, 217
 - 13.8/69 kV 218
 - 132/22 kV 216, 339, 352
 - 132/2x6/11 kV 214
 - 22/2x1.5 kV 211
 - 300/22 kV 36, 174, 296, 307
 - 300/2x9/16 kV 219
 - 300/33 kV 316, 332
 - 33/2x2.2 kV 218
 - 400/33 kV 217, 358
 - 4160/240 V 201
 - 450/220 V 366
 - 69/12.47 kV 217
 - 72/14.5 kV 203
 - admittance 173
 - connection 108, 170, 211, 475
 - delta 46, 170, 277
 - ungrounded wye 46, 170, 277
 - connection group 209, 210, 214
 - core 83
 - core heating loss 91
 - current 109, 135
 - Dd0 188, 205, 463, 498
 - Dd10 473, 503
 - Dd2 465, 499
 - Dd4 467, 500
 - Dd6 469, 501
 - Dd8 471, 502
 - delta-connected 46, 108
 - derating 91, 108, 109, 372
 - distribution 91
 - Dy_g1 184, 419
 - Dy1 186, 199, 203, 421, 488
 - Dy11 217, 218, 493
 - Dy3 489
 - Dy5 172, 173, 217, 490
 - Dy7 491
 - Dy9 492
 - four-winding 3, 169, 215, 216, 219
 - equivalent circuit 213, 214
 - impedances 213
 - harmonics 3
 - heating 91
 - impedance 173, 290, 308, 334, 354, 373
 - inductance 91
 - K-rated 108–110, 372
 - liquid-immersed 91
 - load 81
 - loss-of-life 91
 - magnetising current 46
 - non-sinusoidal 46
 - sinusoidal 46
 - third harmonics 46
 - model 169

- mutual admittance matrix 194, 216, 476
- MVA rating 276
- nameplate rating 81
- no-load 40
- non-harmonic rated 109
- outage 290, 307, 332, 352, 373
- percentage impedance 276
- phase admittance matrix 175, 179, 191, 192, 194, 195, 216, 391, 394, 396, 398, 400, 402, 404, 436, 438, 440, 442, 444, 446, 448, 450, 452, 454, 456, 458, 460, 475, 477, 478
- phase shift 73, 200, 206, 210, 494, 504
- power 46, 91
- rating 35
- regulating 91
- self admittance matrix 194, 216, 476
- sequence admittance matrix 175, 179, 181, 183, 185, 187, 189, 190, 195, 216, 391, 395, 397, 399, 401, 403, 405, 407, 409, 411, 413, 415, 417, 420, 422, 424, 426, 428, 430, 432, 434, 463, 465, 467, 469, 471, 473, 478
- short-circuit impedance 170
- single-phase 40
 - no-load magnetising current 40
- size 290, 373
- standard 110
- tertiary 211
- three-phase 46
 - connection 40
 - delta-connected primary 40
 - harmonics 40
 - wye-connected primary 40
- three-winding 3, 169, 212, 214, 216, 218
 - equivalent circuit 209, 210
 - impedances 209
- transformation ratio 177, 198, 200, 204, 206, 391, 481, 494, 496, 504
- transmission matrix 197, 199, 200, 202, 206, 216, 479, 494, 504, 506
- turns ratio 71, 177, 198, 204, 391, 481, 496
- two-winding 3, 169, 216
- vector group 172, 175, 194, 197, 199, 200, 204, 206, 216, 476, 482, 494, 496, 504
- Y-Y 10, 71, 175, 193, 204, 206, 216, 450, 496, 504
 - Y-Y_g 192, 448
 - Y-Z 199, 494
 - Y- Δ 71, 172, 175, 182, 197, 199, 216, 406, 481, 482, 494
 - Y_gd1 178, 394
 - Y_gd11 404
 - Y_gd3 396
 - Y_gd5 398
 - Y_gd7 400
 - Y_gd9 402
 - Y_gy_g0 189, 424
 - Y_gy_g10 434
 - Y_gy_g2 426
 - Y_gy_g4 428
 - Y_gy_g6 430
 - Y_gy_g8 432
 - Y_gy0 191, 436
 - Y_gy10 446
 - Y_gy2 438
 - Y_gy4 440
 - Y_gy6 442
 - Y_gy8 444
 - Y_g-Y 191, 436
 - Y_g-Y_g 189, 423
 - Y_g- Δ 178, 393
 - Yd1 182, 198, 406, 482
 - Yd11 416, 487
 - Yd3 408, 483
 - Yd5 410, 484
 - Yd7 412, 485
 - Yd9 201, 414, 486
 - Yy_g0 192, 448
 - Yy0 193, 205, 450, 498
 - Yy10 460, 503
 - Yy2 452, 499
 - Yy4 454, 500
 - Yy6 456, 501
 - Yy8 458, 502
 - Z-Y 199, 494
 - Z-Z 204, 206, 496, 504
 - Z- Δ 204, 206, 496, 504
 - zero-sequence equivalent network 170
 - zero-sequence impedance 170
- transmission line 3, 145, 147, 221, 241
 - π model 221
 - attenuation constant 242
 - characteristic impedance 246, 253
 - equivalent π model 241, 255, 260, 270
 - series impedance 252
 - shunt admittance 252

- frequency of oscillation 246, 253, 254, 261
- fully transposed 240
- incident current 243
- incident voltage 243
- lossless 251
- mutually-coupled 228
- nodal admittance matrix 234, 252
- nominal π model 241, 255, 260, 270
 - series impedance 241
 - shunt admittance 241
- outage 290, 373
- parameters
 - lumped model 241
 - uniform distribution 241
- phase constant 242
- propagation constant 242, 246, 253
- reflected current 243
- reflected voltage 243
- sag 223, 229, 233
- series impedance 222, 252
- shunt admittance 252
- shunt capacitance 229
- surge impedance 232, 233, 251
- transmission (ABCD) matrix 233
- transmission (ABCD) parameters 244
- transposed 225, 230
- velocity of propagation 232, 233, 246, 253, 254, 261
- wavelength 246, 253, 254, 261
- transformer
 - vector group 391
- uninterruptable power supplies – UPS's 66
- utility
 - grid infeed 290, 373
 - short circuit capacity 2
 - X/R ratio 2
- variable speed drive – VSD 133
- variable speed drives – VSD's 1
 - 12-pulse 169
 - 6-pulse 18, 80, 141
 - pulse-width-modulated (PWM) 80, 141
- voltage
 - amplification 1
 - base 37
 - bus 275, 277
 - distortion 40, 81
 - drop 1, 35, 40
 - fundamental 276
 - half-wave symmetric 10
 - line 96, 104, 388
 - line, rms 14
 - phase 96, 104, 388
 - phase, total rms 14
 - rated 37
 - regulation 35
 - rise 35, 38, 39
 - secondary 40
 - sinusoidal 40, 45, 46
 - waveform distortion 1
 - zero sequence 388
- waveform
 - basic 5
 - current 15, 19, 22, 42, 74–77
 - dc component 10
 - distorted 2, 5, 7, 15
 - even 11
 - half-wave symmetric 10, 11, 52, 58, 62
 - odd 10
 - periodic 2, 7, 15
 - rectangular 71
 - sinusoidal 1, 5
 - synthesis 8, 10, 11, 42, 52, 58, 62
 - time function 9, 11, 12, 54, 59, 62
 - voltage 15, 97, 98, 102, 135
- winding 46, 91, 94, 108
 - chorded 94
 - chording 94, 98, 110
 - concentrated 94, 95, 101, 102, 135, 136
 - damper 111, 135
 - distributed 94, 95, 100, 101, 135
 - distribution 92, 94, 110
 - fractional-pitch 94
 - full-pitch 94
 - full-pitched 136
 - primary 108, 210
 - quaternary 169, 214
 - secondary 19, 108, 169, 209–214
 - squirrel-cage 111
 - tertiary 169, 209, 210, 212–214
- wire
 - shield 223, 230



<http://www.springer.com/978-3-540-42238-9>

Power Systems Harmonics
Fundamentals, Analysis and Filter Design
Wakileh, G.J.
2001, XV, 506 p., Hardcover
ISBN: 978-3-540-42238-9