

---

# *Table of Contents*

<b>Preface .....</b>	<b>XI</b>
<b>1. Introduction .....</b>	<b>1</b>
1.1 Motivation .....	1
1.2 Car Radio History .....	5
References .....	9
<b>2. DSP Based Radio Receiver Architectures .....</b>	<b>11</b>
2.1 Radio Receiver Architectures .....	12
2.1.1 Heterodyne and Homodyne Receivers .....	12
2.1.2 DSP Based Radio Receiver Architectures .....	14
2.2 ADC Performance Metrics .....	17
2.2.1 Measures of Resolution .....	17
2.2.2 Measures of Linearity .....	18
2.3 Desensitization and Blocking .....	21
2.4 Image Rejection .....	24
2.5 Analog Radio Broadcasting .....	29
2.6 Digital Radio Broadcasting .....	30
2.7 Integrated Solutions for AM/FM Receivers .....	32
References .....	37
<b>3. Continuous-Time <math>\Sigma\Delta</math> Modulation .....</b>	<b>41</b>
3.1 Basic Principles .....	42
3.1.1 Oversampling .....	43
3.1.2 Noise Shaping .....	46
3.1.3 Anti-alias Filtering .....	48
3.2 High-Order $\Sigma\Delta$ Modulators .....	50
3.3 Tonal Behaviour .....	57
3.3.1 DAC Modulation at $f_s/2$ .....	59
3.3.2 2 <sup>nd</sup> -Order Non-linearity.....	61
3.4 Clock Jitter .....	65
3.4.1 Random Jitter .....	65
3.4.2 Deterministic Jitter .....	68
References .....	69

---

<b>4. <math>\Sigma\Delta</math> ADC Topologies for Radio Receivers .....</b>	<b>71</b>
4.1 Lowpass $\Sigma\Delta$ ADCs .....	72
4.1.1 Feedback Compensation .....	73
4.1.2 Feedforward Compensation .....	78
4.1.3 Feedforward and Feedback Compensation .....	81
4.1.4 Feedback Compensation with Local Feedforward Path .....	84
4.1.5 Resonators and Local Feedback .....	87
4.2 IF-to-Baseband $\Sigma\Delta$ ADCs .....	90
4.3 Quadrature IF-to-Baseband $\Sigma\Delta$ ADCs .....	93
4.4 Bandpass $\Sigma\Delta$ ADCs .....	102
4.4.1 Continuous-Time Bandpass $\Sigma\Delta$ Modulators .....	103
4.4.2 Continuous-Time Resonators .....	106
4.5 Quadrature Bandpass $\Sigma\Delta$ ADCs .....	109
4.6 Conclusions .....	111
References .....	113
 <b>5. IF-to-Baseband <math>\Sigma\Delta</math> ADC for AM/FM/IBOC Receivers .....</b>	 <b>117</b>
5.1 IF-to-Baseband Conversion System .....	118
5.2 IF Mixer .....	124
5.2.1 Mixer Linearity .....	125
5.2.2 Mixer Dynamic Performance .....	126
5.2.3 Isolated Mixer Topology .....	132
5.2.4 Mixer Driver .....	136
5.3 First Integrator .....	138
5.3.1 Design of the 1 <sup>st</sup> OTA To Be Used as a CT Integrator .....	140
5.3.2 Design of the 1 <sup>st</sup> OTA To Be Used as a SC Integrator .....	143
5.3.3 1 <sup>st</sup> OTA Transistor Level Design .....	149
5.4 High-Order Integrators and Resonators .....	152
5.5 Feedforward Coefficients and Quantizer .....	157
5.6 SC Feedback DAC .....	159
5.7 Experimental Results .....	163
5.7.1 First Prototype .....	164
5.7.2 Second Prototype .....	171
References .....	176

---

---

<b>6. Conclusion .....</b>	<b>179</b>
6.1 Benchmarking .....	179
6.2 Economic Feasibility .....	181
References .....	183
 <b>A. Harmonic Distortion in CT Integrators Using MOSCAPs .....</b>	 <b>187</b>
A.1 Introduction .....	187
A.2 Harmonic Distortion in Differential $G_m$ -C Integrators .....	189
A.3 Harmonic Distortion in Differential Feedback Integrators .....	192
References .....	195
 <b>B. Noise Analysis of CT <math>\Sigma\Delta</math> Modulators with SC Feedback DAC .....</b>	 <b>197</b>
B.1 Introduction .....	197
B.2 Noise Voltage PSD Across a Switched Capacitor .....	199
B.3 Input-Referred Thermal Noise Due to the SC Feedback DAC MOS Switches .....	201
B.3.1 “Direct Noise” Components.....	201
B.3.2 “Sampled-and-Held” Components.....	203
B.3.3 Input-Referred Noise .....	204
B.4 Input-Referred Thermal Noise Due to the SC Feedback DAC Reference Voltage .....	205
B.5 Input-Referred Thermal Noise Due to the OpAmp .....	206
B.6 Conclusion .....	208
References .....	208
 <b>List of Acronyms.....</b>	 <b>209</b>
 <b>List of Symbols.....</b>	 <b>211</b>
 <b>Index .....</b>	 <b>213</b>
 <b>About the Authors.....</b>	 <b>217</b>

<http://www.springer.com/978-1-4020-8163-7>

High-Resolution IF-to-Baseband SigmaDelta ADC for Car  
Radios

Silva, P.; Huijsing, J.

2008, XII, 217 p., Hardcover

ISBN: 978-1-4020-8163-7