

Contents

1	Components Description.	1
1.1	Cable	1
1.1.1	Electrical Parameters	3
1.1.2	Sequence Impedances	6
1.1.3	Example	7
1.1.4	Other Losses	10
1.2	Bonding Techniques	11
1.3	Cable Thermal Behaviour	12
1.3.1	Internal Thermal Resistances	13
1.3.2	External Thermal Resistances	15
1.3.3	Ampacity Calculation	16
1.3.4	Example	17
1.4	Shunt Reactor	19
1.5	Exercises	22
	References and Further Reading	22
2	Simple Switching Transients.	25
2.1	Laplace Transform	25
2.2	Switching of RL Circuits (or Shunt Reactors)	27
2.2.1	DC Source	27
2.2.2	AC Source	29
2.2.3	Summary	33
2.3	Switching of RC Circuits (or Capacitor Banks)	33
2.3.1	AC Source	34
2.3.2	The Importance of the Time-Step	38
2.3.3	Summary	39
2.4	Switching of RLC Circuits	39
2.4.1	DC Source	40
2.4.2	AC Source	42
2.4.3	Summary	45
2.5	Exercises	45
	References and Further Reading	46

3 Travelling Waves	47
3.1 Introduction	47
3.2 The Telegraph Equations	47
3.2.1 Time Domain	48
3.2.2 Frequency Domain	49
3.3 Impedance and Admittance Matrices of a Cable	51
3.3.1 Both Ends Bonded Cable	51
3.3.2 Cross-Bonded Cable	66
3.3.3 Three-Core Cables (Pipe-Type)	67
3.3.4 Summary	76
3.4 Modal Analysis	77
3.4.1 Method	77
3.4.2 Modal Velocities	84
3.4.3 Modal Attenuation	87
3.4.4 Summary	89
3.5 Frequency Spectrum of a Cable	89
3.5.1 Zero-Sequence	94
3.5.2 Summary	95
3.6 Reflection and Refraction of Travelling Waves	96
3.6.1 Line Terminations	98
3.7 Summary	99
3.8 Exercises	99
References and Further Reading	100
 4 Transient Phenomena	 103
4.1 Introduction	103
4.2 Different Types of Overvoltages	103
4.3 Switching Overvoltage	104
4.3.1 Single-Core Cables	105
4.3.2 Three-Phase Cables	107
4.3.3 Modelling of the Source	109
4.3.4 Influence of the Bonding	111
4.4 Energisation of Cables in Parallel	121
4.4.1 Estimation Formulas	123
4.4.2 Adjustment of the Inductance for High Frequencies	127
4.5 Zero-Missing Phenomenon	130
4.5.1 Countermeasures	133
4.6 De-Energisation of a Cable	137
4.7 Transient Recovery Voltage and Restrikes	142
4.7.1 Example and Influence of the Bonding Configuration	146
4.7.2 Cable and Shunt Reactor	147
4.8 Hybrid Cable-OHL	148
4.8.1 Energisation and Restrikes	148
4.8.2 Summary	153

4.9	Interaction Between Cables and Transformers	153
4.9.1	Series Resonance	153
4.9.2	Parallel Resonance	156
4.9.3	Ferroresonance	158
4.10	Faults	164
4.10.1	Single-Phase	165
4.10.2	Three-Phase Cable	171
4.10.3	Short-Circuit in a Cable Connected to a Shunt Reactor	184
4.10.4	Influence in the Short-Circuit of Other Network Equipment	186
4.10.5	Summary	190
	References and Further Reading	191
5	System Modelling and Harmonics	193
5.1	Introduction	193
5.2	Modelling Depth for Switching Studies	193
5.2.1	Theoretical Background	193
5.2.2	Calculation of the Modelling Depth	197
5.2.3	Modelling of the Cross-Bonded Sections	200
5.2.4	Possible Inaccuracies	202
5.2.5	Extended Method and Minimisation of the Inaccuracies	205
5.2.6	Equivalent Network	207
5.2.7	Systems with Cables and OHL	207
5.3	Harmonics in Cable-Based Systems	208
5.3.1	Introduction	208
5.3.2	Estimation of the Frequency Spectrum	209
5.3.3	Frequency Spectrums and Electromagnetic Transients	212
5.3.4	Sensitivity Analysis	213
5.3.5	Conclusions	214
5.4	Type of Cable Model for the Study of Different Phenomena	214
5.5	Systematic Method for the Simulation of Switching Transients	216
5.5.1	Demonstration	221
	References and Further Reading	227

Electromagnetic Transients in Power Cables

Faria da Silva, F.M.; Leth Bak, C.

2013, XIII, 229 p. With online files/update., Hardcover

ISBN: 978-1-4471-5235-4