

Contents

| | | |
|----------|-----------------------------------------------|-----------|
| 1 | Introduction. | 1 |
| 1.1 | Sensors | 1 |
| 1.2 | Transducers | 2 |
| 1.3 | Biosensors | 5 |
| 1.4 | Bioreceptors | 6 |
| 1.5 | Transducers for Biosensors | 12 |
| 1.6 | Overview of This Textbook | 13 |
| | References and Further Readings | 15 |
| 2 | Resistors | 17 |
| 2.1 | Electric Circuit | 17 |
| 2.2 | Current and Voltage | 17 |
| 2.3 | Resistance and Ohm's Law | 19 |
| 2.4 | Resistors in Series, or Voltage Divider | 20 |
| 2.5 | Potentiometer, or Pot | 22 |
| 2.6 | Resistors in Parallel, or Current Divider | 23 |
| 2.7 | Reading Resistor Values | 24 |
| 2.8 | Breadboards | 26 |
| 2.9 | Laboratory Task 1: Resistors in Series | 27 |
| 2.10 | Laboratory Task 2: Resistors in Parallel | 33 |
| 2.11 | Laboratory Task 3: "Droop" | 34 |
| 2.12 | Laboratory Task 4: Potentiometer (Pot) | 36 |
| 2.13 | Further Study: Thévenin's Theorem | 39 |
| | References and Further Readings | 40 |
| 3 | Diodes and Transistors | 41 |
| 3.1 | Semiconductors | 41 |
| 3.2 | Diodes | 42 |
| 3.3 | Zener Diode | 45 |
| 3.4 | Transistors | 47 |
| 3.5 | Operational Amplifier to Protect Your Circuit | 52 |
| 3.6 | Laboratory Task 1: LED | 54 |

| | | |
|----------|----------------------------------------------------------------------------|------------|
| 3.7 | Laboratory Task 2: Zener Diode | 56 |
| 3.8 | Laboratory Task 3: Transistor | 58 |
| | References and Further Readings | 61 |
| 4 | Temperature Sensors | 63 |
| 4.1 | Thermocouple | 63 |
| 4.2 | Thermistor | 65 |
| 4.3 | Diode Temperature Sensor | 66 |
| 4.4 | Transistor Temperature Sensor | 68 |
| 4.5 | Laboratory Task 1: Thermistor | 69 |
| 4.6 | Laboratory Task 2: Zener Diode Temperature Sensor | 71 |
| 4.7 | Laboratory Task 3: Transistor Temperature Sensor | 74 |
| | References and Further Readings | 78 |
| 5 | Wheatstone Bridge | 79 |
| 5.1 | Wheatstone Bridge | 79 |
| 5.2 | Strain Gauge | 81 |
| 5.3 | Cantilever Biosensor | 82 |
| 5.4 | Laboratory Task 1: Wheatstone Bridge | 84 |
| 5.5 | Laboratory Task 2: Wheatstone Bridge for a Thermistor | 85 |
| 5.6 | Laboratory Task 3: Wheatstone Bridge for a Strain Gauge | 88 |
| | References and Further Readings | 90 |
| 6 | Op-Amp | 91 |
| 6.1 | Op-Amp | 91 |
| 6.2 | Basics of Op-Amp | 91 |
| 6.3 | Voltage Follower or Buffer Op-Amp | 95 |
| 6.4 | Non-Inverting Op-Amp | 95 |
| 6.5 | Inverting Op-Amp | 97 |
| 6.6 | Summing Op-Amp | 98 |
| 6.7 | Differential Op-Amp | 98 |
| 6.8 | Laboratory Task 1: Non-inverting Op-Amp Operation | 99 |
| 6.9 | Laboratory Task 2: Signal Conditioning for Temperature Sensor | 102 |
| 6.10 | Further Study: Op-Amp Filters | 106 |
| | References and Further Readings | 108 |
| 7 | Light Sensors | 109 |
| 7.1 | Light | 109 |
| 7.2 | Photoresistor | 110 |
| 7.3 | Photodiode | 111 |
| 7.4 | Phototransistor | 115 |
| 7.5 | Light-Emitting Diode (LED) | 116 |
| 7.6 | Laser Diode | 118 |
| 7.7 | Laboratory Task 1: Photoconductive Operation | 120 |

| | | |
|-----------|-----------------------------------------------------------------------------------------|------------|
| 7.8 | Laboratory Task 2: Photovoltaic Operation | 123 |
| | References and Further Readings. | 126 |
| 8 | Spectrophotometry | 127 |
| 8.1 | Spectrophotometry | 127 |
| 8.2 | Spectrophotometry Biosensor Example: Pulse Oximeter. | 131 |
| 8.3 | Miniature Spectrophotometer | 133 |
| 8.4 | Optical Fibers | 136 |
| 8.5 | Laboratory Task 1: Hemoglobin Quantification with a Spectrophotometer | 140 |
| 8.6 | Laboratory Task 2: Hemoglobin Quantification with LED/PD Circuit | 146 |
| 8.7 | Laboratory Task 3: Meat Quality Monitoring with Reflection Probe | 148 |
| | References and Further Readings. | 151 |
| 9 | Fluorescence | 153 |
| 9.1 | Fluorescence | 154 |
| 9.2 | Fluorescent Dyes | 156 |
| 9.3 | Advanced Fluorescent Dyes: GFP, SYBR, and QD. | 159 |
| 9.4 | Autofluorescence | 161 |
| 9.5 | Detection of Fluorescence | 163 |
| 9.6 | Laboratory Task 1: 180° Back Scatter Fluorescence Detection for Fluorescein. | 165 |
| 9.7 | Laboratory Task 2: 90° Side Scatter Fluorescence Detection for Urine. | 168 |
| | References and Further Readings. | 170 |
| 10 | Electrochemical Sensors | 171 |
| 10.1 | Electrolytic and Electrochemical Cells. | 171 |
| 10.2 | Ion-Selective Electrodes (ISEs; Potentiometric). | 176 |
| 10.3 | pH Electrode (Potentiometric) | 178 |
| 10.4 | Amperometric Biosensors | 179 |
| 10.5 | Conductometric Biosensors | 180 |
| 10.6 | Laboratory Task 1: Buffer Preparations and Their pH Measurements | 182 |
| 10.7 | Laboratory Task 2: pH Meter Circuit | 186 |
| 10.8 | Laboratory Task 3: Fluoride Ion Selective Electrode with PH Meter. | 189 |
| 10.9 | Laboratory Task 4: Fluoride Ion Selective Electrode with Circuit | 191 |
| | References and Further Readings. | 192 |
| 11 | Piezoelectric Sensors. | 195 |
| 11.1 | Piezoelectricity | 195 |
| 11.2 | Pressure Sensors. | 198 |

| | | |
|-----------|----------------------------------------------------------------------------------------|------------|
| 11.3 | Crystal Oscillators | 198 |
| 11.4 | Quartz Crystal Microbalance (QCM). | 199 |
| 11.5 | Viscoelasticity Consideration in QCM. | 201 |
| 11.6 | Flow Cell QCM as Biosensor | 203 |
| 11.7 | Laboratory Task 1: Quantifying BSA Adsorption on QCM Sensor | 204 |
| | References and Further Readings. | 211 |
| 12 | Glucose Sensors | 213 |
| 12.1 | Optical Glucose Sensor | 213 |
| 12.2 | Electrochemical Glucose Sensor | 215 |
| 12.3 | Other Electrochemical Biosensors | 218 |
| 12.4 | Continuous Glucose Monitoring (CGM) | 219 |
| 12.5 | Laboratory Task 1: Glucose Assay Kit with a Spectrophotometer | 221 |
| 12.6 | Laboratory Task 2: Glucose Assay Kit with LED/PD Circuit | 224 |
| 12.7 | Laboratory Task 3: Commercial Electrochemical Glucose Sensor | 226 |
| | References and Further Readings. | 228 |
| 13 | Immunosensors | 229 |
| 13.1 | Enzyme-Linked Immunosorbent Assay (ELISA). | 229 |
| 13.2 | Antibodies | 232 |
| 13.3 | Antibody Fragments and Aptamers | 234 |
| 13.4 | Lateral-Flow Assay (LFA). | 236 |
| 13.5 | Optical Immunosensors | 238 |
| 13.6 | Surface Plasmon Resonance (SPR) Immunosensor | 239 |
| 13.7 | Electrochemical Immunosensors | 241 |
| 13.8 | Impedance Immunosensors: Interdigitated Microelectrode (IME) Immunosensor | 243 |
| 13.9 | Piezoelectric Immunosensors: QCM Immunosensor. | 244 |
| 13.10 | Immunosensing Kits Versus Handheld Immunosensors | 245 |
| 13.11 | Laboratory Task 1: Insulin ELISA Kit. | 246 |
| 13.12 | Laboratory Task 2: Insulin ELISA Kit with Smartphone Camera | 248 |
| 13.13 | Laboratory Task 3: Pregnancy Test (LFA) with Smartphone Camera. | 251 |
| 13.14 | Further Study: DNA Sensors | 254 |
| | References and Further Readings. | 255 |
| 14 | Lab-on-a-Chip Biosensors. | 257 |
| 14.1 | What Is Lab-on-a-Chip (LOC)? | 257 |
| 14.2 | How to Make LOCs: Photolithography and Soft Lithography | 259 |
| 14.3 | Early LOC: Capillary Electrophoresis (CE) | 263 |

| | | |
|-----------|-------------------------------------------------------------------------|------------|
| 14.4 | LOCs for Point-of-Care Testing (POCT) | 265 |
| 14.5 | Use of Optical Fibers in LOCs. | 267 |
| 14.6 | Sample/Reagent Introduction | 269 |
| 14.7 | Mixing in LOC | 270 |
| 14.8 | Paper-Based LOCs | 272 |
| 14.9 | LOC Sensing with a Smartphone Camera | 273 |
| 14.10 | Other Applications of LOCs | 274 |
| 14.11 | Laboratory Task 1: Fabrication of LOC by Soft Lithography | 275 |
| 14.12 | Laboratory Task 2: Mixing in LOC | 277 |
| 14.13 | Laboratory Task 3: Fabrication of a Paper-Based LOC | 280 |
| 14.14 | Laboratory Task 4: Bradford Assay with Paper-Based LOC | 284 |
| 14.15 | Further Study: Latex Immunoagglutination Assay (LIA) in LOC. | 287 |
| 14.16 | Further Study: Polymerase Chain Reaction (PCR) in LOC | 288 |
| | References and Further Readings. | 293 |
| 15 | Nanobiosensors | 299 |
| 15.1 | Gold Nanoparticles (AuNPs) | 299 |
| 15.2 | Quantum Dots (QDs) | 303 |
| 15.3 | Zinc Oxide (ZnO) Nanostructures. | 305 |
| 15.4 | Carbon Nanotubes (CNTs) and Graphene | 307 |
| 15.5 | Nanoporous Gold | 310 |
| 15.6 | Concluding Remarks. | 310 |
| | References and Further Readings. | 311 |
| | Appendix: Microcontroller | 313 |
| | Index | 325 |

Introduction to Biosensors

From Electric Circuits to Immunosensors

Yoon, J.-Y.

2016, XV, 331 p. 336 illus., 110 illus. in color.,

Hardcover

ISBN: 978-3-319-27411-9