

Contents

1	Introduction.	1
1.1	Review of Graph Theory.	1
1.1.1	Fundamental Cutsets (f-Cutsets).	4
1.1.2	Incidence Matrices	5
1.1.3	Kirchhoff's Laws	6
1.1.4	Primitive Network	6
1.1.5	Network Structure	7
1.1.6	Network Matrices.	8
1.1.7	Power Network	9
1.2	Iterative Load Flow	10
1.3	Issues with Iterative Load Flow	10
1.3.1	Premise.	10
1.3.2	Voltage Specification at PV Buses	10
1.4	Load Representation	10
1.5	Concept of Port	11
1.6	Matrix ξ	11
	References	12
2	Circuit Solutions	13
2.1	Multi-terminal Representation	13
2.2	Solution for Element Variables	14
2.2.1	Single Current Source.	14
2.2.2	Example	15
2.2.3	Single Voltage Source.	16
2.2.4	Example	16
2.2.5	Single Power Source.	17
2.2.6	Example	18
	References	19

3	Kirchhoff State	21
3.1	Kstate-Variables	22
3.2	Kpowers	22
3.3	Kvoltages	23
3.3.1	Example	23
3.4	The Superposition Challenge	25
3.5	Quantum Perspective	25
	Reference	26
4	Modular Load Flow	27
4.1	Concept of Modularity	27
4.2	Power Distribution in Kstates	30
4.3	Line Flows	30
4.4	Superposition of Line Flows	32
4.5	Voltages	32
4.6	Phase Angles	32
4.7	Modular Load Flow Algorithm	33
4.8	Comparison with Conventional Load Flow	34
4.9	HVDC, FACTS and DSG	35
	References	36
5	Load Flow Examples	37
5.1	The 3-Bus System	37
5.1.1	Results for 3-Bus System	37
5.2	The IEEE 30-Bus System	39
5.2.1	Results for 30-Bus System	42
5.3	The Ill-Conditioned 43-Bus System	44
5.3.1	Results for 43-Bus System	48
	References	50
6	Outage Analysis	51
6.1	Line Outage	51
6.1.1	Example	52
6.2	Power Flow Fractions Versus Distribution Factors	54
6.3	Identifying Outaged Generator	56
6.3.1	Example	56
6.4	Selective Computation of Line Flows	57
6.4.1	Example	57
	Reference	58
7	Voltage Behaviour	59
7.1	Problem Formulation	60
7.2	Modular Approach	61
7.2.1	Example: Ill-Conditioned System	63
7.3	Variation of Voltage	65
7.4	Voltage Dependency of Loads	65

7.5	PQ-reserve and PQ-deficit Condition	66
7.5.1	Example: The Switchover	67
7.6	Conclusion	69
	References	69
8	Optimization	71
8.1	Optimal Use of Injected Powers.	71
8.2	Multi-generator Case	72
8.2.1	Example	73
8.3	Load Voltage Optimization	74
8.3.1	Example	76
8.4	Flow Optimization	77
8.4.1	Example	79
8.5	Tieline Dispatch.	80
8.5.1	Example	81
8.6	State Estimation.	82
8.7	Conclusion	82
	References	83
9	Blackout Incipient	85
9.1	Introduction.	85
9.2	Limitations in Blackout Related Studies	86
9.3	Blackout-Incipient and Vulnerability.	86
9.4	The Indian Grid—Overview	87
9.5	Case Study 1: Grid Disturbance on 30th July 2012.	88
9.6	Load Representation.	89
9.7	Radial-Mesh Representation for Sub-grids.	90
9.8	Benchmarking	91
9.9	Algorithm	91
9.10	Case Study 2: Grid Disturbance on 31st July 2012.	97
9.11	Conclusion	101
	References	101
10	Dirac Structures.	103
10.1	Function Spaces with Inner Products	104
10.2	Hilbert Spaces and Orthoframes.	104
10.2.1	Relation Between Orthoframes.	105
10.3	Dirac Structures	107
10.3.1	Dual Spaces.	107
10.3.2	Duality Product	108
10.3.3	Bilinear Form	108
10.3.4	Orthogonal Complement	108
10.3.5	Dirac Structure: Definition.	109

10.4	Dirac Structure for Generators	109
10.5	Geometric Interpretation	109
10.5.1	Electrical Variables in Hilbert Spaces	109
10.5.2	Superposition of Dirac Structures	110
10.5.3	Example	111
10.6	Summary	112
	References	112

Modular Load Flow for Restructured Power Systems

Hariharan, G.; Varwandkar, S.D.; Gupta, P.P.

2016, XX, 113 p. 53 illus., Hardcover

ISBN: 978-981-10-0496-4